

(1)

Inductance

Recall From last lecture:

Self-inductance in a conductor causes a change in the magnetic field. This induces a voltage opposed to the applied voltage such that the change in conductor current is retarded (slowed).

Current-voltage relationship

$$V_L = L \frac{di}{dt}$$

↑ time
change in current



In DC circuits, causes a ~~slowing~~ slowing of the response to a step change in applied voltage

(see plots from previous lecture)

In AC circuits, causes a lag in the current response to the applied voltage



(2)

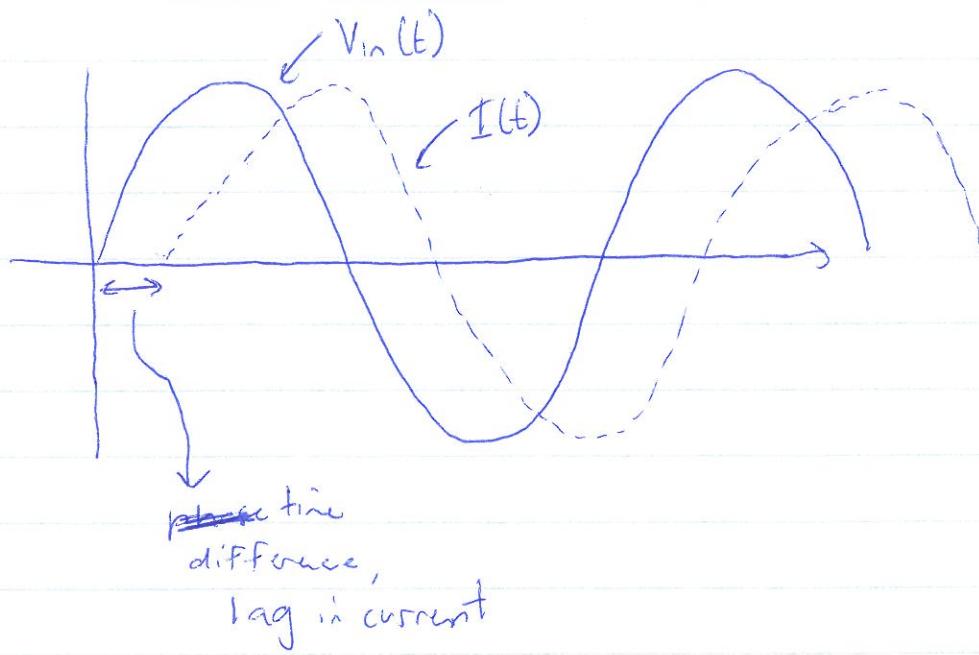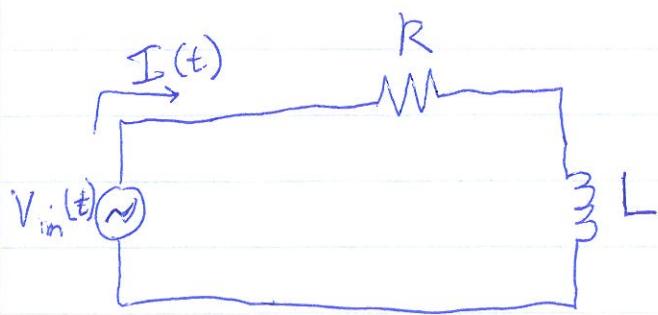

Inductive Reactance

In AC circuits, there is an additional opposition to current flow as compared to DC circuits. This is inductive reactance.

$$X_L = 2\pi f L$$

~~However~~ However, ~~because~~ this opposition is "out of phase" with the resistance.




(3)

Thus, total Impedance (resistive + reactive) is written as

$$Z = R + jX_L$$


\hookrightarrow imaginary indicates $+90^\circ$ out of phase.

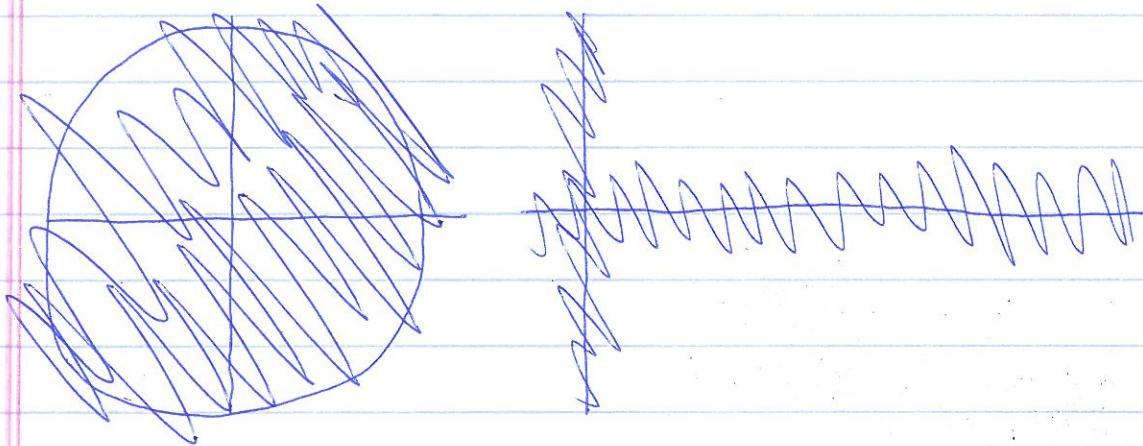Phasor Diagram - Impedance indicates the relationship of the amplitude and phase between voltage and current.




The total impedance of an RL circuit can be represented on a phasor diagram. Typically, resistance is shown on the horizontal axis and positive real or

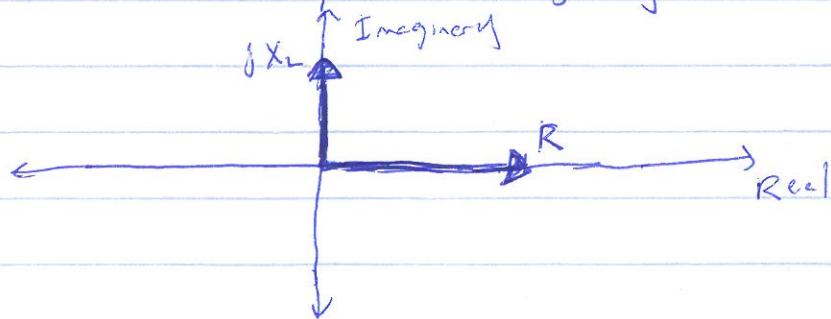inductance is shown on the positive imaginary or vertical axis.



4

Vector addition: Tip to tail!

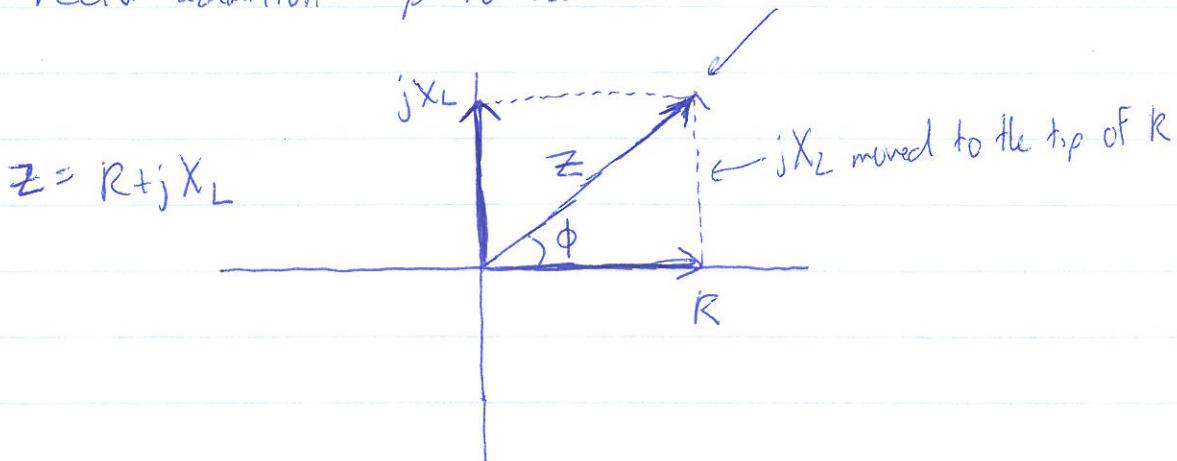


By pythagorean theorem: $Z = \sqrt{R^2 + X_L^2}$
 magnitude of impedance

Q Also phase Found as $\phi = \tan^{-1} \left(\frac{X_L}{R} \right)$

~~Diagram~~ Then $|V| = |I| |Z|$



Capacitance

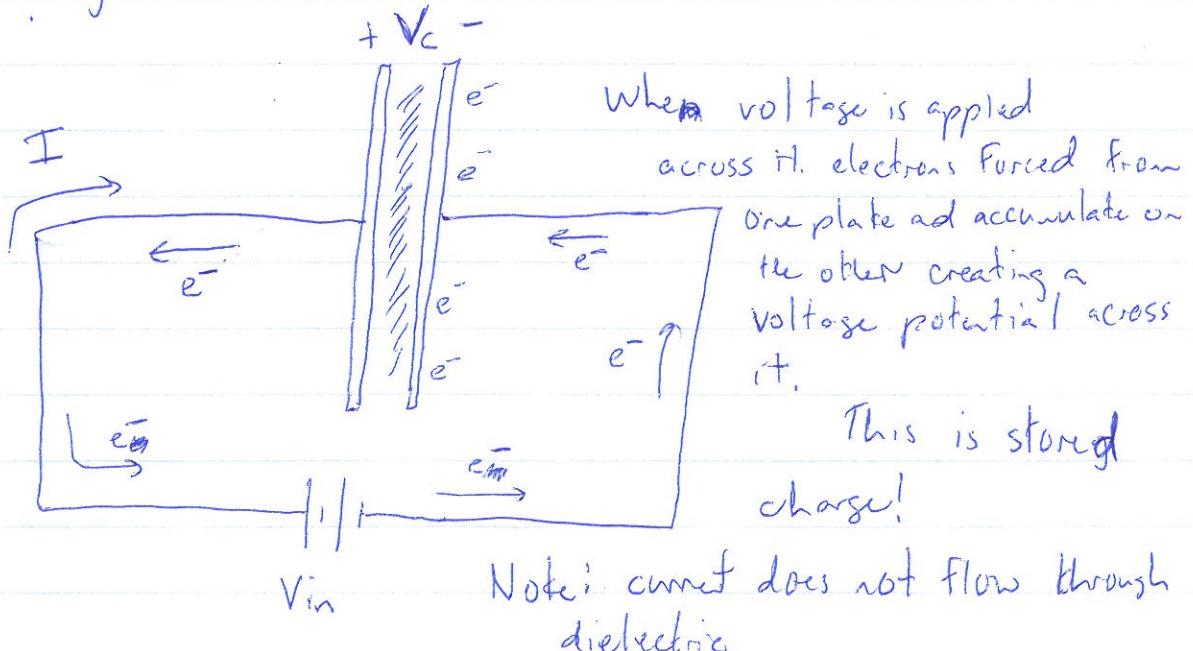Capacitor consists of two conductive plates separated by an insulating material, called the dielectric.




(5)

Effects on current flow:

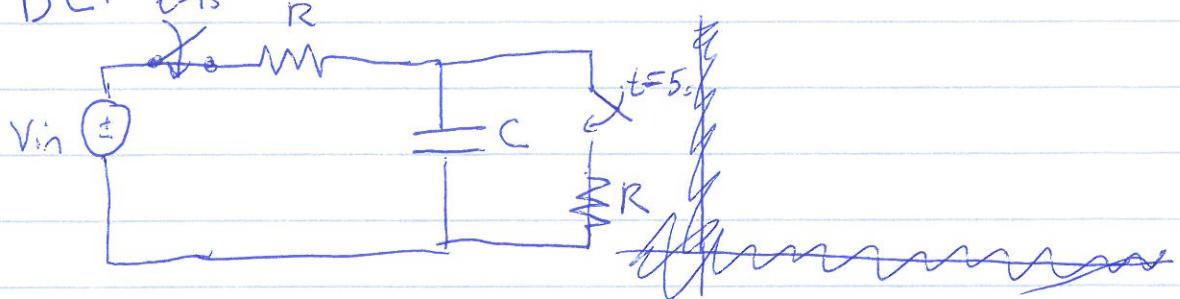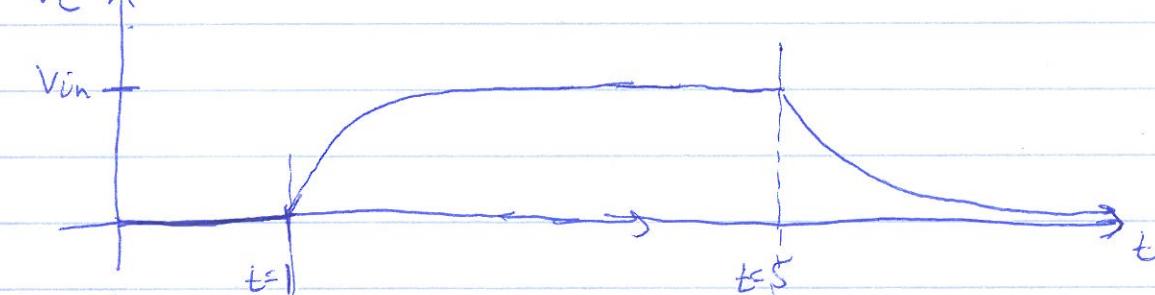DC: $t \leq 0$  V_C  I_C

$$I_{C\max} = \frac{V_{in}}{R}$$

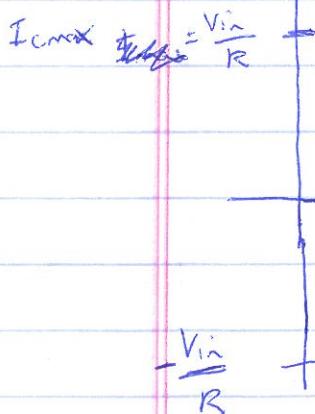

Capacitor units is the Farad (F)

Time constant \Rightarrow ~~time it takes for current to reach its maximum value~~, time it takes for ~~voltage~~ to reach its maximum value

But: Maximum value never "truly" reached, only asymptotically

(6)

$$\tau_c = RC \text{ units in seconds}$$

↳ time it takes to reach 63.2% of maximum.

Voltage / current relationship:

$$V_c(t) = \int \frac{1}{C} I(t) dt \quad \text{or equivalently} \quad I(t) = C \frac{dV_c(t)}{dt}$$

Size of capacitor:

$$C = \frac{Q}{V}$$

charge in coulombs
↓ voltage applied



capacity in Farads.

~~Variable capacitor~~



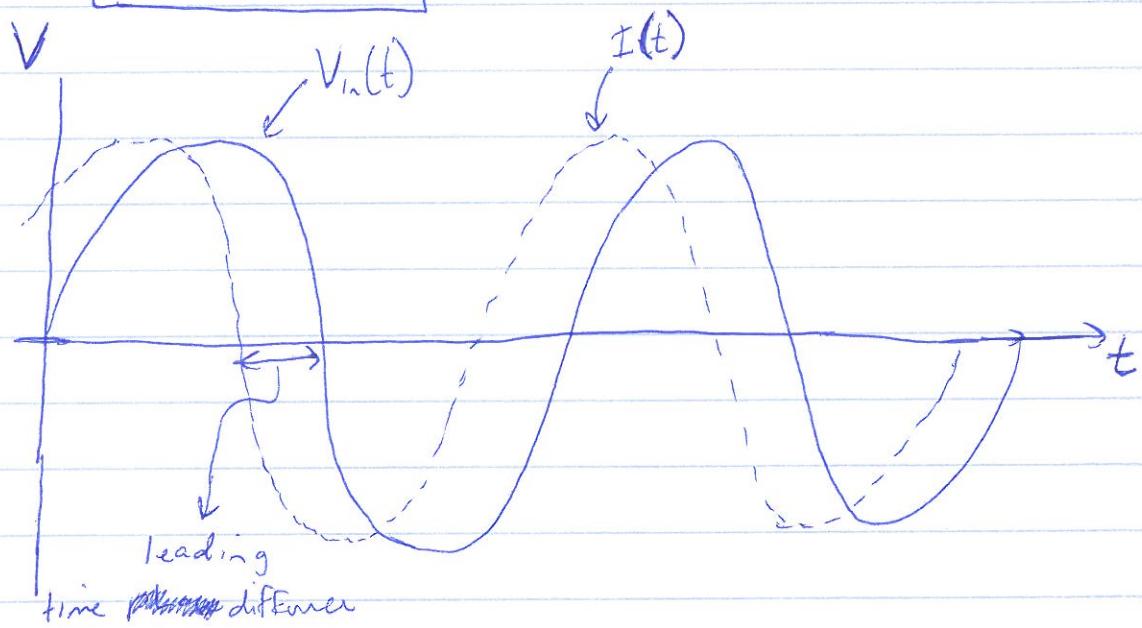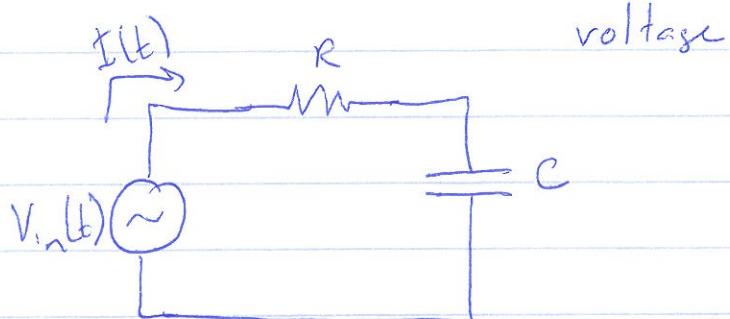(7)

Effect on AC circuit current: causes current to lead



Capacitive Reactance

$$X_c = \frac{1}{2\pi f C} \quad \text{unit in Ohms, } (\Omega)$$


however, similar to inductive reactance, this is "out of phase" with resistance. This time though, 90° leading so

$$Z = R - jX_c$$

$\hookrightarrow j$ is 90° out of phase

(8)

Phasors:

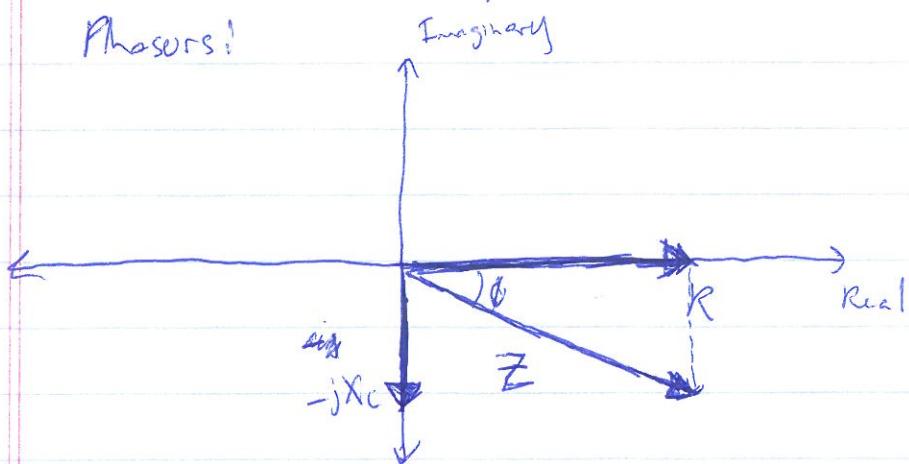

$$|Z| = \sqrt{R^2 + X_C^2}$$

$$\phi = \tan^{-1}\left(\frac{-jX_C}{R}\right)$$

So again $|V| = |I| |Z|$