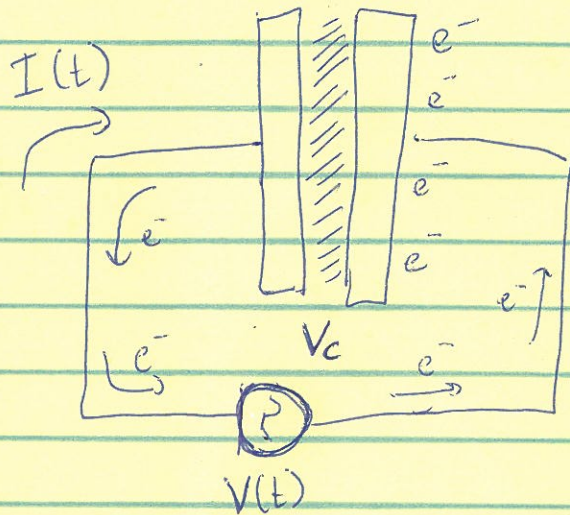


Lecture 11

①


Finishing capacitance

Why current leads voltage



For voltage to build on capacitor, ~~an~~ electrons must move.

Think about wave forms and equations

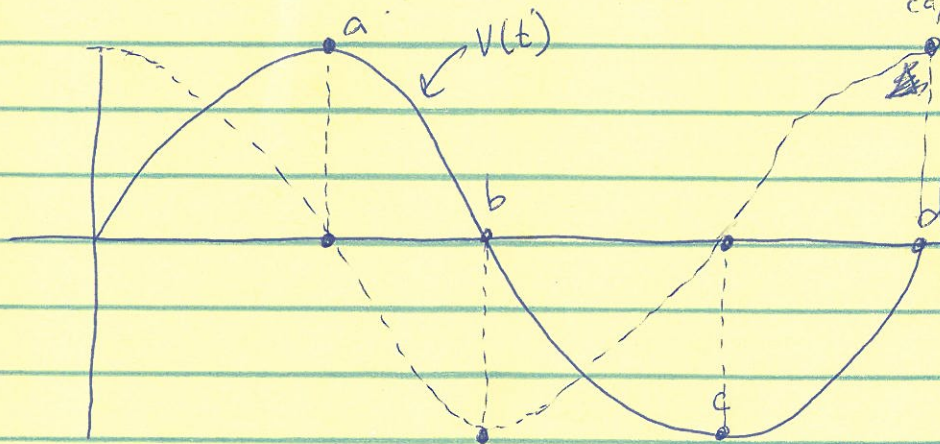

~~capacitance~~ \rightarrow voltage
 $CV = Q$
 \rightarrow charge

$I = \frac{dQ}{dt}$
 \rightarrow time rate
change in charge
is current.

a - Point a, voltage is at a peak and not changing very fast,
~~so~~ So, the flow of electrons through the circuit is relatively
small. ~~That~~ That is current is 0.

(2)

b - voltage across capacitor is 0V but changing quickly.

~~But~~, For voltage to change quickly, the charge on the cap must be changing quickly. Because voltage is going from positive to negative, \rightarrow Change in charge over ~~the~~ electrons must be moving change in time is current. From the negatively charged plate to the positive. Thus, current, which is in the opposite direction, is negative.

c - Voltage is peaking negatively and changing slowly, so current is near zero.

d - Voltage changing quickly so $\frac{\Delta Q}{\Delta t}$ ~~is~~ (i.e. current) is large,

and because voltage is going from negative to positive, current must be positive.


IF we connect the dots with a sine wave, we see current must lead voltage by 90° .

3

Capacitive Reactance:

$$X_c = \frac{1}{2\pi fC} \quad \text{units in ohms } (\Omega)$$

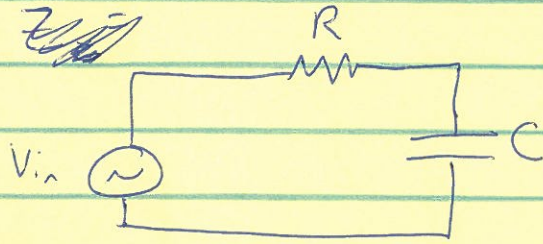
However, similar to inductance, this is "out of phase" with resistance. This time though, ~~90° lead~~ current leads voltage by 90° so in an RC series circuit,



$$Z = R - jX_c$$

\swarrow
 $\rightarrow -j$ means -90° out of phase

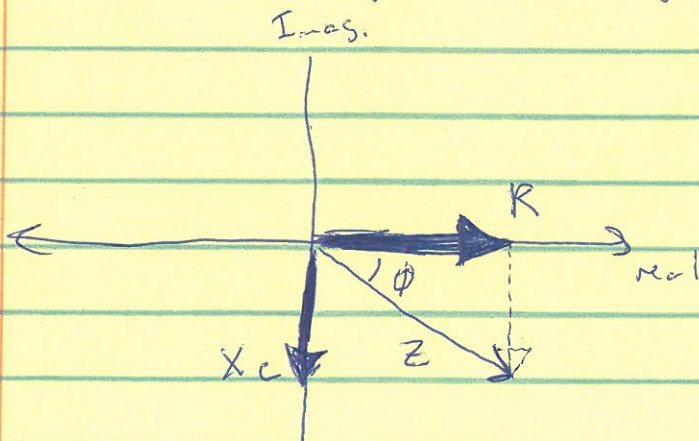So if we do our phasor diagram, and put R on the positive real axis, then capacitive reactance, X_c will be on the negative imaginary axis:



Then ~~we~~ we add the two to get impedance, Z total

(4)

Similar to inductance, we can bet the magnitude of this impedance as:

$$Z = \sqrt{R^2 + X_C^2}$$


And the total phase of the impedance as:

$$\phi = -\tan^{-1}\left(\frac{X_C}{R}\right)$$

Power in AC Circuits

purely capacitive


Use ~~R~~ circuit for example:

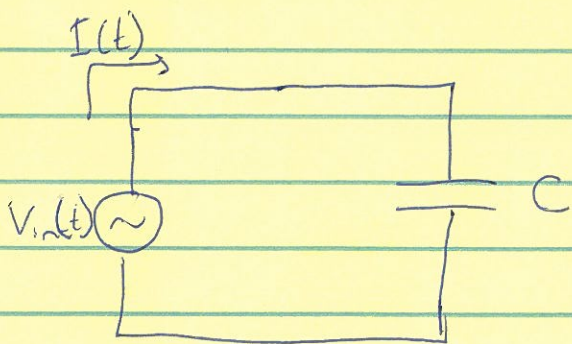



We know in purely capacitive circuit, current leads voltage by 90°



(5)

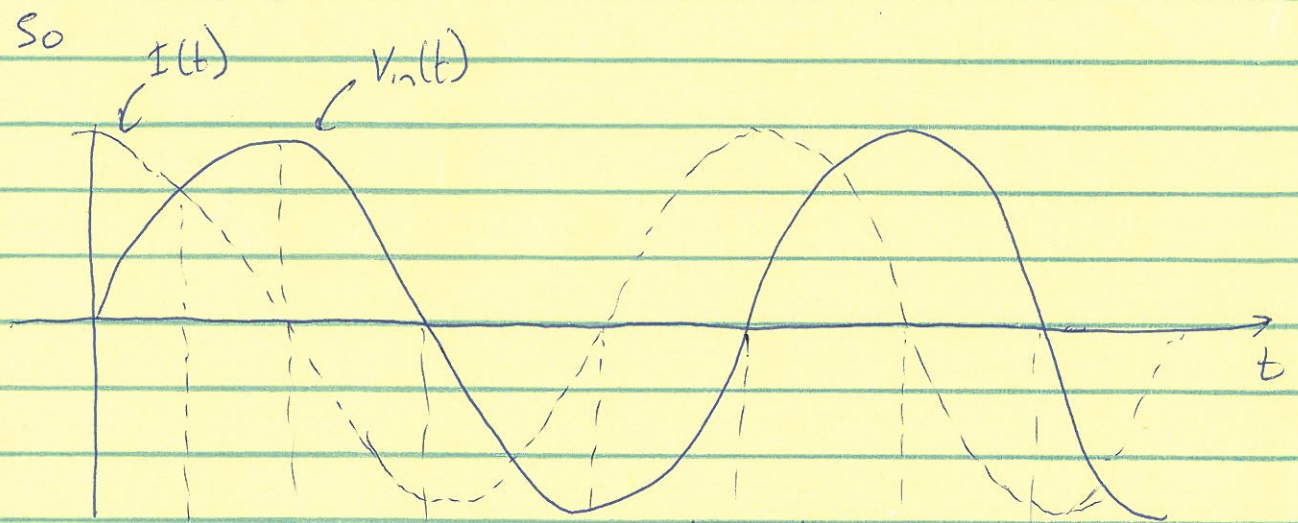

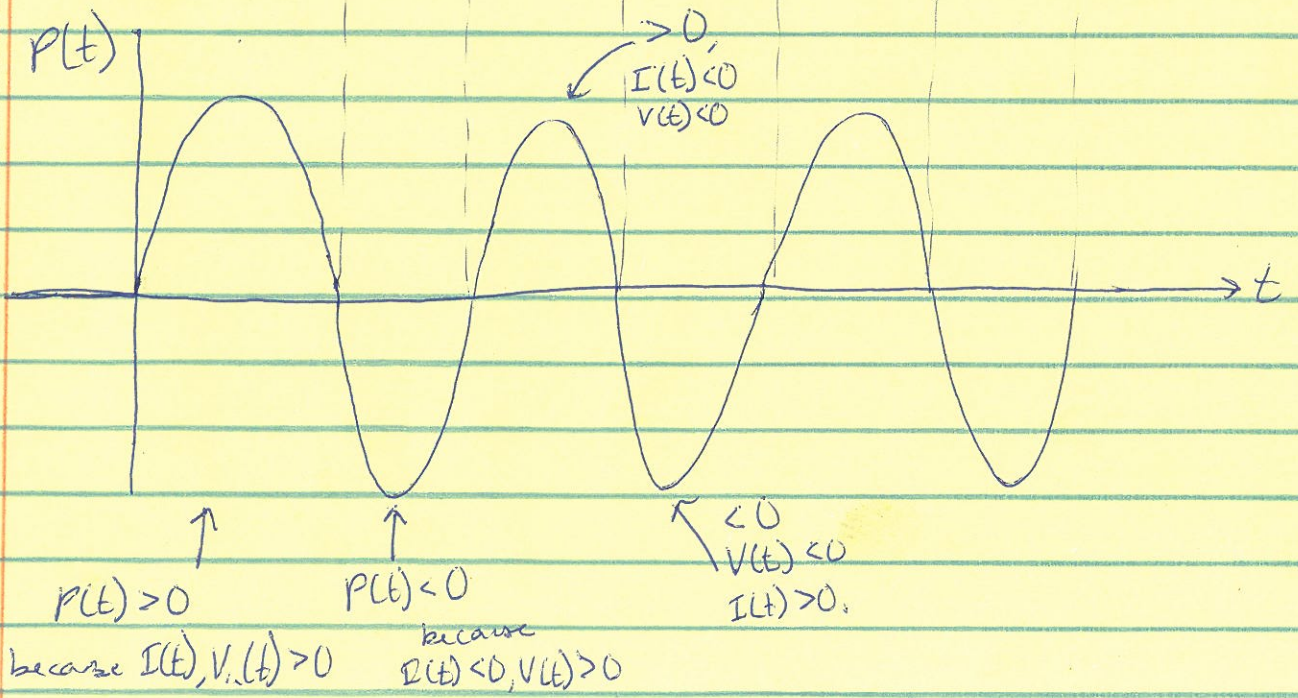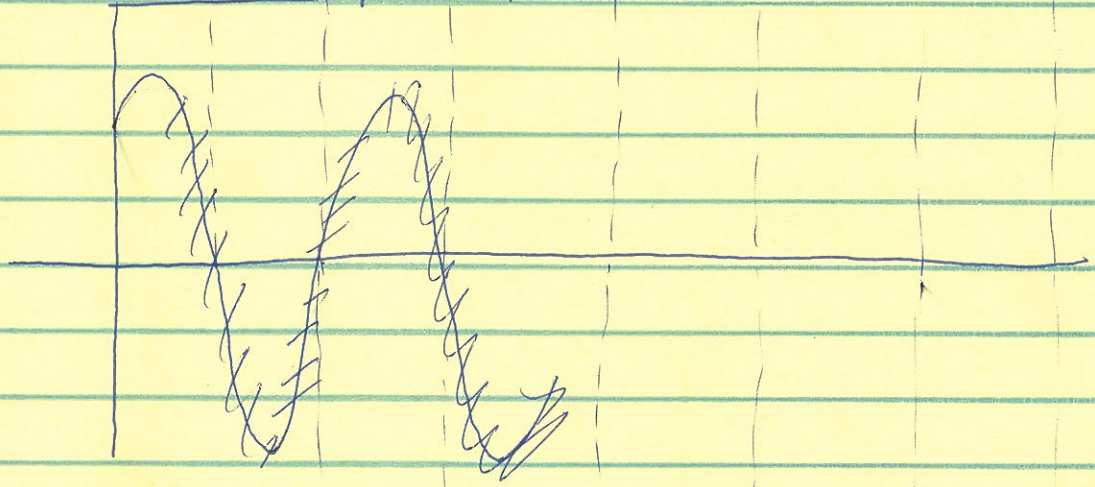Then instantaneous power $P(t) = V_{in}(t) I(t)$ is




⑥

- This net ~~power~~ power (average power) delivered to circuit is 0!!!
- Similar in ^{purely} inductive circuits.

What about RL or RC circuits: - Phase angle no longer $\pm 90^\circ$ so some effective power delivered.


~~Use R~~

RL as example:

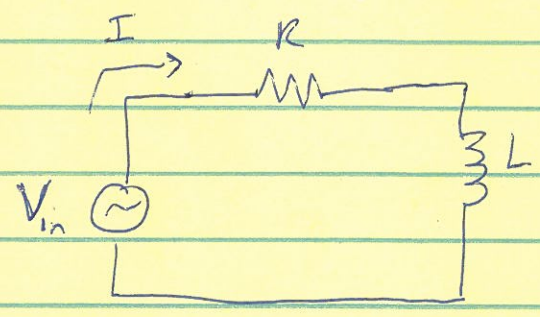


$$Z = R + jX_L$$

~~stop~~

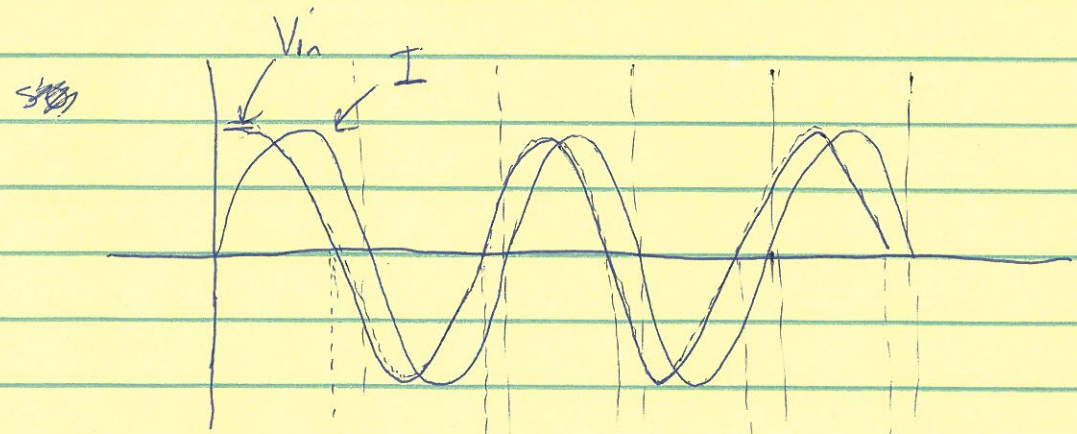

P(t)

Most power positive!

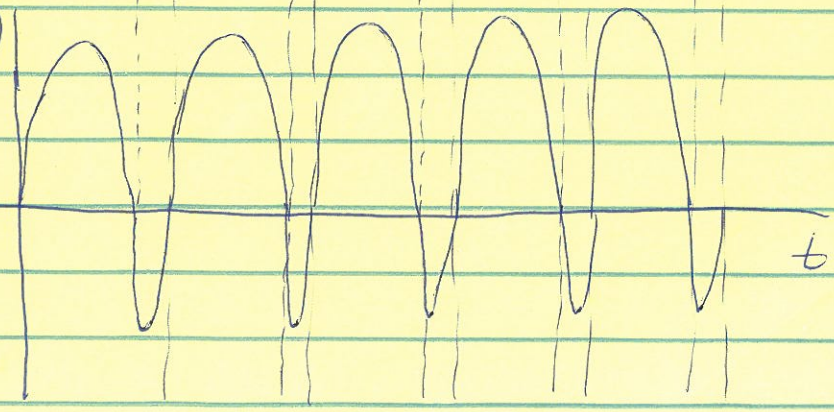

(7)

~~This~~ The average of this power is called the true power in your book. This is the power utilized in the circuit,

- The total power required by the circuit from the source through is larger. That is the apparent power!

~~So~~ The ratio of these two is called the power factor.

$$P_F = \frac{P}{P_{app}}$$

$$P_{app} = |V_{in}| |I| \leftarrow \text{So magnitudes of both, Ignore phase angle.}$$


Apparent power unit \rightarrow VA (volt-amps) to differentiate

The true power ~~is~~ in an RL series circuit is the power dissipated in ~~the~~ resistor only!

Why? Because voltage in resistor is in phase with the current. while voltage across inductor is 90° out of phase with current.

- ~~So~~ - Thus power in resistor is real power
- ~~So~~ - Power in inductor is reactive power (VAR)
- Apparent power is vector sum of the two. magnitude of

8

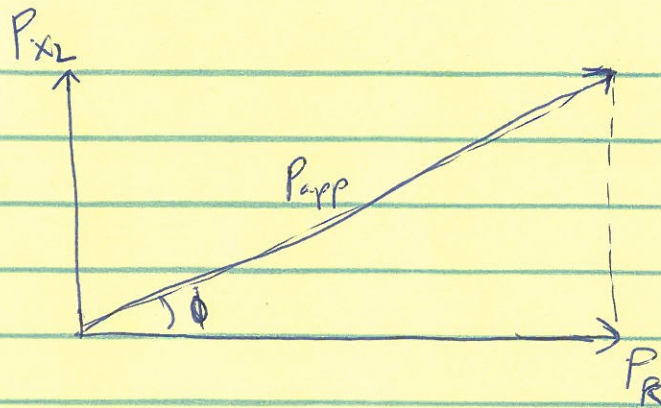

So ~~$P_{app} = |I|^2 Z$~~ $P_{XL} = |I|^2 X_L$

$$P = P_R = |I|^2 R$$

$$P_{app} = \sqrt{P_R^2 + P_{XL}^2}$$

also

$$P_{app} = |V_{in}| |I|$$

real power

so ~~$P = P_{app} \cos(\phi)$~~ also given by

$$P = P_{app} \cos(\phi)$$

ϕ is the same as that of the impedance.

$$P = \sqrt{P_{app}^2 - P_{XL}^2}$$