


# Lecture 13

①

Continuing on with AC circuits:

Parallel circuits continued:

RLC parallel circuit:

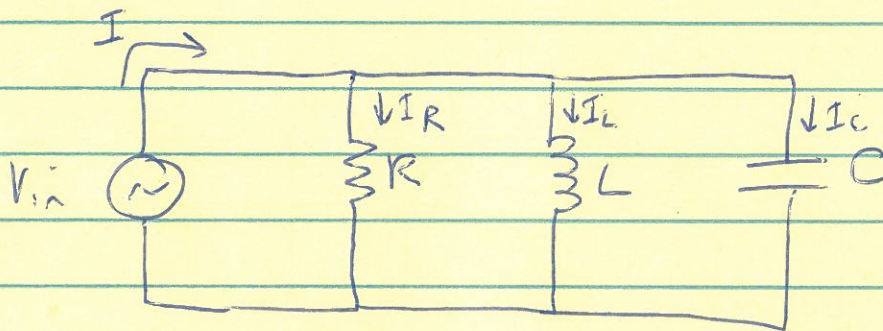

What we might want to know:

Z

I

$I_R$ ,  $V_R$

$I_C$ ,  $V_C$

$I_L$ ,  $V_L$

P

Q

S

$P_R$

$Q_L$

$Q_C$

As long as we consider both magnitude and phase, then

$$I = I_R + I_L + I_C \quad \text{From point 1}$$

$$V_{in} = V_R = V_L = V_C \quad \text{From point 2}$$

$$Z = \frac{1}{\frac{1}{Z_R} + \frac{1}{Z_L} + \frac{1}{Z_C}}$$

where

$$Z_R = R \quad (\text{no reactance})$$

$$Z_L = jX_L$$

$$Z_C = -jX_C$$

Phasor diagram

(2)

Since input voltage is common to all branches, we can use that as reference. So from Ohm's Law:

$$I_R = \frac{V_{in}}{R}$$

$$I Z_L = V_{in}$$

$$I Z_C = V_{in}$$

$$I(jX_L) = V_{in}$$

$$I(-jX_C) = V_{in}$$

Recall from math class:  $\frac{1}{j} = -j$


$$-\frac{1}{j} = j$$

$$\text{So } I_R = \frac{V_{in}}{R} \quad I_C = \frac{V_{in}}{-jX_C} = j \frac{V_{in}}{X_C} \quad I_L = \frac{V_{in}}{jX_L} = -j \frac{V_{in}}{X_L}$$

Does this make sense? Yes


Recall for inductor that current lags voltage by  $90^\circ$  and for capacitor, current leads voltage by  $90^\circ$ .

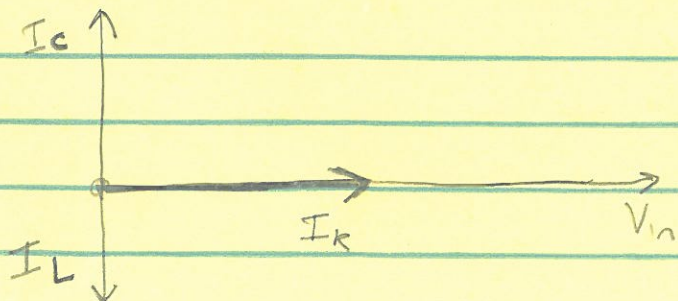If we draw these phasors with  $V_{in}$  as reference:



IF we add tip to tail

3

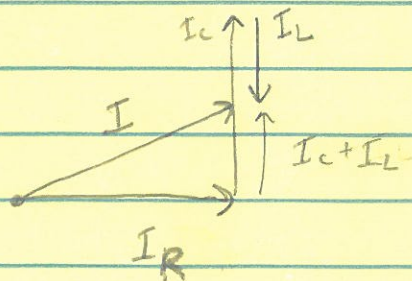

What about power?

!Re Since resistor current is in phase with applied voltage, power is real:

$$\begin{aligned} P &= I^2 R \\ P_R &= I_R V_{in} \\ &= I_R^2 R \\ &= \frac{V_{in}^2}{R} \end{aligned}$$

Since inductor current is out of phase with applied voltage power is reactive:


$$\begin{aligned} Q_L &= |I_L| |V_{in}| \\ &= |I_L^2| |jX_L| \\ &= \frac{|V_{in}|^2}{|jX_L|} \end{aligned} \quad \left. \begin{array}{l} \text{Since current lags voltage} \\ \text{reactive power is lagging by } 90^\circ \end{array} \right\}$$

Since capacitor current is out of phase with applied voltage, also reactive power:


$$\begin{aligned} Q_C &= |I_C| |V_{in}| \\ &= |I_C^2| |(-jX_C)| \\ &= \frac{|V_{in}|^2}{|-jX_C|} \end{aligned} \quad \left. \begin{array}{l} \text{reactive power } 90^\circ \text{ leading.} \end{array} \right\}$$

## Power phasor diagram:

(4)

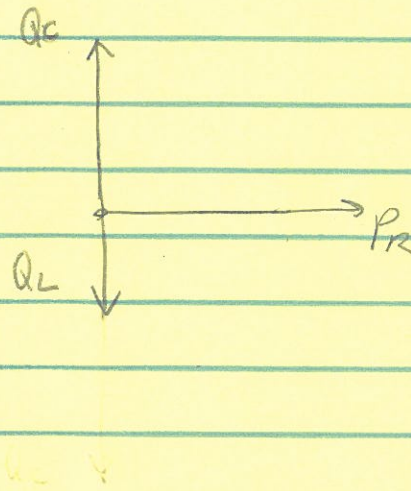

Adding tip to tail:

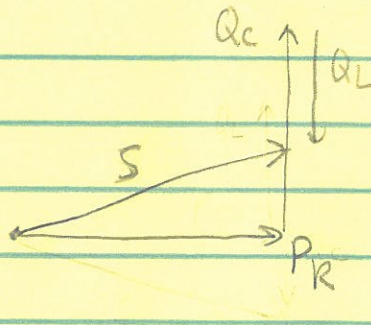

$$S = \sqrt{P^2 + Q^2} \quad \text{where } Q = Q_c - Q_L$$

So by having a capacitor in parallel with inductor, we can cancel out the reactive power


Let's do some examples

(5)

See example 5 in book

RLC series circuit:

$$V_{in} = 120V @ 60Hz$$

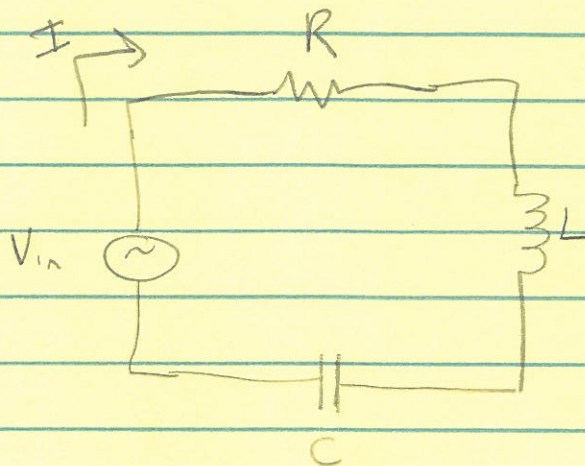

$$\text{Let } R = 5\Omega$$

$$C = 900\mu F$$


$$L = 0.02H$$

First, rewrite circuit with impedance values:

First

$$X_L = 2\pi fL = 7.54\Omega$$

$$X_C = \frac{1}{2\pi fC} = 2.95\Omega$$

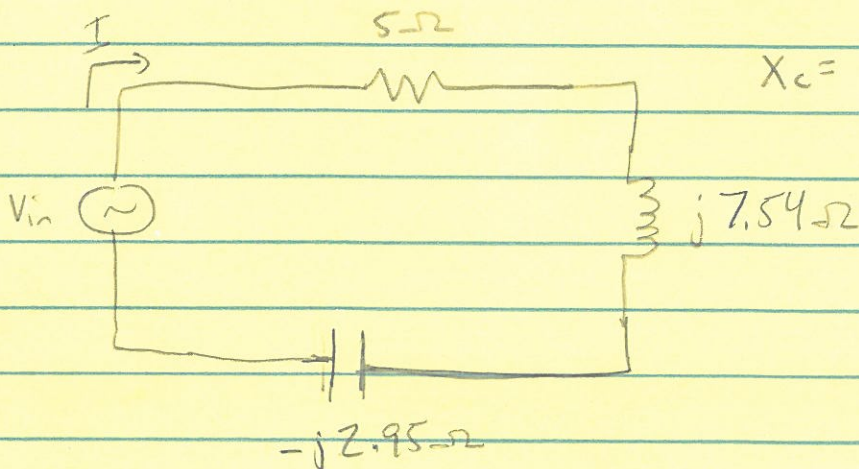

So what if all I cared about was finding  $I$ ,  $P$ ,  $Q$ ,  $S$  and PF

That is, I'm not concerned with individual voltages?


Then start with  $Z$  and find rest:

(6)

$$Z = Z_R + Z_L + Z_C, \quad Z_R = R \quad Z_L = jX_L \quad Z_C = -jX_C$$

then  $Z = 5 + j7.54 - j2.95$

$$Z = 5 + j4.59$$

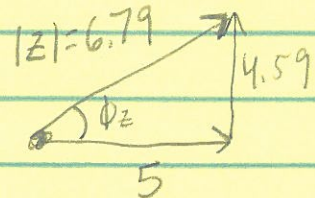

$$|Z| = 6.79, \quad \phi_Z = \tan^{-1} \frac{4.59}{5} = 43^\circ$$

$$\text{So } |I| = \frac{|V_{in}|}{|Z|} = \frac{120}{6.79} = 17.7 \text{ A}$$

$$S = |V_{in}| |I| = 120 \cdot 17.7 = 2.1 \text{ kVA}$$

$$\text{PF} = \cos \phi = 0.74$$


$$\text{PF} = \frac{P}{S} \Rightarrow P = S \cdot \text{PF} = 1.56 \text{ kW}$$

$$Q = \sqrt{S^2 - P^2} \Rightarrow Q = \sqrt{2.1^2 - 1.56^2} = 1.43 \text{ kVAR}$$

And  $I_{in}$  done.

Now if I want voltages:

Use  $I$  as reference and

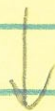


$$V_R = IR$$

$$V_R = 88.5 \text{ V}$$

$$|V_L| = |I| |jX_L|$$

$$= j 133 \text{ V}$$

$$|V_C| = |I| |F - jX_C| = 52.2 \text{ V}$$

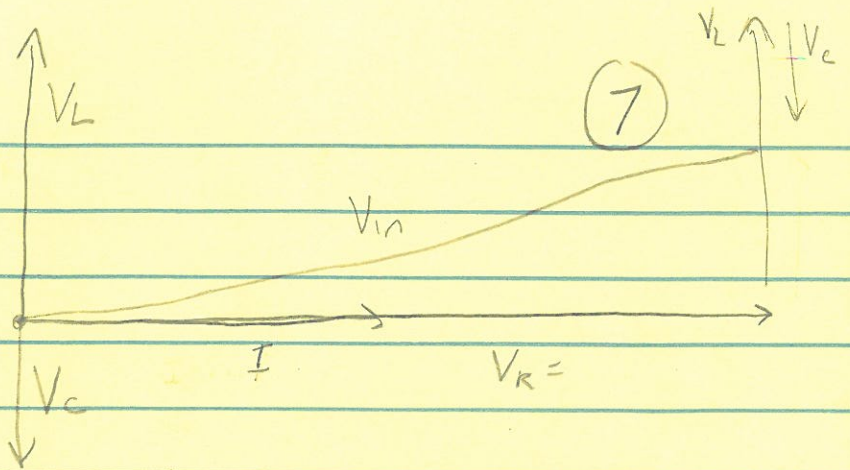

Double check to make sure numbers are correct?

should be:

$$|V_{in}| = 120$$

$$|V_{in}| = \sqrt{V_R^2 + (V_L - V_C)^2}$$


$$= \sqrt{88.5^2 + 80.8^2} = 119.8 \checkmark$$

where we  
left off

## RLC Parallel Circuit

Example 14 in book:

Let

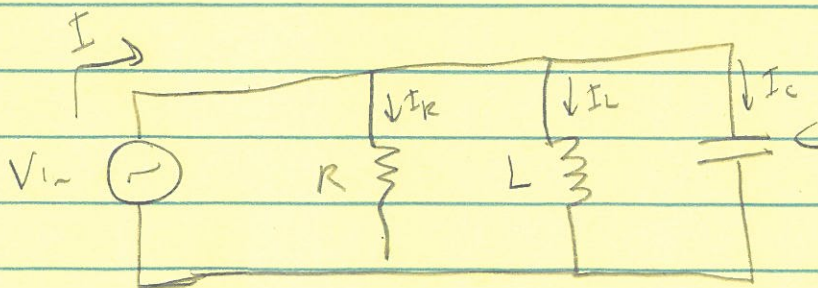

$$V_{in} = 120 \text{ @ } 60 \text{ Hz}$$

$$R = 30 \Omega$$

$$L = 0.531 \text{ H}$$

$$C = 6.3 \mu\text{F}$$

Re write using impedance values;