


Lecture 17: Three-Phase Systems



Autotransformers

Autotransformers

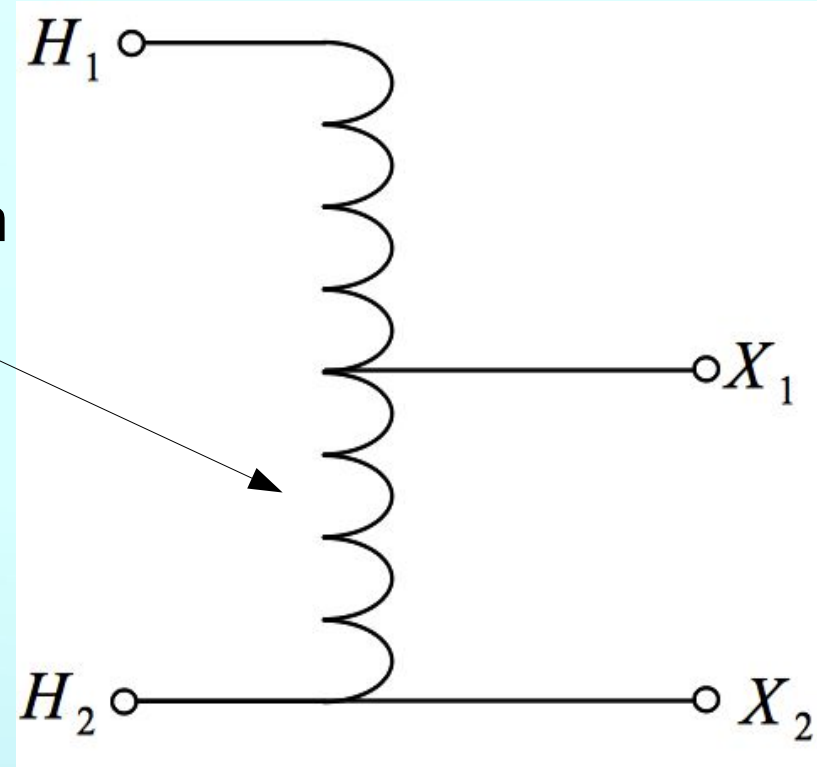- Only has one winding
 - One portion of winding for both primary and secondary
- Standard equations still apply
- Require less copper
 - Cheaper
 - Smaller
- Disadvantage is more hazardous



Three-Phase Systems

- Why generate in three-phase?
 - More efficient generation/transmission/use
 - Three-phase equipment smaller per unit power
 - Easy to create rotating magnetic fields (motors)
 - Smoother power transfer
 - Smoother torque in motors
 - Smoother conversion to DC (e.g. for battery storage)
 - Cost effective transmission
 - Less conductors required
- If we generate/transmit in three-phase, how do we get single-phase?
 - Tap into single leg of three-phase using transformer

Three-Phase Systems

- AC electricity primarily generated and transmitted in the form of three-phase
 - Each phase voltage 120° apart


If load balanced,
current 120° apart as
well

Typical Color Scheme:

Phase 1


Phase 2

Phase 3

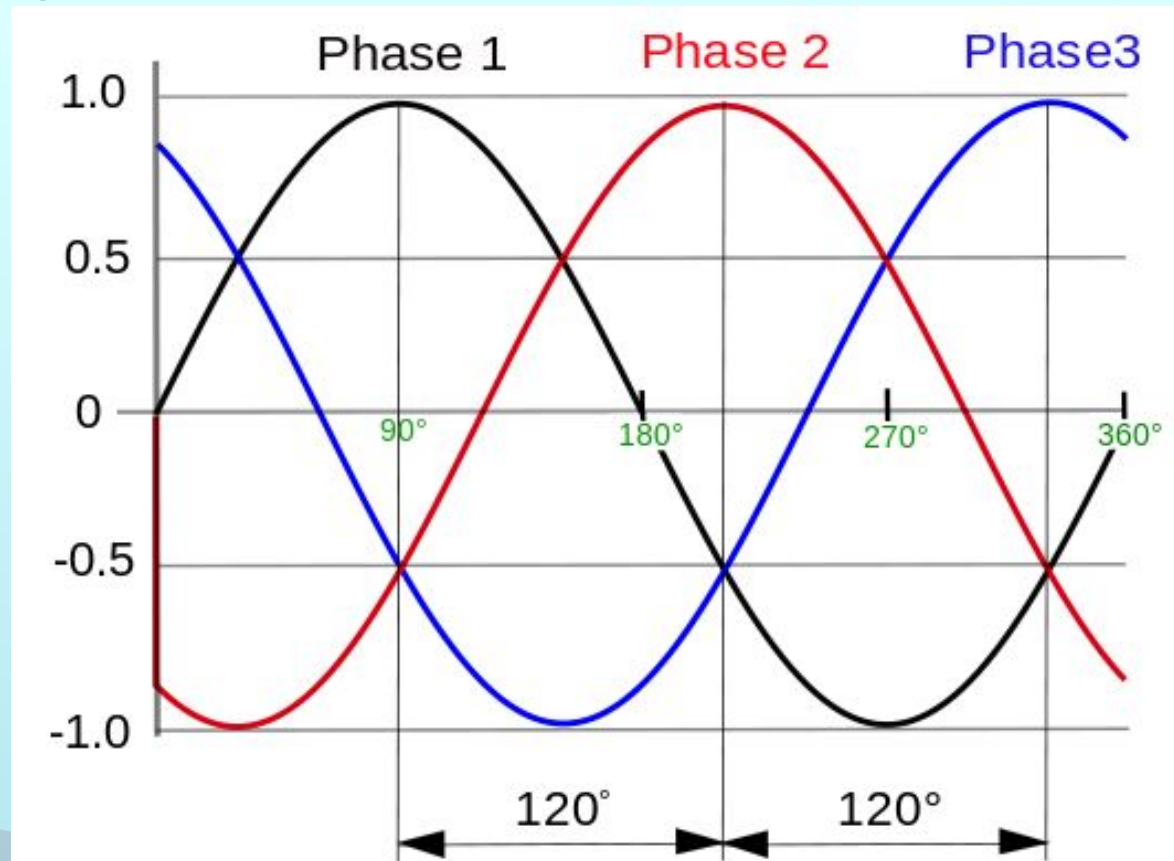

Balanced Loads

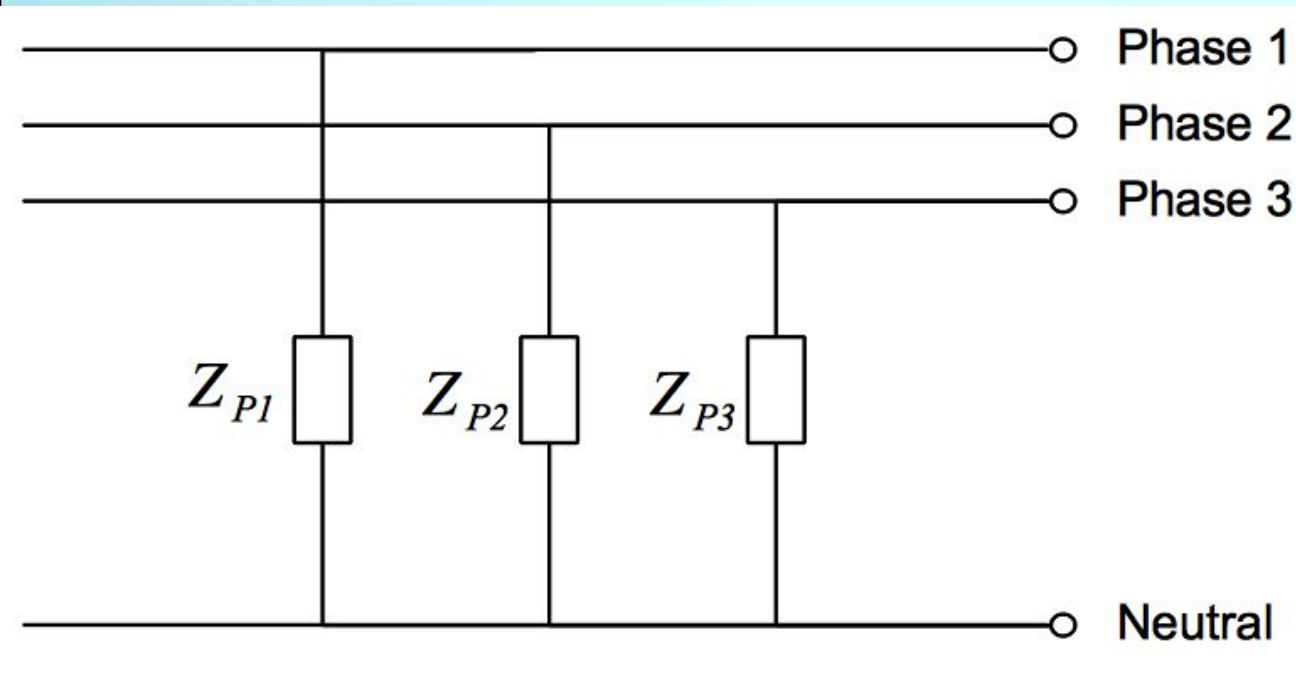- What is a balanced load?
 - All branches of load have equivalent impedance





All phase impedances equivalent:

$$Z = Z_{P1} = Z_{P2} = Z_{P3}$$



Balanced Loads

- Balanced generation with balanced load

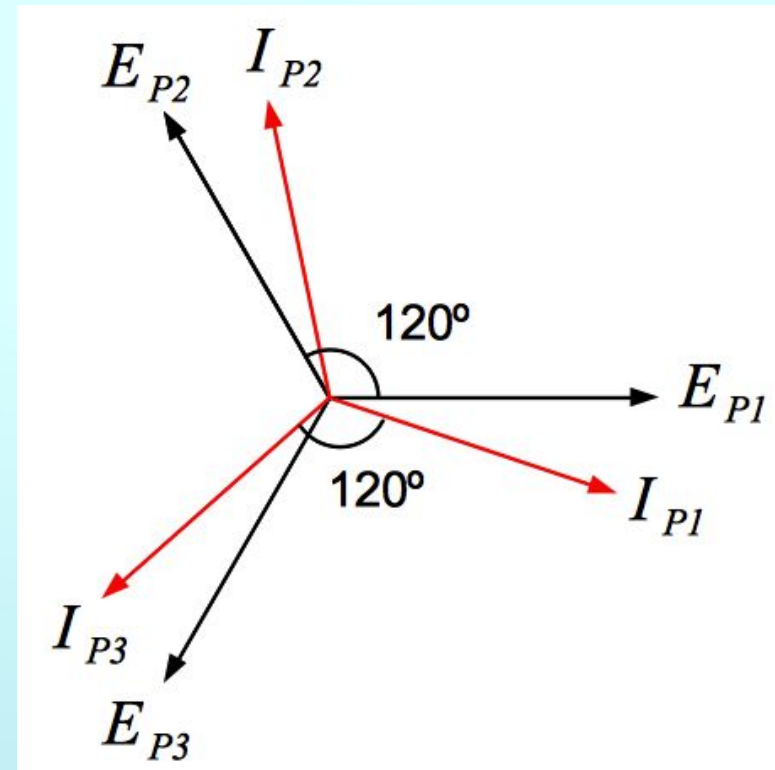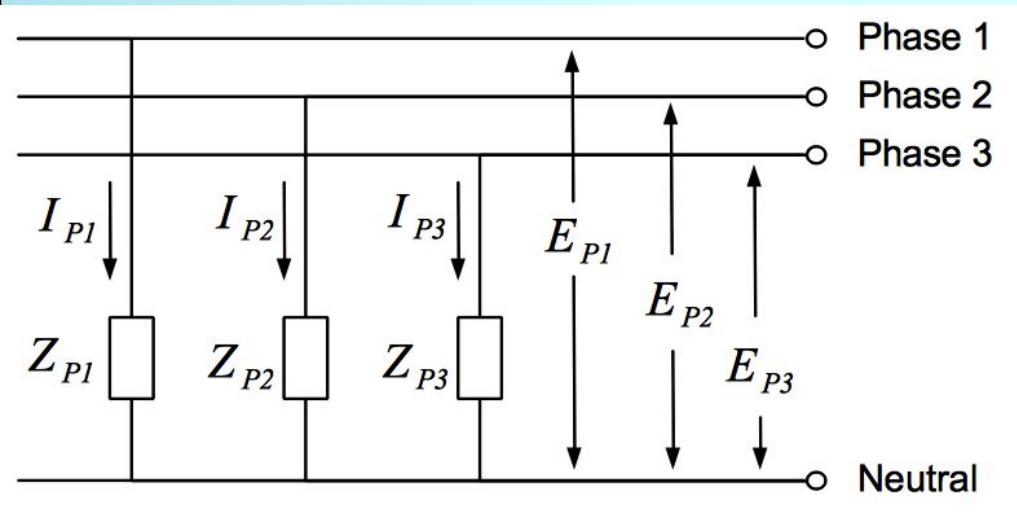

Balanced Loads

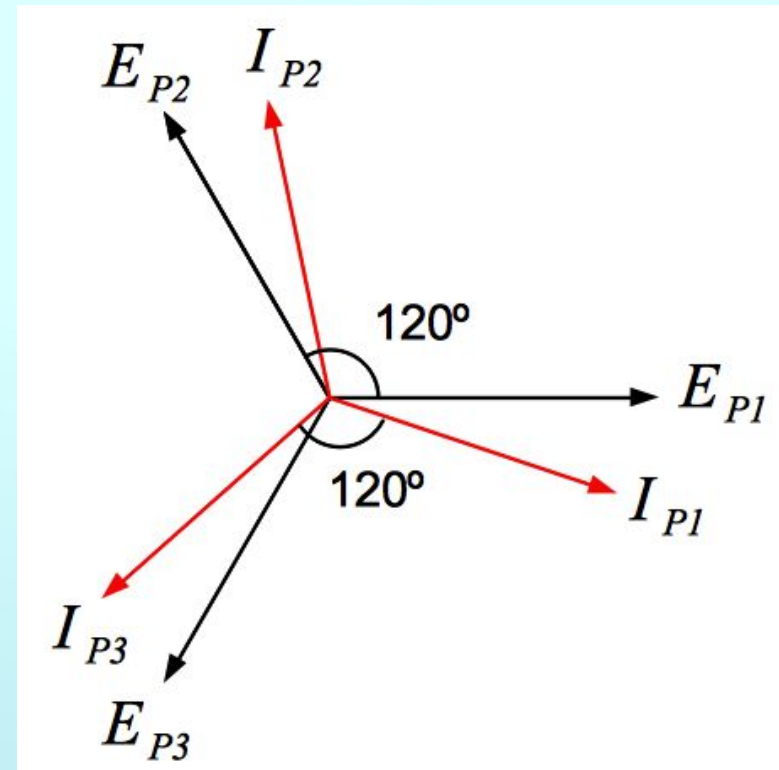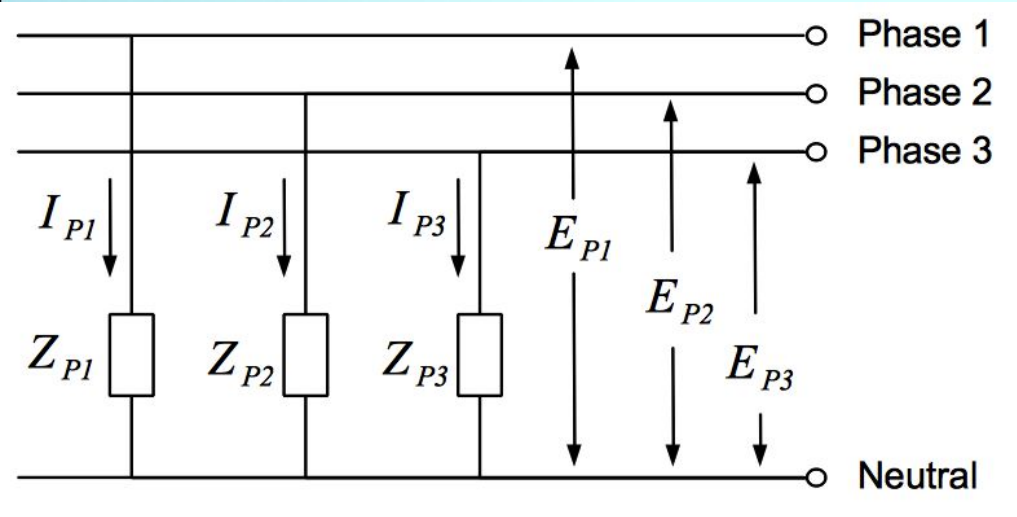- Balanced generation with balanced load:
 - Combined phase currents sum to zero.



Perfect balance \rightarrow no neutral current \rightarrow decreased copper

Balanced Loads

- Three-phase motors
 - Windings pretty well equivalent (if non-damaged)
 - Usually well balanced
- Power system distribution
 - Each house only has single-phase distribution
 - But on average (lots of houses), reasonably balanced
- Why balance loads?
 - More efficient
 - Cost effective
 - Better on equipment

And makes analysis
a whole lot easier!

We will only
consider balanced
systems


Three-Phase Configurations

- Wye-Configuration (Star-Configuration)
 - 4-wire distribution
 - Neutral used for any return current due to imbalance

Phase/line relationships


$$E_L = \sqrt{3} E_P$$

$$I_L = I_P$$

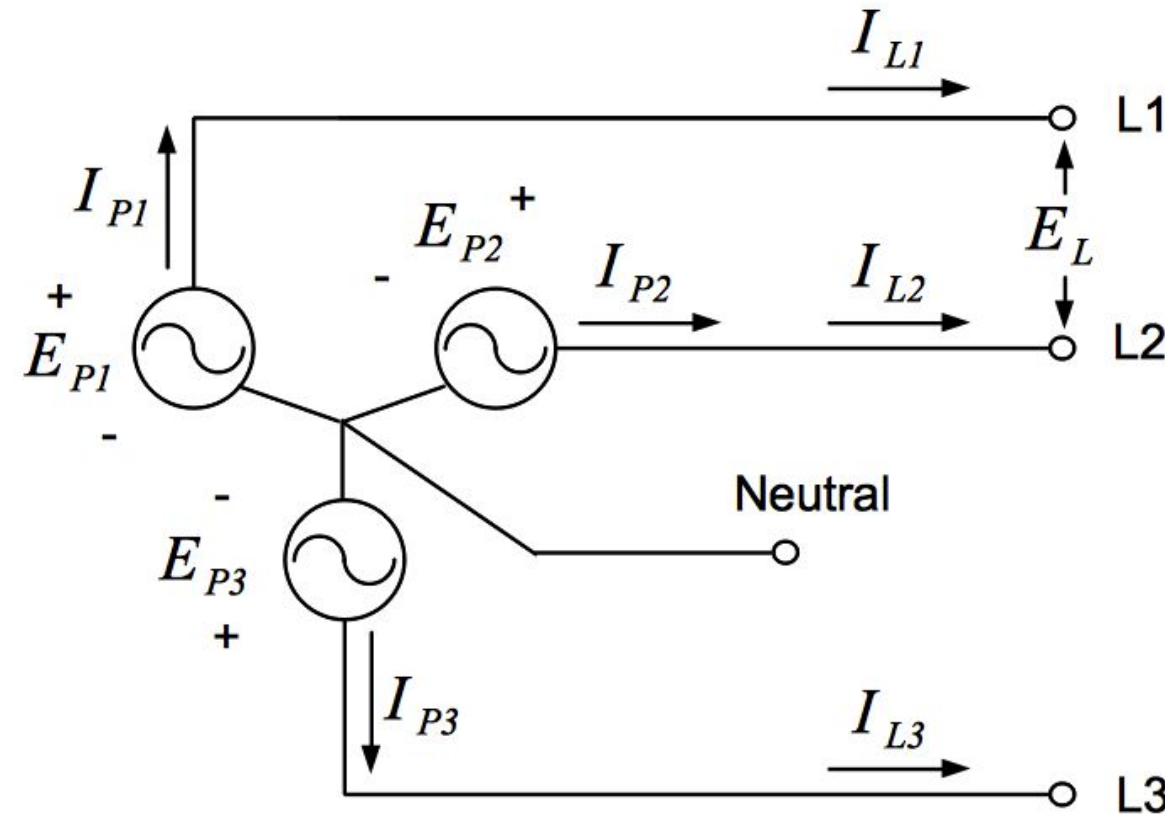

Three-Phase Configurations

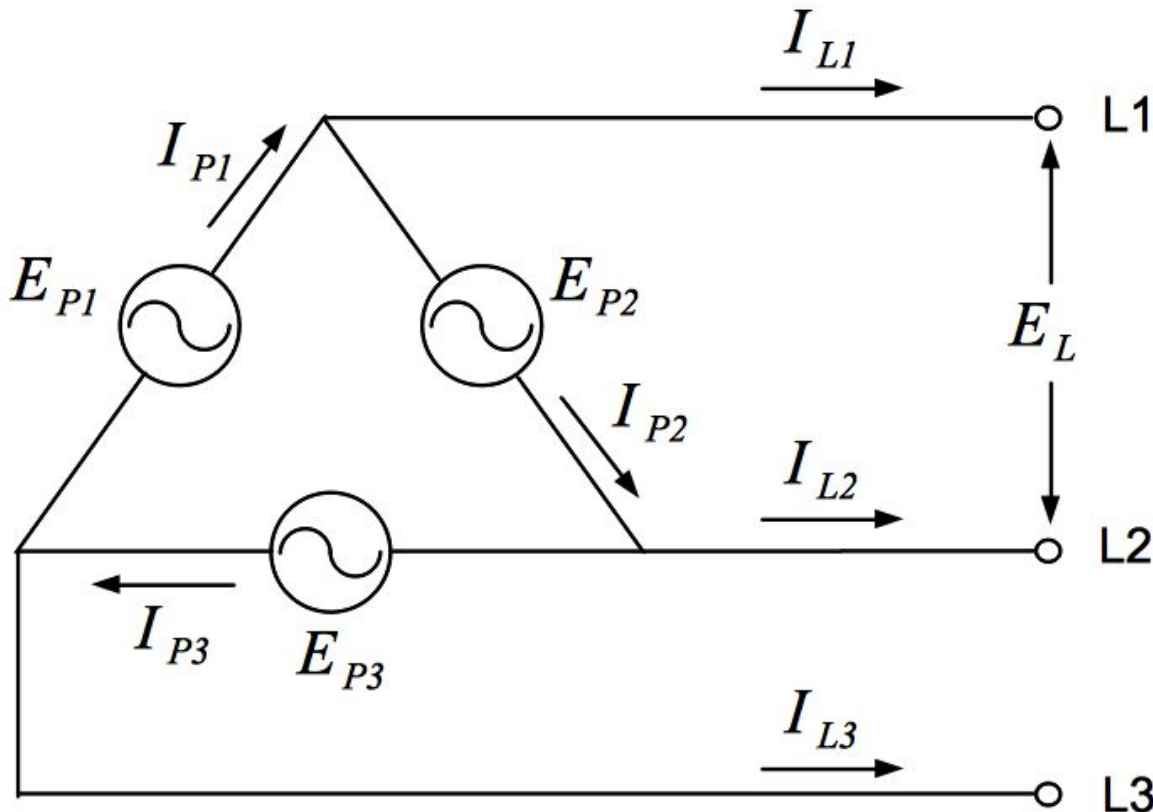- Delta-Configuration
 - 3-wire distribution
 - No neutral (any required current return due to imbalance distributed on other legs)




Phase/line relationships

$$E_L = E_P$$


$$I_L = \sqrt{3} I_P$$

Three-Phase Transformers


delta-delta

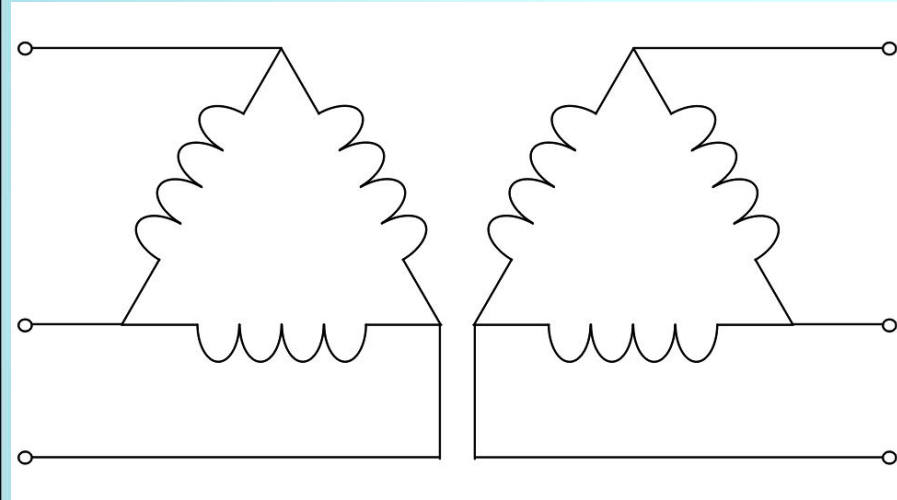


delta-wye

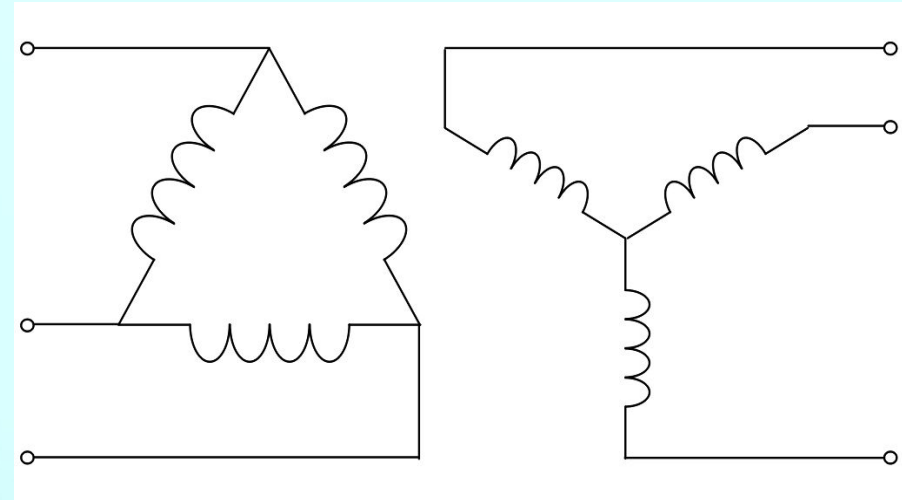

wye-delta

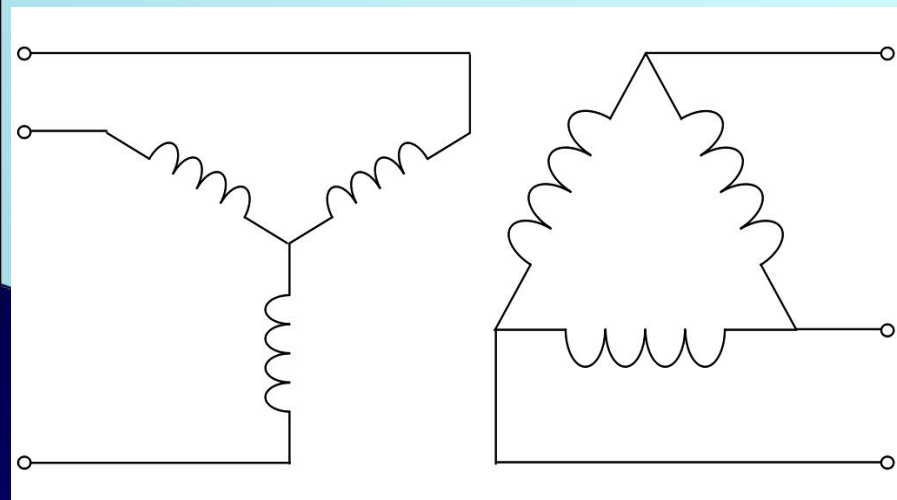

wye-wye

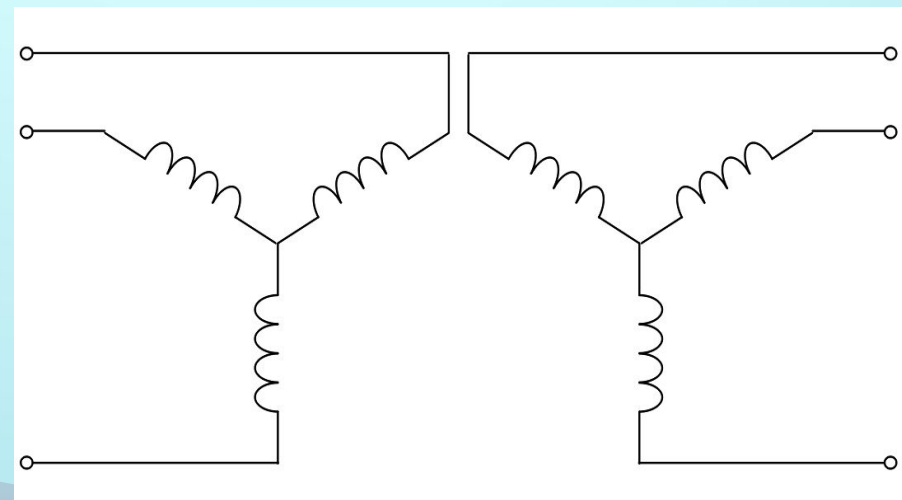


Three-Phase Circuits

- If balanced, can do analysis as single-phase.
 - Use phase variables (voltage, current, impedance, etc)
 - Need to find line variables for some circuits
 - Can easily calculate total three-phase power.
- Can also include transformers
 - For this class we will not consider 3-phase transformers
 - See Ch. 12 if interested.


Three-Phase Circuits

- Can have wye or delta out of transformer secondary
- Can have wye or delta load


wye secondary – wye load

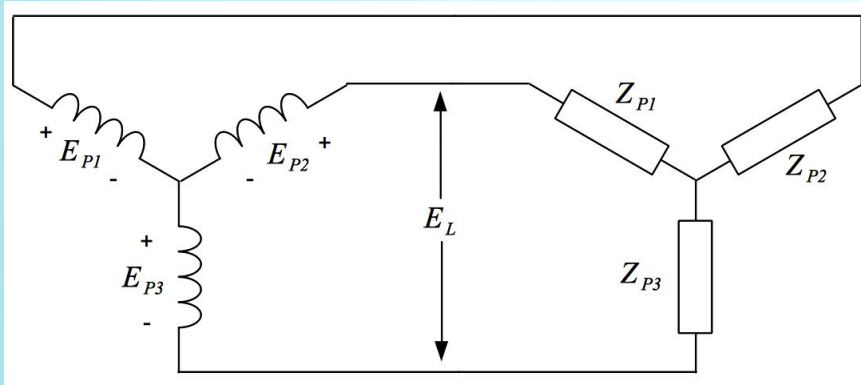


delta secondary – wye load

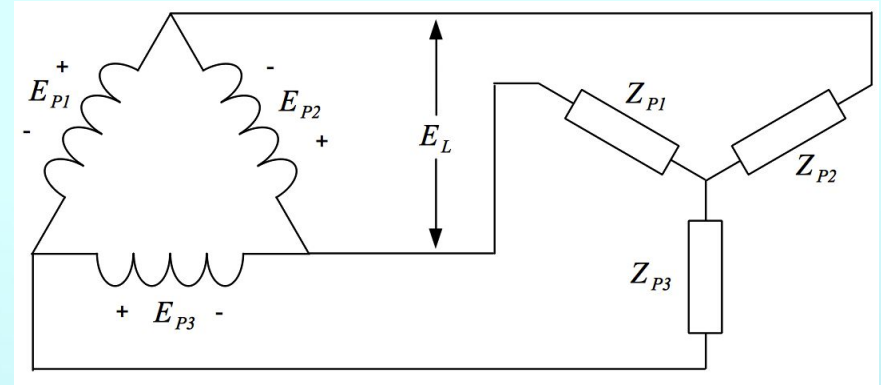

wye secondary – delta load

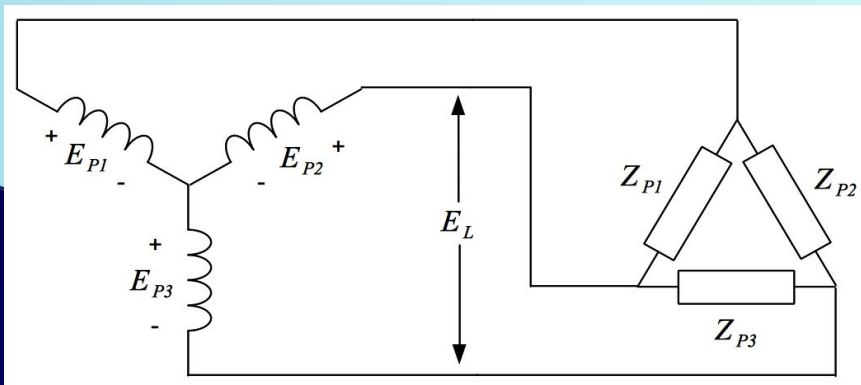

delta secondary – delta load

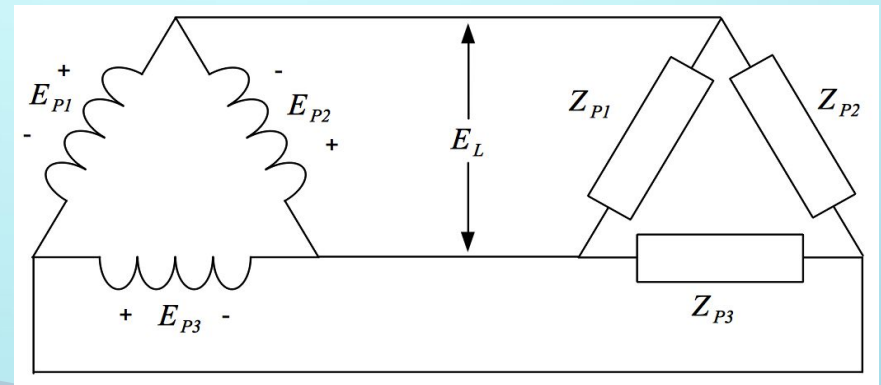

Three-Phase Circuits

- What to calculate?
 - Transformer secondary phase voltage, $E_{S,P}$
 - Transformer secondary line voltage, $E_{S,L}$
 - Transformer secondary phase current, $I_{S,P}$
 - Transformer secondary line current, $I_{S,L}$
 - Load phase voltage, $E_{L,P}$
 - Load line voltage, $E_{L,L}$
 - Load phase current, $I_{L,P}$
 - Load line current, $I_{L,L}$
 - Circuit real, reactive, apparent power, P Q S
 - Circuit power factor, PF

Three-Phase Circuits

- Relevant Equations (we'll consider magnitude only):
 - Ohm's Law: $E_P = I_P Z_P$
 - Real Power: $P = 3 E_P I_P PF$ $P = \sqrt{3} E_L I_L PF$
 - Apparent Power: $S = \sqrt{P^2 + Q^2}$ $S = 3 E_P I_P$ $S = \sqrt{3} E_L I_L$
 - Reactive Power: $Q = \sqrt{S^2 - P^2}$
 - Power Factor: $PF = \frac{P}{S}$

Example: Wye-Wye Circuit

A wye-connected three-phase transformer supplies power to a wye-connected resistive load. The transformer secondary has a phase voltage of 277 V and the resistors of the load have a resistance of 8 Ω .

Step 1: Determine transformer phase voltage and line voltage:

Step 2: Determine load phase voltage and line voltage:

Step 3: Calculate load phase and line current:

Step 4: Determine transformer secondary phase and line current:

Example: Wye-Wye Circuit

A wye-connected three-phase transformer supplies power to a wye-connected resistive load. The transformer secondary has a phase voltage of 277 V and the resistors of the load have a resistance of 8 Ω .

Step 1: Determine transformer phase voltage and line voltage:

$$E_{S,P} = 277\text{V} \qquad E_{S,L} = \sqrt{3} E_{S,P} = 480\text{V}$$

Step 2: Determine load phase voltage and line voltage:

Step 3: Calculate load phase and line current:

Step 4: Determine transformer secondary phase and line current:

Example: Wye-Wye Circuit

A wye-connected three-phase transformer supplies power to a wye-connected resistive load. The transformer secondary has a phase voltage of 277 V and the resistors of the load have a resistance of 8 Ω .

Step 1: Determine transformer phase voltage and line voltage:

$$E_{S,P} = 277\text{V} \quad E_{S,L} = \sqrt{3} E_{S,P} = 480\text{V}$$

Step 2: Determine load phase voltage and line voltage:

$$E_{L,L} = E_{S,L} = 480\text{V} \quad E_{L,P} = \frac{1}{\sqrt{3}} E_{S,L} = 277\text{V}$$

Step 3: Calculate load phase and line current:

Step 4: Determine transformer secondary phase and line current:

Example: Wye-Wye Circuit

A wye-connected three-phase transformer supplies power to a wye-connected resistive load. The transformer secondary has a phase voltage of 277 V and the resistors of the load have a resistance of 8 Ω .

Step 1: Determine transformer phase voltage and line voltage:

$$E_{S,P} = 277\text{V} \quad E_{S,L} = \sqrt{3} E_{S,P} = 480\text{V}$$

Step 2: Determine load phase voltage and line voltage:

$$E_{L,L} = E_{S,L} = 480\text{V} \quad E_{L,P} = \frac{1}{\sqrt{3}} E_{S,L} = 277\text{V}$$

Step 3: Calculate load phase and line current:

$$I_{L,P} = E_{L,P} / Z_{L,P} = 34.6\text{A} \quad I_{L,L} = I_{L,P} = 34.6\text{A}$$

Step 4: Determine transformer secondary phase and line current:

Example: Wye-Wye Circuit

A wye-connected three-phase transformer supplies power to a wye-connected resistive load. The transformer secondary has a phase voltage of 277 V and the resistors of the load have a resistance of 8 Ω .

Step 1: Determine transformer phase voltage and line voltage:

$$E_{S,P} = 277\text{V} \qquad E_{S,L} = \sqrt{3} E_{S,P} = 480\text{V}$$

Step 2: Determine load phase voltage and line voltage:

$$E_{L,L} = E_{S,L} = 480\text{V} \qquad E_{L,P} = \frac{1}{\sqrt{3}} E_{S,L} = 277\text{V}$$

Step 3: Calculate load phase and line current:

$$I_{L,P} = E_{L,P} / Z_{L,P} = 34.6\text{A} \qquad I_{L,L} = I_{L,P} = 34.6\text{A}$$

Step 4: Determine transformer secondary phase and line current:

$$I_{S,L} = I_{L,L} = 34.6\text{A} \qquad I_{S,P} = I_{S,L} = 34.6\text{A}$$

Example: Wye-Wye Circuit

For previous circuit example, determine real, reactive, and apparent power:

Example: Wye-Wye Circuit

For previous circuit example, determine real, reactive, and apparent power:


$$PF = 1$$

$$P = 3 E_{L,P} I_{L,P} PF = 3 * 277V * 34.6A = 28.8kW$$

$$S = P = 28.8kVA$$

$$Q = 0kVAR$$

Resistive circuit so no reactive power!

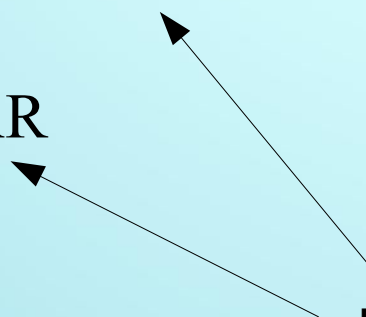

Example: Wye-Delta Circuit

A wye-connected three-phase transformer supplies power to a delta-connected induction motor. The transformer secondary has a phase voltage of 277 V and motor windings have a total impedance of 8Ω . The motor operates with a power factor of 0.8.

Step 1: Determine transformer phase voltage and line voltage:

Step 2: Determine load phase voltage and line voltage:

Step 3: Calculate load phase and line current:

Step 4: Determine transformer secondary phase and line current:

Example: Wye-Delta Circuit

A wye-connected three-phase transformer supplies power to a delta-connected induction motor. The transformer secondary has a phase voltage of 277 V and motor windings have a total impedance of 8 Ω . The motor operates with a power factor of 0.8.

Step 1: Determine transformer phase voltage and line voltage:

$$E_{S,P} = 277 V \qquad E_{S,L} = \sqrt{3} E_{S,P} = 480 V$$

Step 2: Determine load phase voltage and line voltage:

Step 3: Calculate load phase and line current:

Step 4: Determine transformer secondary phase and line current:

Example: Wye-Delta Circuit

A wye-connected three-phase transformer supplies power to a delta-connected induction motor. The transformer secondary has a phase voltage of 277 V and motor windings have a total impedance of 8 Ω . The motor operates with a power factor of 0.8.

Step 1: Determine transformer phase voltage and line voltage:

$$E_{S,P} = 277 V \quad E_{S,L} = \sqrt{3} E_{S,P} = 480 V$$

Step 2: Determine load phase voltage and line voltage:

$$E_{L,L} = E_{S,L} = 480 V \quad E_{L,P} = E_{S,L} = 480 V$$

Step 3: Calculate load phase and line current:

Step 4: Determine transformer secondary phase and line current:

Example: Wye-Delta Circuit

A wye-connected three-phase transformer supplies power to a delta-connected induction motor. The transformer secondary has a phase voltage of 277 V and motor windings have a total impedance of 8 Ω . The motor operates with a power factor of 0.8.

Step 1: Determine transformer phase voltage and line voltage:

$$E_{S,P} = 277 V \quad E_{S,L} = \sqrt{3} E_{S,P} = 480 V$$

Step 2: Determine load phase voltage and line voltage:

$$E_{L,L} = E_{S,L} = 480 V \quad E_{L,P} = E_{S,L} = 480 V$$

Step 3: Calculate load phase and line current:

$$I_{L,P} = E_{L,P} / Z_{L,P} = 60 A \quad I_{L,L} = \sqrt{3} I_{L,P} = 104 A$$

Step 4: Determine transformer secondary phase and line current:

Example: Wye-Delta Circuit

A wye-connected three-phase transformer supplies power to a delta-connected induction motor. The transformer secondary has a phase voltage of 277 V and motor windings have a total impedance of 8 Ω . The motor operates with a power factor of 0.8.

Step 1: Determine transformer phase voltage and line voltage:

$$E_{S,P} = 277 V \quad E_{S,L} = \sqrt{3} E_{S,P} = 480 V$$

Step 2: Determine load phase voltage and line voltage:

$$E_{L,L} = E_{S,L} = 480 V \quad E_{L,P} = E_{S,L} = 480 V$$

Step 3: Calculate load phase and line current:

$$I_{L,P} = E_{L,P} / Z_{L,P} = 60 A \quad I_{L,L} = \sqrt{3} I_{L,P} = 104 A$$

Step 4: Determine transformer secondary phase and line current:

$$I_{S,L} = I_{L,L} = 104 A \quad I_{S,P} = I_{S,L} = 104 A$$

Example: Wye-Wye Circuit

For previous circuit example, determine real, reactive, and apparent power:

Example: Wye-Wye Circuit

For previous circuit example, determine real, reactive, and apparent power:

$$PF = 0.8$$

$$P = 3 E_{L,P} I_{L,P} PF = 3 * 480V * 60A * 0.8 = 69.1kW$$

$$S = \frac{P}{PF} = \frac{69,100}{0.8} = 86.4kVA$$

$$Q = \sqrt{S^2 - P^2} = 51.8kVAR$$

Upcoming in class

- More 3-phase circuits
 - Delta and Wye connections
- Electrical Distribution
- CHANGE TO SYLLABUS
 - There IS lab next week
 - We will do project later (probably week before Thanksgiving)