

EELE 354: Electric Power Applications

Lecture 6: Resistive Electrical Circuits Practice

09/16/2013

1. For the circuit shown in Figure 1, assume voltage and resistance values of $V_{in} = 120$ V, $R_1 = 100 \Omega$, $R_2 = 50 \Omega$, and $R_3 = 25 \Omega$.

- What is the equivalent resistance in the circuit from the perspective of the power source?
- What is the total current, I , drawn from the power source?
- What is the total power demand of the power source?
- What is the voltage drop across each resistor?

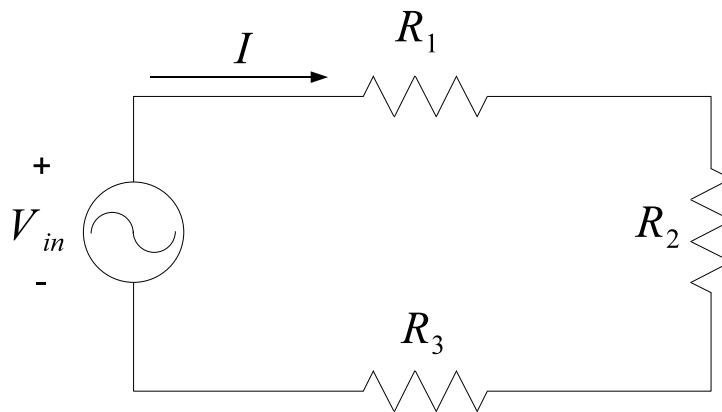


Figure 1: Practice Circuit 1

2. For the circuit shown in Figure 2, assume voltage and resistance values of $V_{in} = 120$ V, $R_1 = 100 \Omega$, $R_2 = 50 \Omega$, and $R_3 = 25 \Omega$.

- What is the equivalent resistance in the circuit from the perspective of the power source?
- What is the total current, I , drawn from the power source?
- What is the current draw through each resistor?

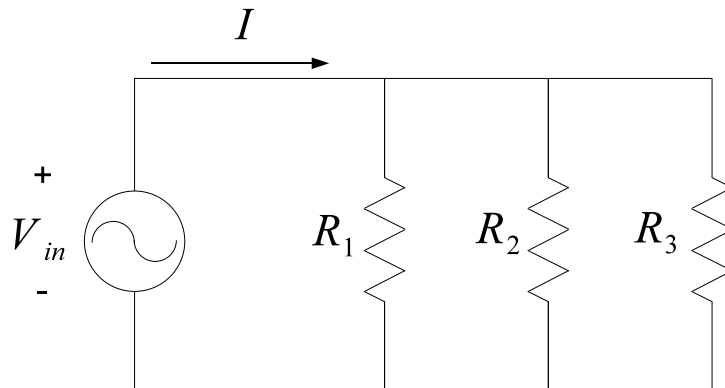


Figure 2: Practice Circuit 2

3. For the circuit shown in Figure 3, assume voltage and resistance values of $V_{in} = 120$ V, $R_1 = 100 \Omega$, $R_2 = 50 \Omega$, and $R_3 = 25 \Omega$.

- What is the equivalent resistance in the circuit from the perspective of the power source?
- What is the total current, I , drawn from the power source?
- What is the current through R_2 , the voltage drop across R_2 and the power dissipated in R_2 ?

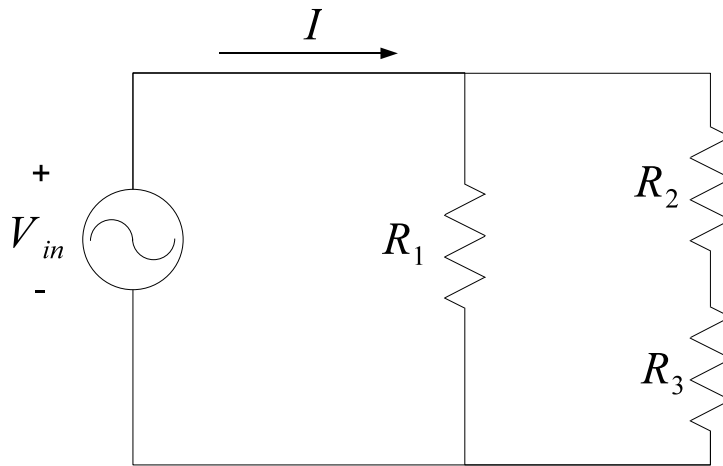


Figure 3: Practice Circuit 3

4. For the circuit shown in Figure 4, assume voltage and resistance values of $V_{in} = 120$ V, $R_1 = 100 \Omega$, $R_2 = 50 \Omega$, and $R_3 = 25 \Omega$.

- What is the equivalent resistance in the circuit from the perspective of the power source?
- What is the total current, I , drawn from the power source?
- What is the current through R_2 , the voltage drop across R_2 and the power dissipated in R_2 ?

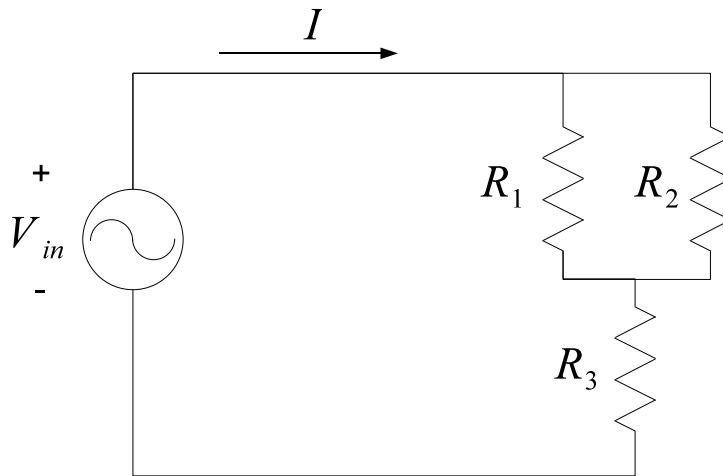


Figure 4: Practice Circuit 4

5. **Application Problem 1: The Dimmer Switch** A dimmer switch for a lighting circuit can be implemented using a variable resistor (aka rheostat). In the circuit of Figure 5, let resistors R_1 through R_4 represent lightbulbs rated for 100 Watts when powered by a 120 V source. For a resistor based dimmer switch to operate well, it's minimum resistance must be much lower than that of the load, and it's maximum resistance must be much higher than that of the load. For this analysis, assume that the variable resistor has a minimum resistance of 0Ω , i.e. it is a perfect short circuit, and a maximum resistance of $\infty \Omega$, i.e. it is a perfect open circuit.

- What is the resistance of each lightbulb (assume the bulbs have been on for a long time and are at a steady temperature)?
- Assuming the dimmer switch is fully on, i.e. perfect short, what is the equivalent resistance in the circuit from the perspective of the power source?
- What is the voltage applied to each lightbulb when the dimmer is adjusted to have a resistance of 36Ω ?
- The dimmer switch dissipates maximum power when it's resistance is equal to the equivalent resistance of the four parallel bulbs. What must the power rating of the dimmer switch be? (Hint: it is not just 4 times 100 W)?

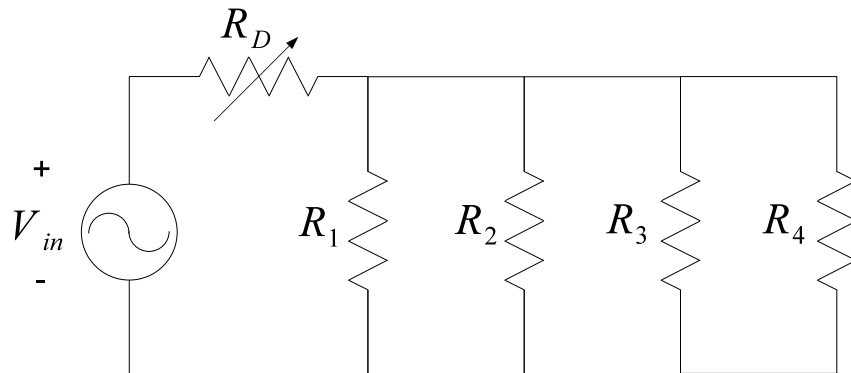


Figure 5: The Dimmer Switch

6. **Application Problem 2: The Wheatstone Bridge** The Wheatstone Bridge is a commonly used electrical circuit for measuring changes in resistance. The circuit, or a variation thereof, is often used with strain gauges. As the gauge deforms due to stress on the measured material/device, e.g. a steel I-beam, the gauge resistance changes. In the circuit below, R_1 through R_3 are standard resistors, while R_g , represents the resistance of the strain gauge.

- Analyze the circuit below to show that the output voltage, V_{out} , is given by,

$$V_{out} = \left(\frac{R_3}{R_g + R_3} - \frac{R_2}{R_1 + R_2} \right) V_{in}$$

- If R_1 , R_2 , R_3 and the **unstrained** gauge resistance, R_g all have the same resistance, R , show that the output voltage $V_{out} = 0$ V regardless of the input voltage, V_{in} .
- If while under stress, the strain gauge resistance increases to $R_g = 3R$, what is V_{out} ?
- Hints: Can always redraw circuit so branches and resistances are vertical. Find the current through each branch first. Then find voltages across R_2 and R_3 .

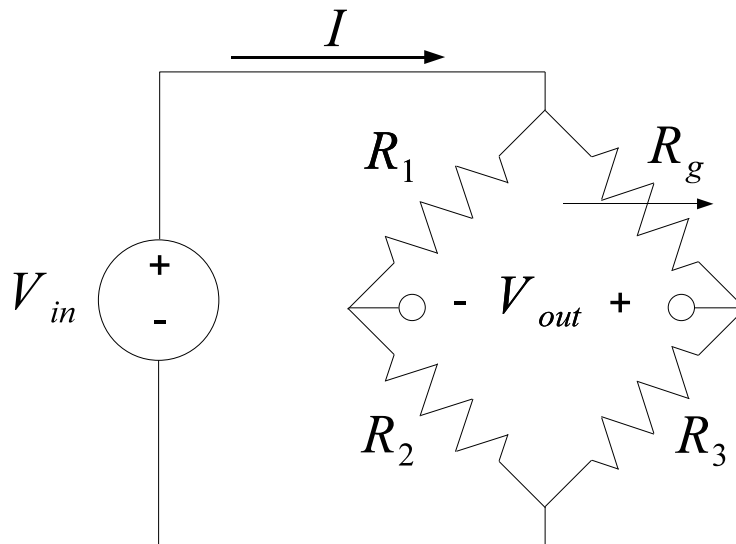


Figure 6: Wheatstone Bridge Circuit