

Problem 1:

$$\begin{aligned}\rightarrow R_{eq} &= R_1 + R_2 + R_3 \\ &= 100 + 50 + 25\end{aligned}$$

$$R_{eq} = 175 \Omega$$

$$\rightarrow I = \frac{V_{in}}{R_{eq}} = \frac{120V}{175 \Omega} = 0.69A$$

$$\rightarrow P = V_{in} \cdot I = 120V \cdot 0.69A = 82.3W$$

$$\rightarrow V_1 = I R_1 = 0.69A \cdot 100 \Omega = 69V$$

$$V_2 = I R_2 = 0.69A \cdot 50 \Omega = 34.5V$$

$$V_3 = I R_3 = 0.69A \cdot 25 \Omega = 17.2V$$

BTW, check KVL $\Rightarrow V_1 + V_2 + V_3 = V_{in} ?$

$$69 + 34.5 + 17.2 = 120.7 \approx \text{error due to rounding}$$

Problem 2:

$$\rightarrow R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \frac{1}{\frac{7}{100}} = \boxed{14.3 \Omega}$$

$$\rightarrow I = \frac{V_{in}}{R_{eq}} = \boxed{8.4 A}$$

$$\rightarrow I_1 = \frac{V_{in}}{R_1} = \boxed{1.2 A}$$

$$I_2 = \frac{V_{in}}{R_2} = \boxed{2.4 A}$$

$$I_3 = \frac{V_{in}}{R_3} = \boxed{4.8 A}$$

Check KCL $\Rightarrow I_1 + I_2 + I_3 = I$

$$\underline{1.2 + 2.4 + 4.8 = 8.4}$$

Problem 3:

$$\rightarrow R_{eq} = R_1 \parallel (R_2 + R_3) = 100 \Omega \parallel (75 \Omega)$$

$$R_{eq} = \frac{1}{\frac{1}{100} + \frac{1}{75}} = \boxed{42.9 \Omega}$$

$$\rightarrow I = \frac{V_{in}}{R_{eq}} = \boxed{2.8 \text{ A}}$$

$$\rightarrow I_2 = \frac{V_{in}}{(R_2 + R_3)} = \frac{120 \text{ V}}{75 \Omega} = \boxed{1.6 \text{ A}}$$

$$V_2 = I_2 R_2 = 1.6 \text{ A} \cdot \overset{50}{\cancel{75}} \Omega = \boxed{80 \text{ V}}$$

$$P_2 = I_2 V_2 = 1.6 \text{ A} \cdot 80 \text{ V} = \boxed{128 \text{ W}}$$

BTW, KVL holds because voltage across $R_3 = 40 \text{ V}$
(check if you want) and $V_2 + V_3 = V_{in}$
 $\underline{40 + 80 = 120}$

KCL holds because current through R_1 is 1.2 A
(again check if you want)

$$\text{and } I_1 + I_2 = I$$
$$1.2 \text{ A} + 1.6 \text{ A} = \boxed{2.8 \text{ A}}$$

Problem 4:

$$\rightarrow R_{eq} = R_1 // R_2 + R_3 = \frac{1}{\frac{1}{100} + \frac{1}{50}} + 25$$
$$= \frac{100}{3} + 25 = \boxed{58.3 \Omega}$$

$$\rightarrow I = \frac{V_{in}}{R_{eq}} = \frac{120V}{58.3 \Omega} = \boxed{2.06A}$$

→ First find voltage across R_2 .

Use KVL,

$$V_{in} = V_2 + V_3 \Rightarrow V_2 = V_{in} - V_3$$

~~Because~~ From KCL:

$$I = I_1 + I_2 \quad \text{Also } I_3 = I_1 + I_2$$

$$\text{so } I_3 = I!$$

Then,

$$V_3 = I R_3 = 51.4V$$

$$\text{then } V_2 = 120V - 51.4V = \boxed{68.6V}$$

$$I_2 = \frac{V_2}{R_2} = \frac{68.6V}{50 \Omega} = \boxed{1.37A}$$

$$P_2 = I_2 \cdot V_2 = \boxed{94W}$$