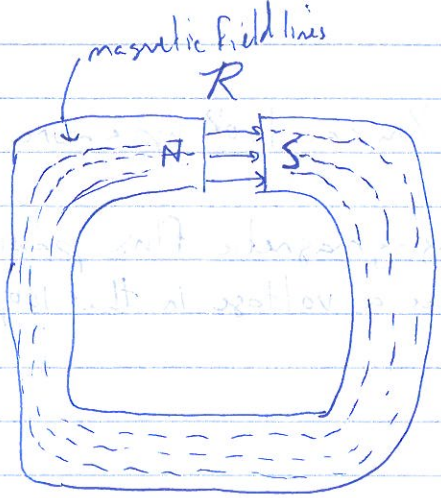


Alternating Current

Correction (kinda) From last lecture:




Φ => magnetic flux SI unit Weber

\mathcal{F} => mmf magnetomotive force (SI unit Ampere)
↳ used to be ampere-turn


R => reluctance

~~$\mathcal{F} = \Phi R$~~

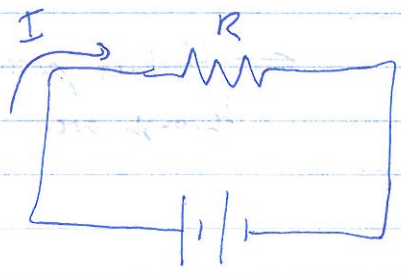

$E = IR$

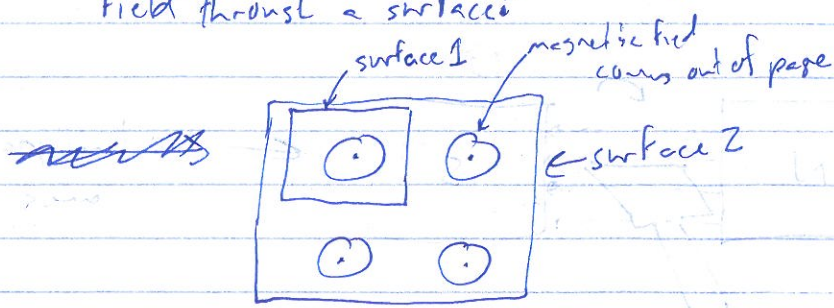Φ => magnetic flux is the component of a magnetic field through a surface



larger area means greater magnetic flux as there are more magnetic field lines passing through it.

(2)


Why is this important?

It helps us understand how we generate alternating current.


Faraday's Law: * You can look up a more formal definition *

For us: A changing magnetic flux passing through a conductive loop induces a voltage in that loop.
(circuit)

Drawing:

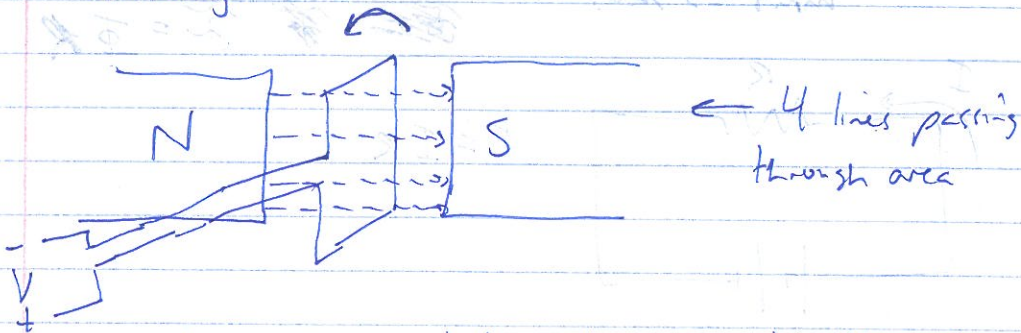


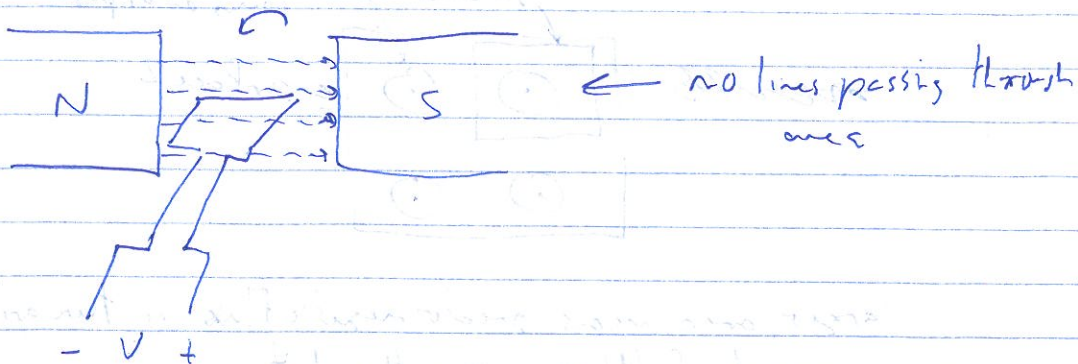As ~~the~~ loop rotates, the magnetic flux through it ~~&~~ changes because the ~~s~~ surface of the loop rotates so that the number of magnetic field lines through the loop changes.



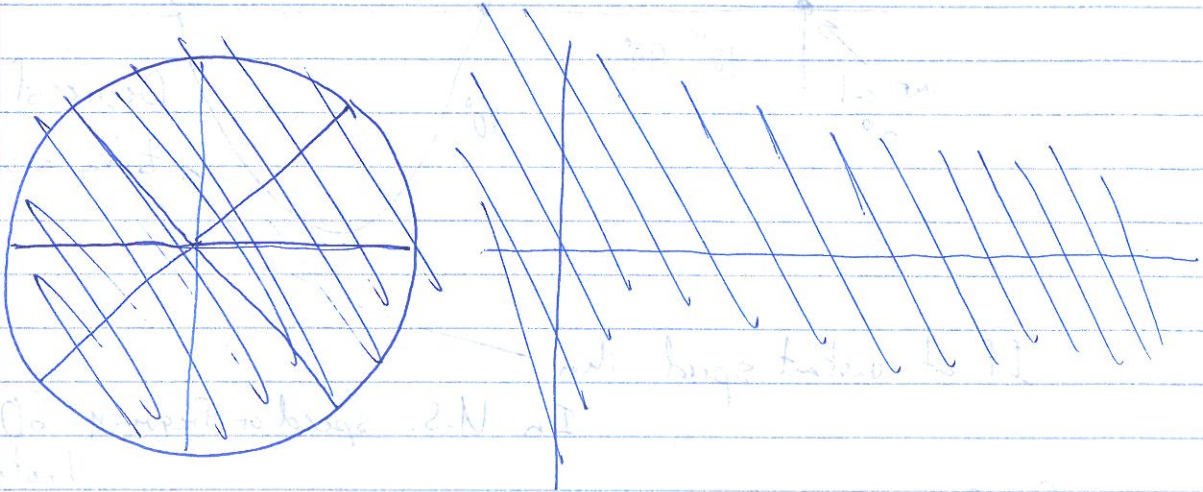
(3)

If this loop is turned at a constant ^{rotational} speed
then the induced voltage will have a sinusoidal
shape




~~Explanation~~ Induced voltage is proportional to change
in magnetic flux.

So

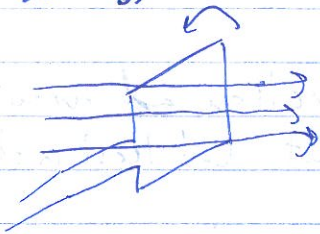

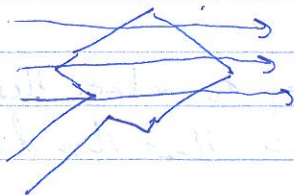← At this point change in magnetic flux
is small so small voltage




← $\Delta \Phi$ medium so medium voltage



$\Delta \Phi$ is large so large voltage

(4)

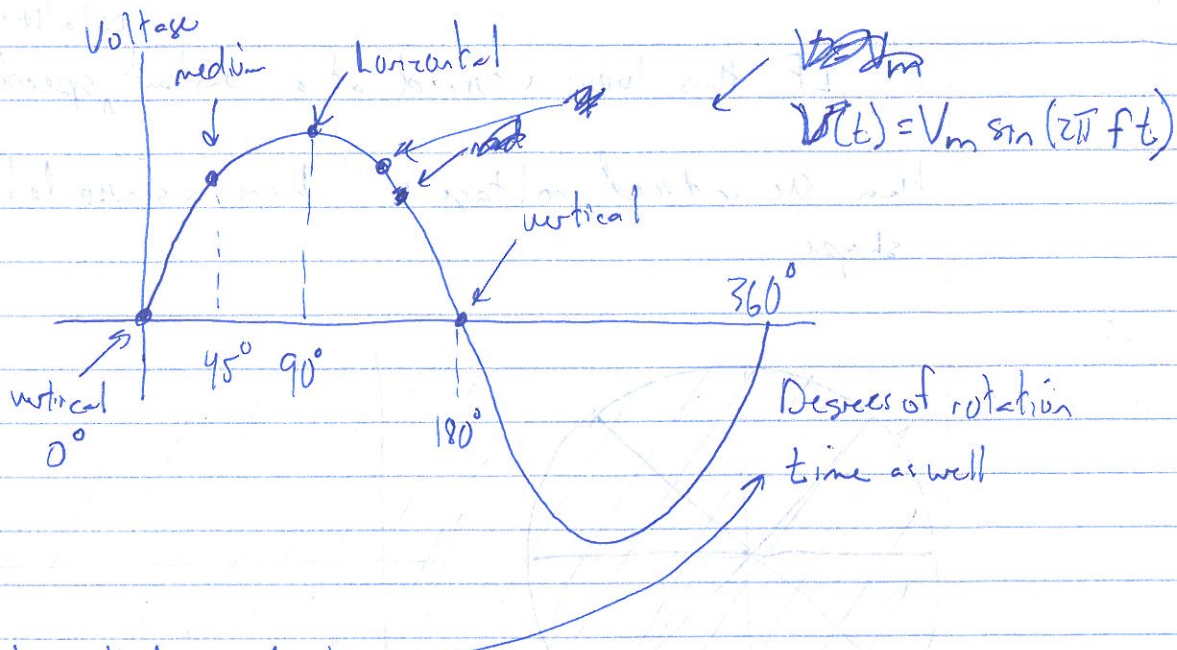

IF at constant speed then

In U.S. speed or frequency 60 Hz
1 rotation/second

~~Vector Diagrams~~

In mod of Europe → 50 Hz.

~~Instantaneous voltages and~~

Root-Mean squared or Effective current and voltage values

- When using DC → ~~current~~ voltage and current values constant (at least in steady-state)
- When using AC → voltage and current values constantly changing
- * We need a way to relate these two.
- * Can't use average value because that should be 0V or A.



RMS gives an effective value for alternating current and ~~that~~ that will produce the same heating effect as a specific value of a steady DC-current.

i.e. 1A ac produces same heating rate of a resistor as 1A dc.

That is multiply the ~~maximum~~ ~~voltage~~ or current by $\frac{1}{\sqrt{2}}$ or 0.707 ~~$V_{ac} = 0.707 I_m$~~
 ~~$V_{rms} =$~~

~~Same for voltage~~

So if current is given by ~~$i(t) = I_m \sin(2\pi f t)$~~ $i(t) = I_m \sin(2\pi f t)$

then $I_{ac} = 0.707 I_m$
 $I_{rms} =$

Same with voltage: $v(t) = V_m \sin(2\pi f t)$

$V_{ac} = 0.707 V_m$
 $V_{rms} =$

BTW definition of RMS \Rightarrow ~~V_{RMS}~~

For ~~smooth~~ periodic function

$V_{RMS} = \frac{1}{T} \int_0^T v(t)^2 dt$
 \uparrow
period $\frac{1}{T}$

So when we say 120V we mean $V_{RMS} = 120V$


Actual magnitude is $\approx 170V$.

More on Electromagnetic Induction

→ Process by which a voltage is produced across a conductor or coil as result of changing magnetic field.

~~Process of Induction~~

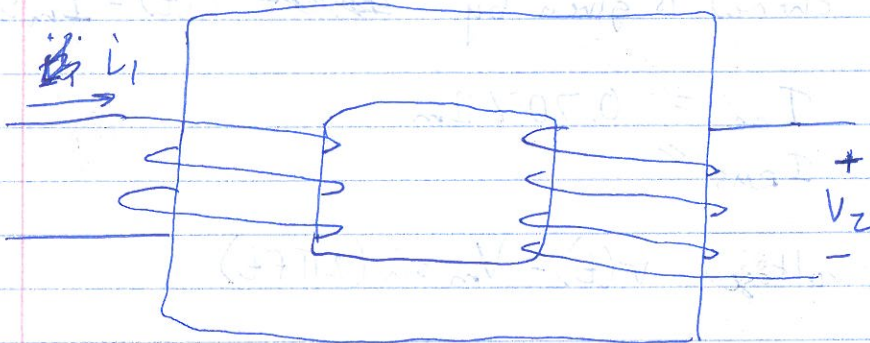- Causes mutual inductance → How transformers work
~~with~~





i_1
induces V_2

Also causes self-inductance. → ~~Change in current~~

→ A change in current in a circuit causes a change in the magnetic field. This causes an induced voltage in the circuit opposed to the applied voltage.

→ Tends to retard changes in circuit current.

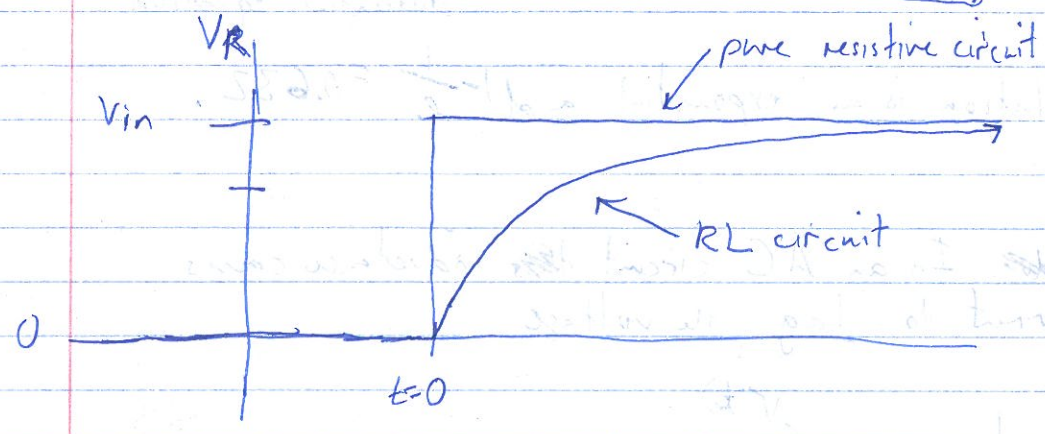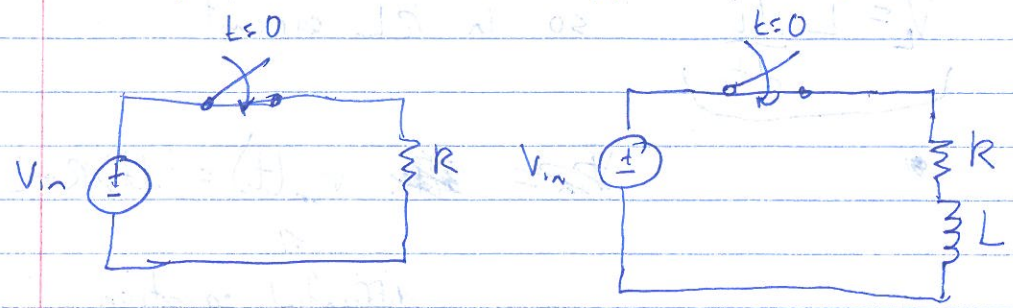In DC circuits, this causes slow response to step changes in ~~current~~ applied voltage.



~~Time constant~~ Inductance ~~Inductor~~ unit (H) Henrys

time constant \Rightarrow measure of ~~how quickly~~ ^{time it takes for} current to reach its maximum value

BUT: it's an exponential relationship so current NEVER ~~actually~~ reaches steady-state value. truly

$$\tau = \frac{R}{L} \text{ units of seconds}$$

\Rightarrow time it takes for current to reach 63.2% of maximum

Why 63.2%? ~~Exponential relationship~~

8

Voltage/current relationship of inductor:


$$V_L = L \frac{di}{dt} \quad \text{so in RL circuit}$$

$$v_{in}(t) = i(t)R + L \frac{di}{dt}$$

differential equation

solution is an exponential and $1 - \frac{1}{e} = 0.632$.

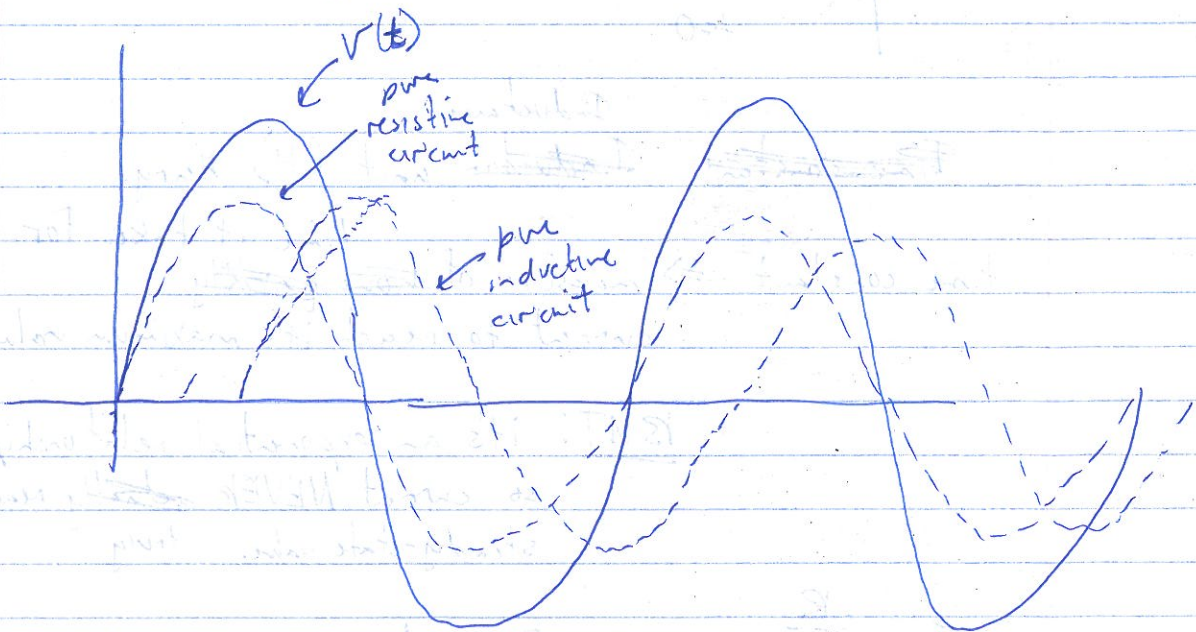In an AC circuit ~~this~~ inductance causes current to lag the voltage



9

Inductive Reactance → opposition to flow of alternating current.

- same unit of measurement as resistance
- but doesn't add simply
- frequency dependent

$$X_L = 2\pi fL$$

~~2 for power supply in the system~~

Total impedance of RL circuit

usually expressed as:

$$Z = \cancel{R + jX_L} R + jX_L$$

→ imaginary symbol don't use i because that's current.

For now know that $|Z| = \sqrt{R^2 + X_L^2}$

↑
magnitude

We are ignoring phase term for now. just know it lags

For AC circuits, Z replaces R in Ohm's Law:

$$V = IZ.$$

Inductor Reactance \rightarrow opposite in phase to capacitor
inductive reactance

resistor in transmission line \rightarrow energy is converted to heat
series like circuit \rightarrow
take it out \rightarrow

$$X_L = 2\pi fL$$

~~Inductive reactance~~

Total impedance of AC circuit

in AC circuit

$$Z = R + jX_L - jX_C$$

Impedance of AC circuit
series circuit

$$Z = R + j(X_L - X_C)$$

we are finding phase angle
of circuit

For AC circuit Z replace R in Ohm law

$$V = IZ$$