

EELE 414 – Introduction to VLSI Design

Module #5 – Inverters

- **Agenda**

1. Inverters

- Static Characteristics
- Switching Characteristics

- **Announcements**


1. Read Chapters 5, & 7



Inverters

- **Inverters**

 - an inverter is a basic gate that complements the input



- we study the invert in order to understand the Static and Dynamic performance


- once we do this, we can model more complex logic gates as "equivalent inverters" and use the same analysis.



Inverters

- **Inverters**

 
- The "Voltage Transfer Characteristics" (VTC) of an ideal inverter



Inverters

- **Inverters**


- Graphically, this looks like:

 

Inverters

- **Logic Levels**

 - We need to define boundaries when the signal is considered HIGH or LOW
- these are called the "Logic Levels"




- what is the logic level in the middle region? It is unknown...



Inverter Static Behavior

- **Static Behavior**

 - "Static" or "DC" refers to the gate's operation when the inputs are NOT changing
- also called "Steady State"
- if we plotted Vout vs. Vin of an Inverter, we would get...



Inverter Static Behavior

- Static Behavior**
 - the region in the middle is not definitely a HIGH or a LOW because of:
 - Power Supply Variation
 - Process
 - Noise

V_{out}

V_{in}

Uncertainty or Transition region

EEL414 – Introduction to VLSI DesignModule #5
Page 7

Inverter Static Behavior

- DC Specifications**
 - we need to be able to guarantee operation of the gate over all possible conditions
 - the limits on guaranteed operation are called "specifications"
 - Specifications can give limits on the worst case situations
 - Specifications can also give limits on typical situations

EEL414 – Introduction to VLSI DesignModule #5
Page 8

Inverter Static Behavior

- DC Specifications**
 - in a real inverter VTC, the output doesn't switch instantaneously
 - there are two critical points on the real VTC curve which occur when the slope of $V_{out}(V_{in}) = -1$
 - V_{IL} is the input low voltage which corresponds to an output high voltage with a slope of -1.
 - V_{IH} is the input high voltage which corresponds to an output low voltage with a slope of -1
 - other critical points are:
 - V_{OH} is the output voltage when the output level is logic "1"
 - V_{OL} is the output voltage when the output level is logic "0"
 - V_{th} is the point at which $V_{out} = V_{in}$

V_{out}

V_{in}

V_{OH}

V_{OL}

V_{IL}

V_{IH}

V_{th}

$V_{out} = V_{in}$

$\frac{dV_{out}}{dV_{in}} = -1$

$\frac{dV_{out}}{dV_{in}} = -1$

EEL414 – Introduction to VLSI DesignModule #5
Page 9

Inverter Static Behavior

- DC Input Specifications**
 - V_{IH} : Minimum input voltage guaranteed to be recognized as a HIGH (aka V_{ILmin})
 - V_{IL} : Maximum input voltage guaranteed to be recognized as a LOW (aka V_{IHmax})

V_{in}

HIGH

LOW

V_{DD}

V_{IH}

V_{IL}

V_{SS}

EEL414 – Introduction to VLSI DesignModule #5
Page 10

Inverter Static Behavior

- DC Output Specifications**
 - V_{OH} : Minimum output voltage guaranteed when driving a HIGH (aka V_{OHmin})
 - V_{OL} : Maximum output voltage guaranteed when driving a LOW (aka V_{OLmax})

V_{out}

HIGH

LOW

V_{DD}

V_{OH}

V_{OL}

V_{SS}

EEL414 – Introduction to VLSI DesignModule #5
Page 11

Inverter Static Behavior

- DC Noise Margins (NM)**
 - HIGH State Noise Margin : $(NM_H) = (V_{OH} - V_{IH}) = (V_{OHmin} - V_{IHmin})$
 - LOW State Noise Margin : $(NM_L) = (V_{IL} - V_{OL}) = (V_{ILmax} - V_{OLmax})$

V_{out}

V_{in}

HIGH

LOW

Noise Margin

Noise Margin

V_{DD}

V_{OH}

V_{OL}

V_{SS}

V_{IH}

V_{IL}

V_{SS}

EEL414 – Introduction to VLSI DesignModule #5
Page 12

Inverter Static Behavior

• DC Power Specifications

- the total DC power dissipated by an IC is given by:

$$P_{DC} = V_{DD} \cdot I_{DC}$$

- for a given gate, the current drawn will vary depending on the logic level

Driving a Logic HIGH: $I_{DC1}(V_{in} = low)$

Driving a Logic LOW: $I_{DC2}(V_{in} = high)$

- the gate will be in each one of these states 50% of the time

- if we assume the output voltage will swing from 0 to V_{DD} , we can estimate the average output voltage as $V_{DD}/2$

- a rough estimate of the DC power is: $P_{DC} = \frac{V_{DD}}{2} \cdot [I_{DC}(V_{in} = low) + I_{DC}(V_{in} = high)]$



Inverter Static Behavior

• Area

- as designers, we can adjust the sizes of L and W.

- we know that there is additional area required to fabricate the MOSFET

- active regions (surrounding FOX)
- channel Length (Y)
- substrate contacts

- but, as a practical measure, we talk about the area of a circuit as **W-L**

- while we know this isn't the full area that the device takes, it gives us a standard way to compare the sizes of different layouts.

- it is widely accepted that the area of a device is **W-L**



Inverter Design

• Inverter Implementations

- now we turn our attention to the circuit level implementation of the inverter

- there are many ways to create an inverter using MOSFETs

- 1) inverter with resistive-load
- 2) inverter with enhancement n-Type MOSFET load operating in the linear region
- 3) inverter with enhancement n-Type MOSFET load operating in the saturation region
- 4) inverter with depletion n-Type MOSFET load
- 5) CMOS inverter

- the most common type of inverter in VLSI is CMOS. This is due to the low static power consumption

- however, it is worth while to briefly look at other types of inverter implementations in case you use a fab that doesn't have PMOS

- for example, the Montana Microfabrication Facility (MMF)

- no N-Well & PMOS

- BUT, we can still design inverters using different circuit styles.



Resistive-Load Inverter

• Resistive-Load Inverter


- this circuit consists of an enhancement-type, N-Channel MOSFET as the driver

- a load resistor is connected between V_{DD} and the Drain (Vout) of the MOSFET

- the gates that this inverter drives are assumed to be of the same configuration so there is no DC load current looking into their gate terminals.

- $V_{out} = V_{DS}$

- $V_{in} = V_{gs}$

 


Resistive-Load Inverter

• Resistive-Load Inverter

- we need a relatively high resistor (kΩ) so we can implement the resistor using either a diffused or undoped-poly resistor

 - this resistor takes a large amount of die area to implement



Resistive-Load Inverter

• Resistive-Load Inverter


- we solve for $V_{out}(V_{in})$ using KVL where:

$$V_{out} = V_{DD} - R_L \cdot I_R$$

$$I_R = I_{DS} = \frac{V_{DD} - V_{out}}{R_L}$$

- we solve for V_{OH} and V_{OL}

 
- applying $V_{in} = V_{GS} = \text{logic '0' or '1'}$
- determining the mode of operation (cut-off, linear, sat)
- creating an equation relating I_{DS} , V_{out} , and V_{in}



Resistive-Load Inverter

Resistive-Load Inverter

- we solve for V_{IH} and V_{IL}
 - applying $V_{in}=V_{GS}=\text{logic "0" or "1"}$
 - determining the mode of operation (cut-off, linear, sat)
 - creating an equation relating I_{DS} , V_{DS} , and V_{in}
- remember that V_{IH} and V_{IL} are defined as the input voltage when the output has a slope of -1
- then we need to:
 - differentiate the equation with respect to V_{in}
 - plug in $(dV_{out}/dV_{in})=-1$
 - solve for V_{IH} or V_{IL}
- note that the solution will be quadratic (i.e., have two solutions). We pick the logical solution i.e., the smaller solution for V_{IL} and the larger solution for V_{IH}

 

Resistive-Load Inverter

Resistive-Load Inverter

- these solutions yield:

$$V_{OH} = V_{DD}$$

$$V_{OL} = V_{DD} - V_{T0} + \frac{1}{k_n \cdot R_L} - \sqrt{\left(V_{DD} - V_{T0} + \frac{1}{k_n \cdot R_L}\right)^2 - \frac{2 \cdot V_{DD}}{k_n \cdot R_L}}$$

$$V_{IH} = V_{T0} + \sqrt{\frac{8}{3} \cdot \frac{V_{DD}}{k_n \cdot R_L}} - \frac{1}{k_n \cdot R_L}$$


$$V_{IL} = V_{T0} + \frac{1}{k_n \cdot R_L}$$



Resistive-Load Inverter

Resistive-Load Inverter

 
- notice that these solutions only depend on $k_n \cdot R_L$
- we have control over W & L , which alters k_n
- we have control over R_L by altering the shape of the resistor



Active-Load Inverter

Inverter with Enhancement-Type NMOS Load

 
- the resistive-load inverter takes a lot of chip area due to the resistor which makes it impractical for VLSI
- another way to implement the load is to use an enhancement-type NMOS transistor
- this gives a load that takes less area
- this topology can have the load either in the linear or saturation region depending on how it is biased



Active-Load Inverter

Inverter with Depletion-Type NMOS Load

 
- the enhancement-type NMOS load has the drawback of a larger DC current when not switching.
- this power consumption makes it less than ideal for VLSI
- another technique is to use a depletion-type NMOS load
- this gives a sharper VTC curve and better noise margin
- however, an additional process step is required to create the depletion-type device



CMOS Inverter

CMOS Inverter


- the CMOS inverter uses an NMOS and a PMOS transistor in a complementary push/pull configuration
- for a Logic "1" output, the PMOS=ON and the NMOS=OFF
- for a Logic "0" output, the PMOS=OFF and the NMOS=ON
- this configuration has two major advantages:
 - 1) low static power consumption : due to one MOSFET always being off
 - 2) a sharp and symmetric VTC profile giving full swing signals ($1=V_{DD}$, $0=V_{SS}$)

 

CMOS Inverter

CMOS Inverter

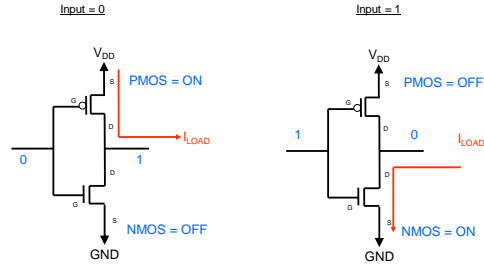- basic operation, complementary switches



CMOS Inverter

CMOS Inverter Static Behavior


- let's start the Static Analysis by describing the regions of operation as the Inverter Switches
- Remember that:

$$V_{GS,n} = V_{in}$$

$$V_{DS,n} = V_{out}$$

$$V_{GS,p} = -(V_{DD} - V_{in})$$

$$V_{DS,p} = -(V_{DD} - V_{out})$$

 

CMOS Inverter

CMOS Inverter Static Behavior

Region A

- let's assume $V_{DD}=5V$, $V_{Tn}=1$, $V_{Tp}=-1$ ($V_{in}=0V$, $V_{out}=5V$)

- When $V_{in}=0V$, the output is $V_{out}=V_{DD}$


- the NMOS transistor is OFF since $V_{GS,n} \leq V_{Tn}$ (**cut-off**) i.e., $0 \leq 1$

- the NMOS drain current $I_{Dn}=0$

- the PMOS transistor is ON since $V_{GS,p} \leq V_{Tp}$ i.e., $(0-5) \leq -1$

- the PMOS drain current $I_{Dp}=0$ since $I_{Dn}=I_{Dp}$

 - since $V_{DS,n}=0V$, then the PMOS is in the **linear region** since: $V_{DS,p} > (V_{GS,p}-V_{Tp})$ i.e., $0 > (0-5) - (-1)$



CMOS Inverter

CMOS Inverter Static Behavior

Region B


- Now let's move V_{in} above V_{Tn} , but below V_{th} ($V_{in}=1V$, $V_{out}=5V$)

- the NMOS transistor turns ON since $V_{GS,n} \geq V_{Tn}$ i.e., $1 \geq 1$

- since $V_{DS,n}$ is still near V_{DD} , the NMOS goes directly into **saturation** since: $V_{DS,n} > (V_{GS,n}-V_{Tn})$ i.e., $(-5) > -1$

- the PMOS transistor is still ON since $V_{GS,p} \leq V_{Tp}$ i.e., $(-1-5) \leq -1$

 - the PMOS is still in the **linear region** since: $V_{DS,p} > (V_{GS,p}-V_{Tp})$ i.e., $(-5) > (1-5) - (-1)$



CMOS Inverter

CMOS Inverter Static Behavior

Region C

- Now let's move to where $V_{in} = V_{out}$ ($V_{in}=2.5V$, $V_{out}=2.5V$)


- This is defined as V_{th}

- the NMOS transistor is ON since $V_{GS,n} \geq V_{Tn}$ i.e., $2.5 \geq 1$

- the NMOS transistor is in **saturation** since $V_{DS,n} > (V_{GS,n}-V_{Tn})$ i.e., $-2.5 > (2.5-1)$

- the PMOS transistor is ON since $V_{GS,p} \leq V_{Tp}$ i.e., $(2.5-5) \leq -1$

 - the PMOS is in **saturation** since: $V_{DS,p} < (V_{GS,p}-V_{Tp})$ i.e., $(2.5-5) < (2.5-5) - (-1)$



CMOS Inverter

CMOS Inverter Static Behavior

Region D


- Now let's move V_{in} above V_{th} but below $(V_{DD}+1)$ ($V_{in}=4V$, $V_{out}=1V$)

- the NMOS transistor is ON since $V_{GS,n} \geq V_{Tn}$ i.e., $4 \geq 1$

- the NMOS transistor is in **linear** since $V_{DS,n} < (V_{GS,n}-V_{Tn})$ i.e., $-1 < (4-1)$

- the PMOS transistor is ON since $V_{GS,p} \leq V_{Tp}$ i.e., $(4-5) \leq -1$

 - the PMOS is in **saturation** since: $V_{DS,p} < (V_{GS,p}-V_{Tp})$ i.e., $(1-5) < (4-5) - (-1)$




CMOS Inverter

CMOS Inverter Static Behavior

Region E

 - Now let's move V_{in} above $(V_{DD} + V_{T,p})$ ($V_{in} = 5V$, $V_{out} = 0V$)
- the NMOS transistor is ON since $V_{GS,n} \geq V_{T,n}$ i.e., $5 \geq 1$
- the NMOS transistor is in **linear** since $V_{DS,n} < (V_{GS,n} - V_{T,n})$ i.e., $-0 < (5 - 1)$
- the PMOS transistor is OFF since $V_{GS,p} \geq V_{T,p}$ i.e., $(5-5) \geq -1$ (**cut-off**)




CMOS Inverter

CMOS Inverter Static Behavior

Summary

Region	NMOS	PMOS
A	cut-off	linear
B	saturation	linear
C	saturation	saturation
D	linear	saturation
E	linear	cut-off

 

CMOS Inverter

CMOS Inverter Static Behavior (V_{OH} & V_{OL})

- Now let's calculate the static operating specifications
- V_{OH} and V_{OL} are trivial since $I_{D,p} = I_{D,n} = 0A$ in both cases
- this condition gives a full output swing across the complementary structure:

$$\begin{aligned} V_{OH} &= V_{DD} \\ V_{OL} &= V_{SS} \end{aligned}$$

- Note that V_{DD} is typically the power supply and V_{SS} is typically GND.



CMOS Inverter


CMOS Inverter Static Behavior (V_{in})

- V_{in} is defined as the input voltage that corresponds to the higher of the two output voltages with a slope of -1.
- we know the modes of operation for the transistors in this region:

NMOS = saturation
PMOS = linear

- we also know from KCL that $I_{D,p} = I_{D,n}$
- from this, we can write our first current equation:
 
$$\begin{aligned} I_{D,n(sat)} &= I_{D,p(linear)} \\ \frac{k_n}{2} (V_{GS,n} - V_{T0,n})^2 &= \frac{k_p}{2} [2 \cdot (V_{GS,p} - V_{T0,p}) \cdot V_{DS,p} - V_{DS,p}^2] \end{aligned}$$



CMOS Inverter

CMOS Inverter Static Behavior (V_{in}) cont...

- remembering the relationships between V_{in} , V_{out} , and V_{GS} & V_{DS} :

$$\begin{aligned} V_{GS,n} &= V_{in} \\ V_{DS,n} &= V_{out} \\ V_{GS,p} &= -(V_{DD} - V_{in}) = V_{in} - V_{DD} \\ V_{DS,p} &= -(V_{DD} - V_{out}) = V_{out} - V_{DD} \end{aligned}$$

- we can write:

$$\frac{k_n}{2} (V_{in} - V_{T0,n})^2 = \frac{k_p}{2} [2 \cdot (V_{in} - V_{DD} - V_{T0,p}) \cdot (V_{out} - V_{DD}) - (V_{out} - V_{DD})^2]$$



CMOS Inverter

CMOS Inverter Static Behavior (V_{in}) cont...

- we are looking for when the derivative of $dV_{out}/dV_{in} = -1$ so we differentiate both sides:

$$\frac{d}{dV_{in}} \left(\frac{k_n}{2} (V_{in} - V_{T0,n})^2 \right) = \frac{d}{dV_{in}} \left(\frac{k_p}{2} [2 \cdot (V_{in} - V_{DD} - V_{T0,p}) \cdot (V_{out} - V_{DD}) - (V_{out} - V_{DD})^2] \right)$$

- the left-hand-side is straight forward to perform a partial derivative on (with respect to V_{in}), but the right-hand side consists of two products that must be differentiated using the product rule.

Remember the product rule:

$$\begin{aligned} Z &= f(x,y) \cdot g(x,y) \\ \frac{dZ}{dx} &= \frac{df}{dx} \cdot g(x,y) + \frac{dg}{dx} \cdot f(x,y) \end{aligned}$$



CMOS Inverter

CMOS Inverter Static Behavior (V_{IL}) cont...

- let's re-write the RHS as the sum of two products:

$$\frac{d}{dV_{in}} \left(\frac{k_n}{2} (V_{in} - V_{T0,n})^2 \right) = \frac{d}{dV_{in}} \left(\frac{k_p}{2} \cdot \underbrace{[2 \cdot (V_{in} - V_{DD} - V_{T0,p}) \cdot (V_{out} - V_{DD})]}_{\text{Product \#1}} - \underbrace{(V_{out} - V_{DD}) \cdot (V_{out} - V_{DD})}_{\text{Product \#2}} \right)$$

- the left-hand-side is straight forward to perform a partial derivative on (with respect to V_{in}),

$$LHS = k_n \cdot (V_{in} - V_{T0,n})$$



CMOS Inverter

CMOS Inverter Static Behavior (V_{IL}) cont...

- now let's perform a partial derivative on the RHS (with respect to V_{in}) using the product rule:

$$RHS = \frac{d}{dV_{in}} \left(\frac{k_p}{2} \cdot [2 \cdot (V_{in} - V_{DD} - V_{T0,p}) \cdot (V_{out} - V_{DD}) - (V_{out} - V_{DD}) \cdot (V_{out} - V_{DD})] \right)$$

$$RHS = \frac{k_p}{2} \cdot \left[2 \cdot \left((1) \cdot (V_{out} - V_{DD}) + (V_{in} - V_{DD} - V_{T0,p}) \cdot \left(\frac{dV_{out}}{dV_{in}} \right) \right) - \left(\left(\frac{dV_{out}}{dV_{in}} \right) \cdot (V_{out} - V_{DD}) + (V_{out} - V_{DD}) \cdot \left(\frac{dV_{out}}{dV_{in}} \right) \right) \right]$$

Combine two like expressions

$$RHS = \frac{k_p}{2} \cdot \left[2 \cdot \left((1) \cdot (V_{out} - V_{DD}) + (V_{in} - V_{DD} - V_{T0,p}) \cdot \left(\frac{dV_{out}}{dV_{in}} \right) \right) - 2 \cdot (V_{out} - V_{DD}) \cdot \left(\frac{dV_{out}}{dV_{in}} \right) \right]$$

Pull out 2

$$RHS = k_p \cdot \left[(V_{out} - V_{DD}) + (V_{in} - V_{DD} - V_{T0,p}) \cdot \left(\frac{dV_{out}}{dV_{in}} \right) - (V_{out} - V_{DD}) \cdot \left(\frac{dV_{out}}{dV_{in}} \right) \right]$$

Rearrange expression

$$RHS = k_p \cdot \left[(V_{in} - V_{DD} - V_{T0,p}) \cdot \left(\frac{dV_{out}}{dV_{in}} \right) + (V_{out} - V_{DD}) - (V_{out} - V_{DD}) \cdot \left(\frac{dV_{out}}{dV_{in}} \right) \right]$$



CMOS Inverter

CMOS Inverter Static Behavior (V_{IL}) cont...

- now our complete differentiated expression is:

$$k_n \cdot (V_{in} - V_{T0,n}) = k_p \cdot \left[(V_{in} - V_{DD} - V_{T0,p}) \cdot \left(\frac{dV_{out}}{dV_{in}} \right) + (V_{out} - V_{DD}) - (V_{out} - V_{DD}) \cdot \left(\frac{dV_{out}}{dV_{in}} \right) \right]$$

- let's plug in the condition we're solving for ($dV_{out}/dV_{in} = -1$)

$$k_n \cdot (V_{in} - V_{T0,n}) = k_p \cdot \left[(V_{in} - V_{DD} - V_{T0,p}) \cdot (-1) + (V_{out} - V_{DD}) - (V_{out} - V_{DD}) \cdot (-1) \right]$$

$$k_n \cdot (V_{in} - V_{T0,n}) = k_p \cdot \left[-V_{in} + V_{DD} + V_{T0,p} + V_{out} - V_{DD} + V_{out} - V_{DD} \right]$$

$$k_n \cdot (V_{in} - V_{T0,n}) = k_p \cdot (2 \cdot V_{out} - V_{in} + V_{T0,p} - V_{DD})$$

- then we can substitute $V_{in} = V_{IL}$:

$$k_n \cdot (V_{IL} - V_{T0,n}) = k_p \cdot (2 \cdot V_{out} - V_{IL} + V_{T0,p} - V_{DD})$$



CMOS Inverter

CMOS Inverter Static Behavior (V_{IL}) cont...

- let's rearrange to solve for V_{IL} :

$$k_n \cdot (V_{IL} - V_{T0,n}) = k_p \cdot (2 \cdot V_{out} - V_{IL} + V_{T0,p} - V_{DD})$$

$$k_n \cdot V_{IL} - k_n \cdot V_{T0,n} = k_p \cdot 2 \cdot V_{out} - k_p \cdot V_{IL} + k_p \cdot V_{T0,p} - k_p \cdot V_{DD}$$

Multiply through by k_n & k_p

$$k_n \cdot V_{IL} + k_p \cdot V_{IL} = k_p \cdot 2 \cdot V_{out} + k_p \cdot V_{T0,p} + k_n \cdot V_{T0,n} - k_p \cdot V_{DD}$$

Arrange V_{IL} terms on LHS

$$V_{IL} \cdot (k_n + k_p) = k_p \cdot 2 \cdot V_{out} + k_p \cdot V_{T0,p} + k_n \cdot V_{T0,n} - k_p \cdot V_{DD}$$

Pull out V_{IL} of LHS

$$V_{IL} = \frac{k_p \cdot 2 \cdot V_{out} + k_p \cdot V_{T0,p} + k_n \cdot V_{T0,n} - k_p \cdot V_{DD}}{k_n + k_p}$$

Bring (rev) to RHS



CMOS Inverter

CMOS Inverter Static Behavior (V_{IL}) cont...

- to make this a little simpler, let's divide the top and bottom of the RHS by k_p :

$$V_{IL} = \frac{\frac{k_p}{k_p} \cdot 2 \cdot V_{out} + \frac{k_p}{k_p} \cdot V_{T0,p} + \frac{k_n}{k_p} \cdot V_{T0,n} - \frac{k_p}{k_p} \cdot V_{DD}}{\frac{k_n}{k_p} + \frac{k_p}{k_p}}$$

- let's define k_R as the ratio of:

$$k_R = \frac{k_n}{k_p}$$



CMOS Inverter

CMOS Inverter Static Behavior (V_{IL}) cont...

- substituting in k_R , we get our final expression for V_{IL} :

$$V_{IL} = \frac{2 \cdot V_{out} + V_{T0,p} - V_{DD} + k_R \cdot V_{T0,n}}{1 + k_R}$$

NOTE:

- this still depends on V_{out} . This means to get a numerical solution, we must solve this together with our expression relating the drain currents:

$$\frac{k_n}{2} \cdot (V_{IL} - V_{T0,n})^2 = \frac{k_p}{2} \cdot [2 \cdot (V_{IL} - V_{DD} - V_{T0,p}) \cdot (V_{out} - V_{DD}) - (V_{out} - V_{DD})^2]$$

this gives us two expressions and two unknowns (V_{IL} and V_{out})



CMOS Inverter

CMOS Inverter Static Behavior (V_{in})

- V_{in} is defined as the input voltage that corresponds to the lower of the two output voltages with a slope of -1.

- we know the modes of operation for the transistors in this region:


NMOS = linear
PMOS = saturation

- we also know from KCL that $I_{D,P} = I_{D,N}$

- from this, we can write our first current equation:

$$I_{D,n(\text{lin})} = I_{D,p(\text{sat})}$$
 
$$\frac{k_n}{2} [2 \cdot (V_{GS,n} - V_{T0,n}) \cdot V_{DS,n} - V_{DS,n}^2] = \frac{k_p}{2} \cdot (V_{GS,p} - V_{T0,p})^2$$



CMOS Inverter

CMOS Inverter Static Behavior (V_{in}) cont...

- remembering the relationships between V_{in} , V_{out} , and V_{GS} & V_{DS} :

$$V_{GS,n} = V_{in}$$

$$V_{DS,n} = V_{out}$$

$$V_{GS,p} = -(V_{DD} - V_{in}) = V_{in} - V_{DD}$$

$$V_{DS,p} = -(V_{DD} - V_{out}) = V_{out} - V_{DD}$$

- we can write:

$$\frac{k_n}{2} \cdot [2 \cdot (V_{in} - V_{T0,n}) \cdot V_{out} - V_{out}^2] = \frac{k_p}{2} \cdot (V_{in} - V_{DD} - V_{T0,p})^2$$



CMOS Inverter

CMOS Inverter Static Behavior (V_{in}) cont...

- we are looking for when the derivative of $dV_{out}/dV_{in} = -1$ so we differentiate both sides:

$$\frac{d}{dV_{in}} \left(\frac{k_n}{2} \cdot [2 \cdot (V_{in} - V_{T0,n}) \cdot V_{out} - V_{out}^2] \right) = \frac{d}{dV_{in}} \left(\frac{k_p}{2} \cdot (V_{in} - V_{DD} - V_{T0,p})^2 \right)$$

- once again, we have a situation where we are differentiating an expression that contains product terms

we use the product rule again:

$$Z = f(x, y) \cdot g(x, y)$$

$$\frac{dZ}{dx} = \frac{df}{dx} \cdot g(x, y) + \frac{dg}{dx} \cdot f(x, y)$$



CMOS Inverter

CMOS Inverter Static Behavior (V_{in}) cont...

- let's expand the product terms in the LHS:

$$\frac{d}{dV_{in}} \left(\frac{k_n}{2} \cdot [2 \cdot (V_{in} - V_{T0,n}) \cdot V_{out} - (V_{out}) \cdot (V_{out})] \right) = \frac{d}{dV_{in}} \left(\frac{k_p}{2} \cdot (V_{in} - V_{DD} - V_{T0,p})^2 \right)$$

Product #1 Product #2

- the right-hand-side is straight forward to perform a partial derivative on (with respect to V_{in}).

$$RHS = k_p \cdot (V_{in} - V_{DD} - V_{T0,p})$$



CMOS Inverter

CMOS Inverter Static Behavior (V_{in}) cont...

- now let's perform a partial derivative on the LHS (with respect to V_{in}) using the product rule:

$$LHS = \frac{d}{dV_{in}} \left(\frac{k_n}{2} \cdot [2 \cdot (V_{in} - V_{T0,n}) \cdot V_{out} - (V_{out}) \cdot (V_{out})] \right)$$

$$\frac{df}{dx} \cdot g(x, y) + \frac{dg}{dx} \cdot f(x, y)$$

$$LHS = \frac{k_n}{2} \cdot \left[2 \cdot \left((1) \cdot V_{out} + (V_{in} - V_{T0,n}) \cdot \left(\frac{dV_{out}}{dV_{in}} \right) \right) - \left((V_{out}) \cdot \left(\frac{dV_{out}}{dV_{in}} \right) + (V_{out}) \cdot \left(\frac{dV_{out}}{dV_{in}} \right) \right) \right]$$

$$LHS = \frac{k_n}{2} \cdot \left[2 \cdot \left((1) \cdot V_{out} + (V_{in} - V_{T0,n}) \cdot \left(\frac{dV_{out}}{dV_{in}} \right) \right) - 2 \cdot \left(V_{out} \cdot \left(\frac{dV_{out}}{dV_{in}} \right) \right) \right]$$

Combine like expressions

$$LHS = k_n \cdot \left[(1) \cdot V_{out} + (V_{in} - V_{T0,n}) \cdot \left(\frac{dV_{out}}{dV_{in}} \right) - \left(V_{out} \cdot \left(\frac{dV_{out}}{dV_{in}} \right) \right) \right]$$

Pull out 2

$$LHS = k_n \cdot \left[(V_{in} - V_{T0,n}) \cdot \left(\frac{dV_{out}}{dV_{in}} \right) + V_{out} - V_{out} \cdot \left(\frac{dV_{out}}{dV_{in}} \right) \right]$$

Rearrange expression



CMOS Inverter

CMOS Inverter Static Behavior (V_{in}) cont...

- now our complete differentiated expression is:

$$k_n \cdot \left[(V_{in} - V_{T0,n}) \cdot \left(\frac{dV_{out}}{dV_{in}} \right) + V_{out} - V_{out} \cdot \left(\frac{dV_{out}}{dV_{in}} \right) \right] = k_p \cdot (V_{in} - V_{DD} - V_{T0,p})$$

- let's plug in the condition we're solving for ($dV_{out}/dV_{in} = -1$)

$$k_n \cdot \left[(V_{in} - V_{T0,n}) \cdot (-1) + V_{out} - V_{out} \cdot (-1) \right] = k_p \cdot (V_{in} - V_{DD} - V_{T0,p})$$

$$k_n \cdot \left[-V_{in} + V_{T0,n} + V_{out} + V_{out} \right] = k_p \cdot (V_{in} - V_{DD} - V_{T0,p})$$

$$k_n \cdot (-V_{in} + V_{T0,n} + 2 \cdot V_{out}) = k_p \cdot (V_{in} - V_{DD} - V_{T0,p})$$

- then we can substitute $V_{in} = V_{th}$:

$$k_n \cdot (-V_{th} + V_{T0,n} + 2 \cdot V_{out}) = k_p \cdot (V_{th} - V_{DD} - V_{T0,p})$$



CMOS Inverter

CMOS Inverter Static Behavior (V_{th}) cont...

- let's rearrange to solve for V_{th} :

$$k_n \cdot (-V_{th} + V_{T0,n} + 2 \cdot V_{out}) = k_p \cdot (V_{th} - V_{DD} - V_{T0,p})$$

$$-k_n \cdot V_{th} + k_n \cdot V_{T0,n} + 2 \cdot k_n \cdot V_{out} = k_p \cdot V_{th} - k_p \cdot V_{DD} - k_p \cdot V_{T0,p} \quad \text{Multiply through by } k_n \& k_p$$

$$-k_n \cdot V_{th} - k_p \cdot V_{th} = -k_p \cdot V_{DD} - k_p \cdot V_{T0,p} - k_n \cdot V_{T0,n} - 2 \cdot k_n \cdot V_{out} \quad \text{Arrange } V_{th} \text{ terms on LHS}$$

$$-V_{th} \cdot (k_n + k_p) = -k_p \cdot V_{DD} - k_p \cdot V_{T0,p} - k_n \cdot V_{T0,n} - 2 \cdot k_n \cdot V_{out} \quad \text{Pull out } V_{th} \text{ of LHS}$$

$$V_{th} \cdot (k_n + k_p) = k_p \cdot V_{DD} + k_p \cdot V_{T0,p} + k_n \cdot V_{T0,n} + 2 \cdot k_n \cdot V_{out} \quad \text{Multiply both sides by } -1$$

$$V_{th} = \frac{k_p \cdot V_{DD} + k_p \cdot V_{T0,p} + k_n \cdot V_{T0,n} + 2 \cdot k_n \cdot V_{out}}{k_n + k_p} \quad \text{Bring (invert) to RHS}$$



CMOS Inverter

CMOS Inverter Static Behavior (V_{th}) cont...

- again, let's divide the top and bottom of the RHS by k_p :

$$V_{th} = \frac{\frac{k_p}{k_p} \cdot V_{DD} + \frac{k_p}{k_p} \cdot V_{T0,p} + \frac{k_n}{k_p} \cdot V_{T0,n} + 2 \cdot \frac{k_n}{k_p} \cdot V_{out}}{\frac{k_n}{k_p} + \frac{k_p}{k_p}}$$

- remember that we defined k_R as:

$$k_R = \frac{k_n}{k_p}$$



CMOS Inverter

CMOS Inverter Static Behavior (V_{th}) cont...

- substituting in k_R , we get our final expression for V_{th} :

$$V_{th} = \frac{V_{DD} + V_{T0,p} + k_R \cdot V_{T0,n} + 2 \cdot k_R \cdot V_{out}}{1 + k_R}$$

$$V_{th} = \frac{V_{DD} + V_{T0,p} + k_R \cdot (2 \cdot V_{out} + V_{T0,n})}{1 + k_R}$$

NOTE:

- this expression again depends on V_{out} . This means to get a numerical solution, we must solve this together with our expression relating the drain currents (where $V_{in} = V_{th}$):

$$\frac{k_n}{2} \cdot [2 \cdot (V_{th} - V_{T0,n}) \cdot V_{out} - V_{out}^2] = \frac{k_p}{2} \cdot (V_{th} - V_{DD} - V_{T0,p})^2$$

this gives us two expressions and two unknowns (V_{th} and V_{out})



CMOS Inverter

CMOS Inverter Static Behavior

- we now have all of the critical voltages to describe the Noise Margins of the Inverter:

$$V_{OL} = 0$$

$$V_{OH} = V_{DD}$$

$$V_{IL} = \frac{2 \cdot V_{out} + V_{T0,p} - V_{DD} + k_R \cdot V_{T0,n}}{1 + k_R}$$

$$V_{IH} = \frac{V_{DD} + V_{T0,p} + k_R \cdot (2 \cdot V_{out} + V_{T0,n})}{1 + k_R}$$




CMOS Inverter Threshold

CMOS Inverter Static Behavior (V_{th})

- one of the most important static parameters of a CMOS inverter is the switching Threshold

- Remember that V_{th} is defined as when $V_{in} = V_{out}$

 - this occurs in Region C of the VTC where both transistors are in **saturation**




CMOS Inverter Threshold

CMOS Inverter Static Behavior (V_{th}) cont...

- since we know the modes of operation we can write KCL to get our current equation:

$$I_{D,n(sat)} = -I_{D,p(sat)}$$
 
$$\frac{k_n}{2} \cdot (V_{GS,n} - V_{T0,n})^2 = -\frac{k_p}{2} \cdot (V_{GS,p} - V_{T0,p})^2$$



CMOS Inverter Threshold

- CMOS Inverter Static Behavior (V_{in}) cont...

- remembering the relationships between V_{in} , V_{out} and V_{GS} & V_{DS} :

$$\begin{aligned} V_{GS,n} &= V_{in} \\ V_{DS,n} &= V_{out} \\ V_{GS,p} &= -(V_{DD} - V_{in}) = V_{in} - V_{DD} \\ V_{DS,p} &= -(V_{DD} - V_{out}) = V_{out} - V_{DD} \end{aligned}$$

- we can write:

$$\frac{k_n}{2} \cdot (V_{in} - V_{T0,n})^2 = \frac{k_p}{2} \cdot (V_{in} - V_{DD} - V_{T0,p})^2$$



CMOS Inverter Threshold

- CMOS Inverter Static Behavior (V_{in}) cont...

- now we solve for V_{in}

$$\frac{k_n}{2} \cdot (V_{in} - V_{T0,n})^2 = \frac{k_p}{2} \cdot (V_{in} - V_{DD} - V_{T0,p})^2$$

- let's walk through the steps of this solution:

$$k_n \cdot (V_{in} - V_{T0,n})^2 = k_p \cdot (V_{in} - V_{DD} - V_{T0,p})^2$$

Multiply both sides by 2

$$\sqrt{k_n} \cdot (V_{in} - V_{T0,n}) = \sqrt{k_p} \cdot (V_{in} - V_{DD} - V_{T0,p})$$

Take square root of both sides

$$\sqrt{k_n} \cdot \sqrt{(V_{in} - V_{T0,n})^2} = \sqrt{k_p} \cdot \sqrt{(V_{in} - V_{DD} - V_{T0,p})^2}$$

Break square roots into equivalent products

$$\sqrt{k_n} \cdot (V_{in} - V_{T0,n}) = -\sqrt{k_p} \cdot (V_{in} - V_{DD} - V_{T0,p})$$

Simplify the square roots. Choosing the correct solution for 'in' under the square gives a negative.

$$(V_{in} - V_{T0,n}) = -\frac{\sqrt{k_p}}{\sqrt{k_n}} \cdot (V_{in} - V_{DD} - V_{T0,p})$$

Divide by sqrt(k_n)



CMOS Inverter Threshold

- CMOS Inverter Static Behavior (V_{in}) cont...

- continuing...

$$V_{in} - V_{T0,n} = -\sqrt{\frac{k_p}{k_n}} \cdot (V_{in} - V_{DD} - V_{T0,p})$$

Simplify the square root ratio

$$V_{in} - V_{T0,n} = -\sqrt{\frac{k_p}{k_n}} \cdot (V_{in} - (V_{DD} + V_{T0,p}))$$

Group the V_{in} and V_{DD} terms

$$V_{in} - V_{T0,n} = -\sqrt{\frac{k_p}{k_n}} \cdot V_{in} + \sqrt{\frac{k_p}{k_n}} \cdot (V_{DD} + V_{T0,p})$$

Multiply through the sqrt(k_p/k_n) term

$$V_{in} + \sqrt{\frac{k_p}{k_n}} \cdot V_{in} = V_{T0,n} + \sqrt{\frac{k_p}{k_n}} \cdot (V_{DD} + V_{T0,p})$$

Rearrange terms to get Vin on the LHS

$$V_{in} \cdot \left(1 + \sqrt{\frac{k_p}{k_n}}\right) = V_{T0,n} + \sqrt{\frac{k_p}{k_n}} \cdot (V_{DD} + V_{T0,p})$$

Pull out Vin of LHS



CMOS Inverter Threshold

- CMOS Inverter Static Behavior (V_{in}) cont...

- continuing...

$$V_{in} = \frac{V_{T0,n} + \sqrt{\frac{k_p}{k_n}} \cdot (V_{DD} + V_{T0,p})}{\left(1 + \sqrt{\frac{k_p}{k_n}}\right)}$$

Divide both sides by $(1 + \sqrt{k_p/k_n})$

$$V_{in} = \frac{V_{T0,n} + \sqrt{\frac{1}{k_R}} \cdot (V_{DD} + V_{T0,p})}{\left(1 + \sqrt{\frac{1}{k_R}}\right)}$$

Substitute in $k_n = k_p/k_R$

$$V_{in} = \frac{V_{T0,n} + \sqrt{\frac{1}{k_R}} \cdot (V_{DD} + V_{T0,p})}{\left(1 + \sqrt{\frac{1}{k_R}}\right)}$$

Replace Vin with Vth



CMOS Inverter Threshold

- CMOS Inverter Static Design

- notice that V_{DD} , $V_{T0,p}$, and $V_{T0,n}$ are constants for a given system:

- this means that the only thing that effects the switching threshold is k_R


$$V_{in} = \frac{V_{T0,n} + \sqrt{\frac{1}{k_R}} \cdot (V_{DD} + V_{T0,p})}{\left(1 + \sqrt{\frac{1}{k_R}}\right)}$$



CMOS Inverter Threshold

- CMOS Inverter Static Design

 - we actually have control over k_R by altering the Widths and Lengths of the transistors:



CMOS Inverter Threshold

• **CMOS Inverter Static Design**

$$V_{th} = \frac{V_{DD} + \sqrt{\frac{1}{k_R}} (V_{DD} + V_{T0,p})}{1 + \sqrt{\frac{1}{k_R}}}$$

Original expression for V_{th}

- let's relate the threshold voltage's sensitivity to k_R :

$$V_{th} \left(1 + \sqrt{\frac{1}{k_R}} \right) = V_{T0,n} + \sqrt{\frac{1}{k_R}} (V_{DD} + V_{T0,p})$$

Multiply both sides by $(1 + \sqrt{1/k_R})$

$$V_{th} + V_{th} \sqrt{\frac{1}{k_R}} = V_{T0,n} + \sqrt{\frac{1}{k_R}} (V_{DD} + V_{T0,p})$$

Multiply V_{th} through

$$V_{th} - V_{T0,n} = \sqrt{\frac{1}{k_R}} (V_{DD} + V_{T0,p}) - V_{th} \sqrt{\frac{1}{k_R}}$$

Rearrange terms to get k_R on RHS

$$V_{th} - V_{T0,n} = \sqrt{\frac{1}{k_R}} (V_{DD} + V_{T0,p} - V_{th})$$

Pull out $(1 + \sqrt{1/k_R})$

$$\sqrt{\frac{1}{k_R}} = \frac{V_{th} - V_{T0,n}}{V_{DD} + V_{T0,p} - V_{th}}$$

Divide to get k_R term alone



CMOS Inverter Threshold

• **CMOS Inverter Static Design**

- rearranging the expression to get in terms of k_R , we get:

$$k_R = \frac{k_n}{k_p} = \left(\frac{V_{DD} + V_{T0,p} - V_{th}}{V_{th} - V_{T0,n}} \right)^2$$

- an ideal inverter puts the switching threshold directly in the middle of the voltage swing:

$$V_{th,ideal} = \frac{V_{DD}}{2}$$

- if we plug in the ideal threshold voltage, we get:

$$\left(\frac{k_n}{k_p} \right)_{ideal} = \left(\frac{V_{DD} + V_{T0,p} - 0.5 \cdot V_{DD}}{0.5 \cdot V_{DD} - V_{T0,n}} \right)^2 = \left(\frac{0.5 \cdot V_{DD} + V_{T0,p}}{0.5 \cdot V_{DD} - V_{T0,n}} \right)^2$$



CMOS Inverter Threshold

• **CMOS Inverter Static Design**

- in most processes, $V_{T0,n} = |V_{T0,p}|$.

- since $V_{T0,p}$ is negative, then our Transconductance ratio looks like:

$$\left(\frac{k_n}{k_p} \right)_{ideal} = \left(\frac{0.5 \cdot V_{DD} + V_{T0,p}}{0.5 \cdot V_{DD} - V_{T0,n}} \right)^2 = 1$$



CMOS Inverter Threshold

• **CMOS Inverter Static Design**

- remembering the expression for k_n/k_p , we can see that C_{ox} will not have an effect:

$$k_R = \frac{k_n}{k_p} = \frac{\mu_n \cdot C_{ox} \cdot \left(\frac{W}{L}\right)_n}{\mu_p \cdot C_{ox} \cdot \left(\frac{W}{L}\right)_p} = \frac{\mu_n \cdot \left(\frac{W}{L}\right)_n}{\mu_p \cdot \left(\frac{W}{L}\right)_p}$$

- since for an ideal (symmetric) inverter, we have:

$$\left(\frac{k_n}{k_p} \right)_{ideal} = 1 = \frac{\mu_n \cdot \left(\frac{W}{L}\right)_n}{\mu_p \cdot \left(\frac{W}{L}\right)_p}$$



CMOS Inverter Threshold

• **CMOS Inverter Static Design**

- we can rearrange to see that for a symmetrical inverter:

$$\left(\frac{W}{L}\right)_p = \frac{\mu_n}{\mu_p} \left(\frac{W}{L}\right)_n$$


- this means that for the given electron mobility of a process, we can size the PMOS and NMOS transistors in order to move the switching threshold to $V_{DD}/2$



CMOS Inverter Threshold

• **CMOS Inverter Static Design**

 - sizing of the transistor can have a large impact on the noise margins and sensitivity of the inverter




CMOS Inverter Power

CMOS Inverter Power

- CMOS inverters don't draw a significant amount of current when they are static (except for leakage)
- however, when they switch, a path forms between V_{DD} and GND that goes through both transistors
- the peak current comes at $V_{in}=V_{out}$ when both devices are in saturation
- this current is also called *short circuit* since V_{DD} has a low resistance path to GND
- we typically say that the majority of current consumed in a CMOS inverter is *dynamic*
 
$$I_{D(max)} = \frac{k_n}{2} (V_{GS,n} - V_{T0,n})^2 = \frac{k_p}{2} (V_{GS,p} - V_{T0,p})^2$$




CMOS Inverter Power Supply Scaling

CMOS Inverter Power Supply

- in theory, we can reduce the power supply voltage to the point at which:

$$V_{DD,min} = V_{T0,n} + |V_{T0,p}|$$
- below this minimum amount, the inverter will exhibit *hysteresis*
- in reality, other noise sources in the system require us to select the supply voltage so that the Noise Margins are enough to ensure robust operation.
- most modern designs select V_{DD} to be $\sim 5xV_{T0}$

 


CMOS Inverter Area

CMOS Inverter Area

- there are many different ways to layout a CMOS inverter
- typically, the PMOS electron mobility is lower than the NMOS electron mobility
- this means that when we design a *symmetric* inverter, the PMOS device is larger
- we typically make the Lengths of the NMOS and PMOS devices equal (usually L_{min} of the process)
- this leaves simply the ratio of W_p to W_n as the only design parameters:
 
$$\frac{W_p}{W_n} = \frac{\mu_n}{\mu_p}$$



CMOS Switching Characteristics

CMOS Switching Characteristics


- we studied the DC (or Static) characteristics of the CMOS inverter
- we learned how to calculate: V_{OH} , V_{OL} , V_{IL} , V_{IH} , V_{in} , NM_L , NM_H
- we learned that we can modify some of these parameters using the W/L ratios of the inverter
- specifically, we say that the V_{in} is solely dependent on W/L and is usually the most important and most commonly controlled parameter
- we now turn to the Switching (or AC or Dynamic) behavior of the inverter
- the switching characteristics give us how *fast* the circuit will run
- when designing, we must meet both DC and AC specs



CMOS Switching Characteristics

CMOS Switching Characteristics

 
- in an AC analysis, we need to consider the capacitance in the circuit
- note that the parasitic inductance tends to be small enough to be ignored (for now!)
- we consider an inverter that is driving another CMOS device or multiple CMOS devices in parallel



CMOS Switching Characteristics

CMOS Switching Characteristics

 - there are 4 main groups of capacitance in the circuit
 - 1) Driver's Oxide Capacitance
 - 2) Driver's Junction Capacitance
 - 3) Interconnect Capacitance
 - 4) Receiver Oxide Capacitance




CMOS Switching Characteristics

CMOS Switching Characteristics

- we know that all of these capacitances vary as the dimensions of the inverter are altered and for various interconnect configurations
- in order to get a feel for how the capacitance effects performance, we assume that we can lump all of the capacitances into a fixed load capacitance (C_{load})
 
$$C_{load} = C_{gd,n} + C_{gd,p} + C_{dn,n} + C_{dn,p} + C_{int} + C_g$$



CMOS Switching Characteristics

CMOS Switching Characteristics

- in this expression we eliminate some of the capacitances:

$C_{dn,n}, C_{dn,p}$: There is no voltage change from $V_{dn,n}$ or $V_{dn,p}$ so there is no net capacitance

$C_{gs,n}, C_{gs,p}$: Since these are connected between V_{in} and V_{DD}/V_{SS} the input drives these capacitances. It is not part of the capacitance that the device output drives.

- this expression does include the interconnect and gate capacitance of the circuits that this inverter is driving

$$C_{load} = C_{gd,n} + C_{gd,p} + C_{dn,n} + C_{dn,p} + C_{int} + C_g$$

Oxides of Driver Junctions of Driver Interconnect Oxide of Receiver




CMOS Switching Characteristics

CMOS Switching Characteristics

- the speed of the device describes how fast we can charge or discharge the load capacitor

$$i_c = C \frac{dV}{dt}$$

 

CMOS Switching Characteristics

Delay Time Definition

- the delay is the time it takes to switch from the steady state level to the 50% level

$$\tau_{FHL} = t_1 - t_0$$

$$\tau_{FHL} = t_3 - t_2$$


$$V_{50\%} = V_{OL} + \frac{1}{2} \cdot (V_{OH} - V_{OL}) = \frac{1}{2} \cdot (V_{OH} + V_{OL})$$

- Note that in CMOS:

$$V_{OH} = V_{DD}$$

$$V_{OL} = V_{SS}$$

$$\text{So } V_{50\%} = V_{DD}/2$$

 


CMOS Switching Characteristics

Delay Time Derivation (τ_{PHL})

- The current that is used to discharge C_{load} is dictated by the region of operation that the NMOS is in.
- There are two distinct regions of operation that the NMOS operates in during the transition:

 - 1) V_{OH} to $(V_{OH} - V_{TN})$ NMOS in Saturation
- 2) $(V_{OH} - V_{TN})$ to $V_{50\%}$ NMOS in Linear



CMOS Switching Characteristics

Delay Time Derivation (τ_{PHL})

"Differential Equation Method"


- we can re-arrange the current expression in the capacitor to be:

$$i_c = -i_{D,n} = C_{load} \frac{dV_{out}}{dt}$$

$$dt = -C_{load} \frac{dV_{out}}{i_{D,n}}$$

- now we can integrate to solve for t

 - we need to perform two integrals, one for each of the two regions of operation



CMOS Switching Characteristics

Delay Time Derivation (τ_{PHL})

"Differential Equation Method"

- For the *saturation* region, our integral is:


$$t_1 - t_0 = \int_{t_0}^{t_1} dt = -C_{load} \int_{V_{OH}}^{V_{50\%}} \frac{1}{i_{D,n-sat}} dV_{out}$$

- For the *linear* region, our integral is:

$$t_1 - t_1' = \int_{t_1'}^{t_1} dt = -C_{load} \int_{V_{50\%}}^{V_{OL}} \frac{1}{i_{D,n-lin}} dV_{out}$$

- The delay is simply the sum of these two solutions:
 
$$\tau_{PHL} = (t_1 - t_0) + (t_1 - t_1')$$



CMOS Switching Characteristics

Delay Time Derivation (τ_{PHL})

"Differential Equation Method"

- evaluating these integrals and adding the two delays together, we get:

$$\tau_{PHL} = \frac{C_{load}}{k_n(V_{OH} - V_{T,n})} \left[\frac{2 \cdot V_{T,n}}{V_{OH} - V_{T,n}} + \ln \left(\frac{4(V_{DD} - V_{T,n})}{V_{OH} + V_{OL}} - 1 \right) \right]$$

- we can simplify this further by substituting in $V_{OH} = V_{DD}$ and $V_{OL} = 0$

$$\tau_{PHL} = \frac{C_{load}}{k_n(V_{DD} - V_{T,n})} \left[\frac{2 \cdot V_{T,n}}{V_{DD} - V_{T,n}} + \ln \left(\frac{4(V_{DD} - V_{T,n})}{V_{DD}} - 1 \right) \right]$$



CMOS Switching Characteristics

Delay Time Derivation (τ_{PHL})

"Differential Equation Method"

- we can follow the same process to find τ_{PHL} using the current equations for the PMOS:

$$\tau_{PHL} = \frac{C_{load}}{k_p(V_{DD} - |V_{T,p}|)} \left[\frac{2 \cdot |V_{T,p}|}{V_{DD} - |V_{T,p}|} + \ln \left(\frac{4(V_{DD} - |V_{T,p}|)}{V_{DD}} - 1 \right) \right]$$

- these solutions are accurate from the standpoint that we use the exact current in the transistors in our derivation of delay.

- these are still *estimates* and don't include *channel-length-modulation* or small-geometry effects



CMOS Switching Characteristics

Delay Time Derivation (τ_{PHL})

"Average Current Method"


- a simpler technique to estimate the delay is to use the *average current* in the capacitor during the transition.

- this is accomplished by solving for the current at the beginning of the transition and the current at the end of the transition and then averaging the two.

- at the beginning of the High-to-Low transition, the NMOS is in *saturation*

- at the end of the High-to-Low transition, the NMOS is in the *linear region*
 
$$\tau_{PHL} = \frac{C_{load} \cdot \Delta V_{HL}}{I_{avg,HL}} = \frac{C_{load} \cdot \Delta V_{HL}}{\frac{1}{2} [i_{D-sat} + i_{D-lin}]}$$



CMOS Switching Characteristics

Delay Time Derivation (τ_{PHL} & τ_{PLH})

"Average Current Method"

- we can write the expression in terms of the voltages at V_m ($V_{gs,n}$) and V_{out} ($V_{ds,n}$):

$$\tau_{PHL} = \frac{1}{2} \frac{C_{load} \cdot \Delta V_{HL}}{[i_{D-sat}(V_m = V_{OH}, V_{out} = V_{OH}) + i_{D-lin}(V_m = V_{OH}, V_{out} = V_{50\%})]}$$

$$\tau_{PLH} = \frac{1}{2} \frac{C_{load} \cdot \Delta V_{LH}}{[i_{D-sat}(V_m = V_{OL}, V_{out} = V_{OL}) + i_{D-lin}(V_m = V_{OL}, V_{out} = V_{50\%})]}$$

- this technique tends to be faster and easier to use than the *differential equation* method.




CMOS Switching Characteristics

Rise & Fall Time Definitions (τ_{rise} & τ_{fall})

- rise time (τ_{rise}) is the time it takes to transition from $V_{10\%}$ to $V_{90\%}$

 - fall time (τ_{fall}) is the time it takes to transition from $V_{90\%}$ to $V_{10\%}$



- we can use either the (1) *differential equation* or the (2) *average current* technique to solve for these

- in these transitions, the transistors again operate in both the *saturation* and *linear* regions

- the only difference is that the limits of the transition are $V_{10\%}$ and $V_{90\%}$



CMOS Switching Characteristics

Non-ideal Inputs

- in all of these derivations, we have assumed a perfect step input.
- if the input is not a perfect step (i.e., it has a finite delay or rise time), it will increase the delay of the gate
- we can use an RMS estimation to account for the non-ideal input:

$$\tau_{PHL(\text{non-ideal})}^2 = \tau_{PHL(\text{ideal, step})}^2 + \tau_{rise}^2$$

$$\tau_{PHL(\text{non-ideal})}^2 = \tau_{PHL(\text{ideal, step})}^2 + \tau_{fall}^2$$

- we can also estimate the delay of the input if we are only given its rise/fall time by using:

$$\tau_{PHL} = \frac{\tau_{rise}}{2}$$

$$\tau_{PHL} = \frac{\tau_{fall}}{2}$$



CMOS Switching Characteristics

Non-ideal Inputs

- we can apply this technique to the rise and fall times also:

$$\tau_{rise(\text{non-ideal})}^2 = \tau_{rise(\text{ideal, step})}^2 + \tau_{rise}^2$$

$$\tau_{fall(\text{non-ideal})}^2 = \tau_{fall(\text{ideal, step})}^2 + \tau_{fall}^2$$



CMOS Switching Characteristics

Designing for Constraints

- when we begin a design, we typically start with specification
- we then size the transistors to achieve the desired performance
- we saw how the sizes of the transistor effect the DC specs, specifically V_{th}
- we also need to size the transistors so that for a given load capacitance, the gate can achieve a designed delay or rise/fall time.
- we can use the expressions for delay and rise/fall time that we derived to calculate the necessary transistor sizes.



CMOS Switching Characteristics

Designing for Constraints

- the *average current* method is the simplest technique to use:

$$\tau_{PHL} = \frac{C_{load} \cdot \Delta V_{HL}}{\frac{1}{2} [i_{D-sat}(V_{in} = V_{OH}, V_{out} = V_{OH}) + i_{D-lin}(V_{in} = V_{OH}, V_{out} = V_{50\%})]}$$

$$\tau_{PHL} = \frac{C_{load} \cdot \Delta V_{HL}}{\frac{1}{2} [i_{D-sat}(V_{in} = V_{OL}, V_{out} = V_{OL}) + i_{D-lin}(V_{in} = V_{OL}, V_{out} = V_{50\%})]}$$

- in this expression, we can insert our timing spec in for τ_{PHL} or τ_{PLH}
- the RHS of the expression must evaluate to be less than or equal to the timing spec



CMOS Switching Characteristics

Designing for Constraints



- in the timing expression, notice that k_n and k_p are parameters under our control
- these parameters are in the denominator of the timing expression, meaning that as k_n and k_p increase, the delay of the circuit will decrease.
- this means that *larger = faster*
- we typically leave the lengths of the NMOS and PMOS transistors equal to each other
- we also typically set the lengths to the smallest possible dimension for a given process.
- this gives us the highest transconductance for a given *Length* and also minimizes the area.
- a given design process consists of the following steps:
 - 1) set $L_n=L_p=L_{min}$
 - 2) find the W_p/W_n ratio that will yield the desired V_{th}
 - 3) find the minimum values for W_p and W_n to achieve timing
 - 4) combine the minimum sizes and the W_p/W_n ratio to select final sizes
 - 5) round up the dimensions to give additional margin and standard sizes (i.e., 4.927um rounds up to 5um)



CMOS Switching Characteristics

Area vs. Delay


- we've seen that *larger = faster* for a given inverter
- however, we have made an assumption that the load capacitance is independent of transistor size
- we know what a portion of the load capacitance comes from the driver oxide and driver junctions
- this means that as the inverter gets larger, so does the capacitance
- this leads to a point of *diminishing returns* with regards to reducing delay

  

CMOS Switching Characteristics

Area vs. Delay


- we can look at the **Area X Delay Product** to gauge the *quality* of a design with regards to efficient area usage.
- typically we will see an inflection point which indicates the point at which increasing the size of the transistors to decrease delay is out-weighted by the negative impact of increasing the area used on the silicon.
- if a timing specifications requires an excessively large sized gate, it typically means that the process is not sufficient to meet timing.

 

CMOS Switching Characteristics

Interconnect

- one of the components in the load capacitance is the interconnect.
- the interconnect refers to the polysilicon and metal layers that are used to connect the gates together.
- as sizes on-chip shrink, we've seen that the scaling of interconnect is a big problem because the delay actually increases as you get smaller.
- in addition, the delay scales quadratically with length meaning that intra-module traces and global interconnect can create significant timing challenges.
- in modern processes, the delay of the interconnect is actually more than the switching delay of the transistors.

 

CMOS Switching Characteristics

Interconnect Modeling

- modeling of the interconnect describes the equivalent circuits we use to describe the electrical behavior of the materials.
- the type of model we use is a trade-off between accuracy and simulation time
- we typically use 1 of the 3 following models:

	Typical Uses
1) Lumped Capacitance	inter-module
2) RC network	intra-module and global
3) Transmission Line	global and off-chip



CMOS Switching Characteristics

Interconnect Modeling

- we choose the appropriate model based on the rise/fall time of the driver relative to the *prop delay* of the interconnect
- the *prop delay* (t_{prop}) is the time it takes for the wave to travel down the length of the interconnect:
- the velocity of a wave in a dielectric is given by:

$$v = \frac{c}{\epsilon_r}$$

- the *prop delay* can then be given by:

$$t_{prop} = \frac{\text{length}}{v}$$




CMOS Switching Characteristics


Interconnect Modeling

- we move between a *lumped* (C or RC) and a *distributed* (transmission line) model as follows:

 "Lumped" $\tau_{rise} < 2.5 \cdot \left(\frac{l}{v}\right)$



 "Distributed" $\tau_{rise} \geq 2.5 \cdot \left(\frac{l}{v}\right)$




CMOS Switching Characteristics

Interconnect Resistance

- resistance is based on the geometry and materials of the interconnect
 
$$R = \frac{\rho \cdot l}{A} = R_s \cdot (\# \text{ of } _ \text{ squares})$$




CMOS Switching Characteristics

Interconnect Capacitance

- capacitance depends on the surface area of the conductor, the insulating materials between the conductors, and the distance between the conductors.

$$C = \frac{\epsilon \cdot A}{l}$$

 


EELE 414 – Introduction to VLSI Design

Module #5
Page 97

CMOS Switching Characteristics

Interconnect Capacitance

- interconnect modeling becomes a complex problem due to the 3D geometries present on-chip
- we typically take a *guess* at the capacitance of the interconnect for initial simulations.
- once we start physically laying out our design, we can use the CAD tool to *extract* the actual capacitance and back annotate it into our simulation.
- we then run a new simulation with accurate capacitance models to verify timing is still met post-layout.

 


EELE 414 – Introduction to VLSI Design

Module #5
Page 98

CMOS Switching Characteristics

Interconnect Capacitance

- Cross-talk refers to the noise that is generated on a line due to capacitive coupling from neighboring lines that are switching.
- as geometries get smaller, lines are closer together so capacitance goes up.
- we can reduce cross-talk by separating the traces or inserting ground lines between the signals, but this takes area.

 

EELE 414 – Introduction to VLSI Design

Module #5
Page 99

CMOS Switching Characteristics

Elmore Delay

- when we model interconnect using RC networks, it doesn't take many branches in the net before the KVL/KCL solution for the delay gets complex.
- *Elmore Delay* is a technique to estimate the overall delay between two nodes of an RC network tree.
- in Elmore Delay, we find the equivalent RC network of the path between two nodes by:
 - summing the delay of each segment in our path-of-interest
 - we construct a set of RC networks as seen by our path-of-interest and then sum them together
 - we walk through the series resistance in our path-of-interest.
 - for each resistor node in our path-of-interest, we include RC's in our expression as follows:
 - C's NOT in our path-of-interest are included as $(R_{node} \cdot C_i)$
 - C's that ARE in our path-of-interest can't be seen if they are on the far side of a resistor in our path-of-interest
 - as we get to the end of our path-of-interest, we can see all of the downstream Capacitances past our end-node.


EELE 414 – Introduction to VLSI Design

Module #5
Page 100

CMOS Switching Characteristics

Elmore Delay

 - example: Find the expression for the equivalent RC from V_{in} to node 7:



$$\tau_{D7} = (R_1)(C_1) + (R_1 + R_2)(C_2) + (R_1 + R_2 + R_3)(C_3) + (R_1 + R_2 + R_3 + R_4)(C_4) + (R_1 + R_2 + R_3 + R_4 + R_5)(C_5) + (R_1 + R_2 + R_3 + R_4 + R_5 + R_6)(C_6) + (R_1 + R_2 + R_3 + R_4 + R_5 + R_6 + R_7)(C_7)$$

EELE 414 – Introduction to VLSI Design

Module #5
Page 101

CMOS Switching Characteristics

Dynamic Power Consumption

- in theory, a CMOS gate does not consume any Static Power because the NMOS and PMOS transistors are in the cut-off regions when driving V_{OH} or V_{OL} .
- we know what there is leakage current in cut-off, however to the first order we neglect it.
- the majority of the power is due to the charging and discharging of C_{load}
- this is called *Dynamic Power* because it is AC in nature and only occurs when the gate switches
- this current is described as:

$$i_C = C_{load} \frac{dV_{out}}{dt}$$
- since the current consumed is proportional to the number of times that the gate switches, we need to make an assumption to the number of times per second that V_{out} switches
- since we have a binary system, we can assume that the output will be a '0' 50% of the time and a '1' 50% of the time.
- we can model the voltage on V_{out} as a periodic square wave


EELE 414 – Introduction to VLSI Design

Module #5
Page 102

CMOS Switching Characteristics

- Dynamic Power Consumption

 - current will be drawn from V_{DD} and sunk into V_{SS} during a transition



CMOS Switching Characteristics

- Dynamic Power Consumption

- assuming a periodic input and output waveform, the average power dissipated by a device over one period is given as:

$$P_{avg} = \frac{1}{T} \int_0^T v(t) \cdot i(t) dt$$

- we split up the period into two sections:

$0 \rightarrow T/2$ V_{in} transitions from a 0 to a 1, the NMOS discharges C_{load}

$T/2 \rightarrow T$ V_{in} transitions from a 1 to a 0, the PMOS charges C_{load}



CMOS Switching Characteristics

- Dynamic Power Consumption

- we can now re-write our average power expression as:

$$P_{avg} = \frac{1}{T} \left[\int_0^{T/2} V_{out} \left(-C_{load} \frac{dV_{out}}{dt} \right) dt + \int_{T/2}^T (V_{DD} - V_{out}) \left(C_{load} \frac{dV_{out}}{dt} \right) dt \right]$$

$$P_{avg} = \frac{1}{T} \left[\left(-C_{load} \frac{V_{out}^2}{2} \right) \Big|_0^{T/2} + \left(V_{DD} \cdot V_{out} \cdot C_{load} - C_{load} \frac{V_{out}^2}{2} \right) \Big|_{T/2}^T \right]$$

$$P_{avg} = \frac{1}{T} \cdot C_{load} \cdot V_{DD}^2$$

$$P_{avg} = f \cdot C_{load} \cdot V_{DD}^2$$



CMOS Switching Characteristics

- Dynamic Power Consumption

- a more qualitative view of this power consumption is as follows:

Capacitance is defined as:

$$C = \frac{Q}{V}$$

Each cycle, the average current in the capacitor is:

$$I_{AVG} = \frac{Q}{T} = \frac{C \cdot V}{T}$$

Power is IV , which gives:

$$P_{AVG} = V_{AVG} \cdot I_{AVG} = V \cdot \frac{C \cdot V}{T} = \frac{1}{T} \cdot C_{load} \cdot V^2 = f \cdot C_{load} \cdot V^2$$



CMOS Switching Characteristics

- Power Delay Product (PDP)

- another *quality* measure of a design is the PDP

- this is a measure of the energy required to switch logic levels in a given period.

- qualitatively, Power x Time is:

$$P_{avg} = \frac{1}{T} \cdot C_{load} \cdot V_{DD}^2$$

$$P_{avg} \cdot \tau = C_{load} \cdot V_{DD}^2$$



CMOS Switching Characteristics

- Power Delay Product (PDP)

- as the delay goes down, the power goes up.

- the power going up is due to the increase in intrinsic junction capacitance of the driver.

- the delay reaches an -asymptotic limit as the size is increased.

- the power increases as the size is increased.


- looking at the PDP can give an estimate of when you are optimally sized to deliver energy in the most effective manner.



Ring Oscillator

Ring Oscillator

- if we connect a chain of inverters in a loop and have an ODD number of inverters, the circuit is inherently unstable.
- the circuit will *oscillate* between a 0 and 1 indefinitely.
- the frequency of the oscillation depends on the gate delay of the inverter.
- this type of circuit is commonly used to test the device delay of a given process.
- this can also be used to create a clock.
- the clock frequency of the ring oscillator is not typically controlled tight enough to be used as the system clock.

 

Super Buffer

Super Buffer

- off-chip capacitances are typically an order of magnitude larger than on-chip capacitances.
- VLSI gates that are used in logic circuitry are sized to drive other gates of comparable size.
- if these smaller gates are connected to a much larger load capacitance, they are not sized optimally.
- a gate can typically not drive a capacitance that has a much larger capacitance than its own junction capacitance.
- a *super buffer* is a circuit that consists of a series of gates, each with an increasingly larger size and drive strength.
- we define the relative size of each subsequent gate using the *optimal sizing factor* (α)
- we start with a typical logic gate and then design a subsequent stage that is larger by a factor of α
- we continue to add stages until the final capacitance that is to be driven (C_{load}) is a factor of α larger than the last stage of the *super buffer*.
- we define the number of stages in the *super buffer* as N




Super Buffer

Super Buffer

- we define C_g as the gate capacitance of the next stage.
- we define C_d as the output drain capacitance of current stage.
- we can derive an expression to find the total delay as a function of (N, α).
- this expression gives us a relationship between N and α .
- we can differentiate this expression to find the optimal scaling factor:
 
$$\alpha(\ln \alpha - 1) = \frac{C_d}{C_g}$$



Super Buffer

Super Buffer

- we first find α .
- this defines how much larger each subsequent stage is relative to its driving stage
- we continue to add stages until the final C_g that can be driven is C_{load}

