

EE 414 – Introduction to VLSI Design

Module #6 – Combinational Logic

- **Agenda**

1. Combinational Logic

- n-Input Gates & Equivalent Inverter
- AOI/OAI Logic Synthesis
- Transmission Gates
- Layout of Complex Logic

- **Announcements**


1. Read Chapter 7



CMOS Combinational Logic

- **CMOS Combinational Logic**

 - combinational logic refers to circuits with 2 or more inputs and 1 output
- the output depends on the *combination* of the input values
- we describe the logic operation of a circuit using *truth tables*
- from this, we can find a minimal Sum of Products expression using K-maps
- once we have a logic expression, we then move into the transistor-level implementation stage



CMOS Combinational Logic

- **CMOS Basic Gates**

- in CMOS, we always have:
 - a pull-up network using PMOS transistors
 - a pull-down network using NMOS transistors
- the pull-up and pull-down networks are configured in a complementary topology
- the complementary topology guarantees that when driving a '1', the pull-up network is ON and the pull-down network is OFF
- it also guarantees that when driving a '0', the pull-up network is OFF and the pull-down network is ON
- circuit topology gives us the ability to design logic functionality where transistors:
 - in series = an AND'ing function
 - in parallel = an OR'ing function



CMOS Combinational Logic

- **CMOS 2-Input NOR Gate**

- the truth table for a 2-input NOR gate is:



| V _A | V _B | V _{out} |
|----------------|----------------|------------------|
| low | low | high |
| low | high | low |
| high | low | low |
| high | high | low |



CMOS Combinational Logic

- **CMOS 2-Input NOR Gate**

PMOS Pull-Up Network

- The only time the pull-up network drives the output is when we have two 0's on the inputs.
- Since the pull-up network uses PMOS transistors (0=ON), we can say that the pull-up network is conducting if V_A AND V_B are 0.
- This implies a **series** configuration in the pull-up (PMOS) network.

NMOS Pull-Down Network


- The pull-down network is continually driving the output unless V_A AND V_B are 0.
- Since the pull-down network uses NMOS transistors (1=ON), we can say that the pull-down network is conducting if V_A OR V_B are 1.
- This implies a **parallel** configuration in the pull-down (NMOS) network.



CMOS Combinational Logic

- **CMOS 2-Input NOR Gate**

 - the transistor level implementation for the NOR gate is:



CMOS Combinational Logic

CMOS 2-Input NOR Gate

- we have already derived expressions for how to find the critical voltages for an inverter
- of specific interest is V_{th} , which we can adjust with the sizing of the transistors
- in order to analyze a more complex logic gate, we convert it into an *equivalent inverter*

Transistors in Series

- conceptually, the current flowing in series transistors needs to go through two channels, each with an equivalent resistance (or transconductance k)
- with the effective resistance doubling, we can say that the transconductance (or the ability to drive a current given an input voltage) is divided by 2
- transistors in series with the same size can be modeled as an equivalent transistor with $k_{eq}=k/2$

Transistors in Parallel


- conceptually, the current flowing in parallel transistors can conduct twice the amount of current compared to a single transistor with the same gate voltage.
- we can model this behavior with an equivalent transistor with $k_{eq}=2 \cdot k$



CMOS Combinational Logic

CMOS 2-Input NOR Gate

 - we can model a 2-Input NOR gate as an equivalent inverter as follows:



- let's use representative voltages of $V_{DD}=5v$ and $V_{th}=2.5$ to illustrate the derivation



CMOS Combinational Logic

CMOS 2-Input NOR Gate

- we can derive the switching threshold by stating that:

$$V_{in} = V_{out} = V_A = V_B = V_{th}$$

- we can begin by writing the KCL equation at the V_{out} node:

$$|I_{D,n-network}| = |I_{D,p-network}|$$

- for the NMOS, since $V_{GS,p} = V_{GS,n}$, we know that both transistors are in *saturation*


- in addition, we can state that the current at the V_{out} node is the combination of both NMOS currents

$$I_{D,n-network} = 2 \cdot I_{D,n,out}$$

$$I_{D,n-network} = 2 \cdot \left[\frac{1}{2} \cdot k_n \cdot (V_{in} - V_{T,n})^2 \right] = k_n \cdot (V_{in} - V_{T,n})^2$$

- rearranging this equation to get in terms of V_{th} , we have:
 
$$V_{th} = V_{T,n} + \sqrt{\frac{I_{D,p-network}}{k_n}}$$



CMOS Combinational Logic

CMOS 2-Input NOR Gate

- now we look at the PMOS network, which has a +2.5v drop across it.


- since both transistors are ON, we can estimate that $\sim 1.25v$ drops across each transistor:

$$V_{DS,M3} = V_{DS,M4} = -1.25V$$

- looking at M3, we know that $V_{GS,pM3} = -2.5v$ and $V_{DS,pM3} = -1.25v$ so M3 is in the *linear region*.

- looking at M4, the node between M3 and M4 is estimated to be at ~ 3.75 (i.e., $5v - 1.25v$)

 - this puts $V_{GS,pM4} = -1.25v$ and $V_{DS,pM4} = -1.25v$, which means M4 is in the *saturation region*.



CMOS Combinational Logic

CMOS 2-Input NOR Gate

- since we know the regions of operation for M3 and M4, we can write:

$$I_{DS,3in} = \frac{1}{2} \cdot k_p \cdot \left[2 \cdot (V_{GS,p} - V_{T,p}) \cdot V_{DS,p} - V_{DS,p}^2 \right]$$


- Since the PMOS current is expressed terms of I_{DS} , we can rewrite this as:

$$I_{DS,n} = I_{SD,p} = -I_{DS,p}$$

- we know that for M3, $V_{GS,p} = V_{th} - V_{DD}$. substituting this in and carrying the (-) through, in we get:

$$I_{SD,3in} = -I_{DS,3in} = -\frac{1}{2} \cdot k_p \cdot \left[2 \cdot (V_{th} - V_{DD} - V_{T,p}) \cdot V_{DS,p} - V_{DS,p}^2 \right]$$

$$I_{SD,3in} = \frac{1}{2} \cdot k_p \cdot \left[2 \cdot (V_{DD} - V_{th} - |V_{T,p}|) \cdot V_{SD,p} - V_{SD,p}^2 \right]$$

 

CMOS Combinational Logic

CMOS 2-Input NOR Gate

- M4 is in the *saturation region* so we can write the current as:

$$I_{DS,4out} = \frac{1}{2} \cdot k_p \cdot \left[(V_{GS,p} - V_{T,p})^2 \right]$$

- Again, the PMOS current can be rewritten as:

$$I_{DS,n} = I_{SD,p} = -I_{DS,p}$$

- we know that for M4:


$$V_{GS,pM4} = V_{th} - (V_{DD} - V_{SD3})$$

$$V_{DS,pM4} = V_{th} - (V_{DD} - V_{SD3})$$

- which gives the M4 current as:

$$I_{SD,4out} = -I_{DS,4out} = -\frac{1}{2} \cdot k_p \cdot (V_{th} - V_{DD} + V_{SD3} - V_{T,p})^2$$

$$I_{SD,4out} = \frac{1}{2} \cdot k_p \cdot (V_{DD} - V_{th} - |V_{T,p}| - V_{SD3})^2$$

 

CMOS Combinational Logic

CMOS 2-Input NOR Gate

- Now we can relate the drain currents knowing that $I_{Dn} = I_{Dp} = I_{Dn}$ giving a 2nd equation relating V_{in} to I_{Dn} .


$$V_{DD} - V_{in} - |V_{T,p}| = 2 \sqrt{\frac{I_{Dn}}{k_p}}$$

- combining this with our previous expression we get:

$$V_{in}(NOR2) = \frac{V_{T,p} + \frac{1}{2} \sqrt{\frac{1}{k_p} (V_{DD} - |V_{T,p}|)}}{1 + \frac{1}{2} \sqrt{\frac{1}{k_p}}}$$

- or...

$$V_{in}(NOR2) = \frac{V_{T,p} + \sqrt{\frac{1}{4 \cdot k_p} (V_{DD} - |V_{T,p}|)}}{1 + \sqrt{\frac{1}{4 \cdot k_p}}}$$

 

CMOS Combinational Logic


CMOS 2-Input NOR Gate

- in an equivalent inverter model, to get $V_{in} = V_{DD}/2$, we can use:

$$k_p = \frac{k_n}{k_p} = 1 = \frac{2 \cdot k_n}{k_p/2}$$

$$k_p = 4 \cdot k_n$$

 - note that the PMOS series network has to be sized larger in order to overcome the voltage drop across each stage.




CMOS Combinational Logic

CMOS N-Input NOR Gate

- to expand the NOR gate to N-inputs,

 - add more PMOS transistors in series in the Pull-up Network
- add more NMOS transistors in parallel in the Pull-down Network



CMOS Combinational Logic

CMOS N-Input NOR Gate

- our V_{in} expression for an N-input NOR gate becomes:

$$V_{in}(NOR) = \frac{V_{T,p} + \frac{1}{N} \sqrt{\frac{1}{k_p} (V_{DD} - |V_{T,p}|)}}{1 + \frac{1}{N} \sqrt{\frac{1}{k_p}}}$$

- and our rule of thumb for an ideal symmetric equivalent inverter becomes:

$$k_p = \frac{k_n}{k_p} = 1 = \frac{N \cdot k_n}{k_p/N}$$

$$k_p = N^2 \cdot k_n$$




CMOS Combinational Logic

CMOS N-Input NOR Gate


- an equivalent network for **series-connected** transistors with the same sizes:
 
$$\left(\frac{W}{L}\right)_{\text{equivalent}} = \frac{1}{\sum \left(\frac{1}{\left(\frac{W}{L}\right)_i}\right)}$$




- an equivalent network for **parallel-connected** transistors with the same sizes:
 
$$\left(\frac{W}{L}\right)_{\text{equivalent}} = \sum \left(\frac{W}{L}\right)_i$$



CMOS Combinational Logic

CMOS 2-Input NOR Gate Layout

 

CMOS Combinational Logic

CMOS 2-Input NAND Gate

- the truth table for a 2-input NAND gate is:



| V_A | V_B | V_{out} |
|-------|-------|-----------|
| low | low | high |
| low | high | high |
| high | low | high |
| high | high | low |



CMOS Combinational Logic

CMOS 2-Input NAND Gate

PMOS Pull-Up Network

- The pull-up network is continually driving the output unless V_A AND V_B are 1.
- Since the pull-up network uses PMOS transistors (0=ON), we can say that the pull-up network is conducting if V_A OR V_B are 0.
- This implies a **parallel** configuration in the pull-up (PMOS) network.

NMOS Pull-Down Network


- The only time the pull-down network drives the output is when we have two 1's on the inputs
- This means the pull-down network is conducting only when V_A AND V_B are 1.
- This implies a **series** configuration in the pull-down (NMOS) network.



CMOS Combinational Logic

CMOS 2-Input NAND Gate

 
- the transistor level implementation for the NAND gate is:



CMOS Combinational Logic

CMOS 2-Input NAND Gate

 - we can model the 2-Input NAND gate as an equivalent invert as follows:




CMOS Combinational Logic

CMOS 2-Input NAND Gate

- the switching threshold for the 2-input NAND gate is:

$$V_{th}(NAND) = \frac{V_{tp} + 2 \sqrt{\frac{1}{k_s} (V_{DD} - |V_{tp}|)}}{1 + 2 \sqrt{\frac{1}{k_s}}}$$

 

CMOS Combinational Logic

CMOS 2-Input NAND Gate

- in an equivalent inverter model, to get $V_{in} = V_{DD}/2$, we can use:

$$k_s = \frac{k_n}{k_p} = 1 = \frac{k_p/2}{k_p}$$

$$4 \cdot k_p = k_n$$



- note that the NMOS series network has to be sized larger in order to overcome the voltage drop across each series stage.




CMOS Combinational Logic

CMOS N-Input NAND Gate

- to expand the NAND gate, we

 - add more PMOS transistors in parallel in the Pull-up Network
- add more NMOS transistors in series in the Pull-down Network



CMOS Combinational Logic

CMOS N-Input NAND Gate

- our V_{th} expression for an N-input NAND gate becomes:

$$V_{th}(NAND) = \frac{V_{tp} + N \sqrt{\frac{k_p}{k_n}} (V_{DD} - |V_{tp}|)}{1 + N \sqrt{\frac{k_p}{k_n}}}$$

$$V_{th}(NAND) = \frac{V_{tp} + \sqrt{\frac{N^2}{k_p}} (V_{DD} - |V_{tp}|)}{1 + \sqrt{\frac{N^2}{k_p}}}$$

- and our rule of thumb for an ideal symmetric equivalent inverter becomes:


$$k_p = \frac{k_n}{N} = 1 = \frac{k_p / N}{N \cdot k_p}$$

$$N^2 \cdot k_p = k_n$$



CMOS Combinational Logic

CMOS 2-Input NAND Gate Layout

 

CMOS Combinational Logic

Complex CMOS Logic Circuits

- we can implement any logic functions using NANDs, NORs, and INV's.

- however, the timing and area of the standard SOP approach can be improved further by creating the entire logic function in one circuit.

- we can design a complex function by:

1) Creating the NMOS pull-down network of F' where:

- an OR is performed using parallel connected NMOS's
- an AND is performed using series connected NMOS's

NOTE: this is an NMOS pull-down network so the logic function must be in an F' form (or a dual of F).

NOTE: these rules can be used in a *nested* configuration to form any logic function

2) Creating the PMOS pull-up network to be the *complement* of the pull-down network




CMOS Combinational Logic

Complex CMOS Logic Circuits

- an example of the NMOS pull-down network synthesis is:

$$F = A \cdot (D + E) + B \cdot C$$

 - D+E is created with two NMOS's in parallel
- A(D+E) puts an NMOS in series with the (D+E) network
- the entire A(D+E) network is in parallel with the BC network
- the BC network is created with two series NMOS's



CMOS Combinational Logic

Complex CMOS Logic Graphs


- the *complementary* PMOS network is created with a technique called a *dual pull-up/down graph*

- this is a graphical way to create the PMOS network for a given NMOS pull-down circuit.

- we first create the *pull-down graph* by representing:

 - 1) each NMOS transistor as an *edge* (i.e., a line), and
- 2) each node as a *vertex* (i.e., a dot)


- we orient the *pull-down graph* in the same orientation as the NMOS circuit (V_{DD} on top, V_{SS} on bottom)



CMOS Combinational Logic

Complex CMOS Logic Graphs

 - next, we create the **dual pull-up graph** on top of the pull-down graph.
- we orient the pull-up graph with V_{DD} on the left and V_{out} on the right.
- we create the pull-up graph using the rules:
 - 1) a new vertex is created within each confined area of the pull-down graph
 - 2) each vertex is connected by an edge which crosses each edge of the pull-down graph




CMOS Combinational Logic

Complex CMOS Logic Graphs

- now we can separate the graphs and synthesize the PMOS pull-up network

 Remember that: an edge (a line) = a transistor
a vertex (a dot) = a node



CMOS Combinational Logic

AOI / OAI CMOS Logic

- we classify the common types of logic expression forms as:

AOI - AND-OR-INVERT

- this corresponds to a Sum-of-Products logic expression form:

$$\text{ex) } F = \overline{A \cdot B + B' \cdot C + C' \cdot D}$$

OAI - OR-AND-INVERT

- this corresponds to a Products-of-Sums logic expression form:

$$\text{ex) } F = \overline{(A+B) \cdot (B'+C) \cdot (C'+D)}$$

- Note that we have the *Invert* portion in these forms so that we can directly synthesize the NMOS pull-down network.


- we can create this form of a logic expression using *DeMorgan's Theorem*



CMOS Combinational Logic

AOI / OAI CMOS Logic

 - AOI and OAI logic expressions can create standardized layouts due to their symmetry



CMOS Combinational Logic

Complex CMOS Logic Graphs (XOR)


- let's design a 2-input XOR gate.

- 1) we first find the traditional SOP expression
- 2) we then manipulate it into an OAI or AOI form so that the pull-down network can be directly synthesized

Truth Table

| AB | OUT |
|----|-----|
| 00 | 0 |
| 01 | 1 |
| 10 | 1 |
| 11 | 0 |

K-Map

 

Logic Manipulation

$$\text{Out} = A'B + AB'$$

$$\text{Out} = \overline{A'B} + \overline{AB'}$$

$$\text{Out} = \overline{(A'B) \cdot (AB')}$$

$$\text{Out} = \overline{(A+B) \cdot (A+B')}$$

$$\text{Out} = \overline{(A+B) \cdot (A'+B)}$$




CMOS Combinational Logic

Complex CMOS Logic Graphs (XOR)

 - 3) We directly synthesize the pull-down network and create its equivalent pull-down graph
- 4) We then create the dual pull-up graph on top of the pull-down graph


- insert a vertex in each enclosed region of the pull-down graph (vertex=nodes)
- connect each vertex such that each pull-down is crossed by one pull-up edge (edge=PMOS)



CMOS Combinational Logic

Complex CMOS Logic Graphs (XOR)

 5) we then unfold the dual pull-up/down graph and directly synthesize the pull-up network



CMOS Combinational Logic

Complex CMOS Logic Equivalent Inverters

- to calculate the performance of a complex Logic Circuit, we need create an **equivalent inverter**
- we then use our equations for V_{th} , τ_{pHL} , and τ_{pLH} on the equivalent transconductance values
- we know that

- an equivalent network for series-connected transistors with the same sizes:

$$\left(\frac{W}{L}\right)_{equivalent} = \frac{1}{\sum \left(\frac{W}{L}\right)_N}$$

- an equivalent network for parallel-connected transistors with the same sizes:


$$\left(\frac{W}{L}\right)_{equivalent} = \sum \left(\frac{W}{L}\right)_N$$



CMOS Combinational Logic

Complex CMOS Logic Equivalent Inverters

- for example:

 

CMOS Combinational Logic

Complex CMOS Logic Stick-Diagrams

- a **stick diagram** is a graphical way to map a complex CMOS circuit into a layout diagram
- in a stick diagram, draw the general layout configuration that will be used in order to figure out how the diffusion layer contacts are placed.
- a stick diagram has:


- diffusion regions as rectangles
- metal traces are lines
- contacts are circles
- polysilicon inputs are columns

- the intent of a **stick diagram** is to figure out how the inputs and outputs are connected to the diffusion regions

- we don't put any size information in this diagram

- we typically sketch this out with *pencil-and-paper* prior to going into the tool

 - planning ahead can save a lot of time in the tool




CMOS Combinational Logic

Transmission Gate (Pass Gate)

- A Transmission Gate (T-gate or TG or *pass gate*) is a bi-directional switch made up of an NMOS and PMOS in parallel.

- a control signal is connected to the gate of the NMOS (C) and its complement is sent to the gate of the PMOS (C')

 - The T-gate is a bidirectional switch between A and B which is controlled by C



CMOS Combinational Logic

Transmission Gate (Pass Gate)

- When the control signal is HIGH (V_{DD}):

- both transistors are turned on
- a low resistance path exists between A and B

- When the control signal is LOW (0v)

- both transistors are off
- the T-gate looks like an open circuit



- this type of operation is commonly used in bus situations where only one gate can drive the bus line at the same time


- T-gates are put on the output of each gate on the bus. The circuit that drives will use a T-gate to connect to the bus with a low impedance path. All other circuits that aren't driving will switch their T-gates to be a high-impedance.



CMOS Combinational Logic

Transmission Gate (Pass Gate)

- When the T-gate is on, the regions of operation of the transistors will depend on V_{in} and V_{out}
- let's say we drive $V_{in}=V_{DD}$ and initially $V_{out}=0V$
- As V_{out} moves from 0v to V_{DD} , the regions of operation for the transistors are as follows:

 

EELE 414 – Introduction to VLSI Design

Module #6
Page 43

CMOS Combinational Logic


Transmission Gate (Pass Gate)

- we typically model the T-gate as a switch with an equivalent resistance
- at any point, the equivalent resistance is given by:

$$R_{eq,p} = \frac{V_{DD} - V_{out}}{I_{DS,p}}$$

$$R_{eq,n} = \frac{V_{out} - V_{DD}}{I_{DS,n}}$$

$$R_{eq,TG} = R_{eq,p} \parallel R_{eq,n}$$

 

EELE 414 – Introduction to VLSI Design

Module #6
Page 44

CMOS Combinational Logic

Transmission Gate (Pass Gate)

- as the PMOS and NMOS transistors turn on/off, they keep the overall T-gate resistance LOW

Region 1

$$R_{eq,n1} = \frac{(V_{DD} - V_{out})}{\frac{1}{2}k_n(V_{DD} - V_{out} - V_{Tn})^2}$$

$$R_{eq,p1} = \frac{(V_{DD} - V_{out})}{\frac{1}{2}k_p(V_{DD} - |V_{Tp}|)^2}$$

Region 2

$$R_{eq,n2} = \frac{(V_{DD} - V_{out})}{\frac{1}{2}k_n(V_{DD} - V_{out} - V_{Tn})^2}$$

$$R_{eq,p2} = \frac{(V_{DD} - V_{out})}{\frac{1}{2}k_p[2(V_{DD} - |V_{Tp}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2]}$$

Region 3

$$R_{eq,n3} = HIGH$$

$$R_{eq,p3} = \frac{(V_{DD} - V_{out})}{\frac{1}{2}k_p[2(V_{DD} - |V_{Tp}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2]}$$




EELE 414 – Introduction to VLSI Design

Module #6
Page 45

CMOS Combinational Logic

Transmission Gate (Pass Gate)

- as the PMOS and NMOS transistors turn on/off, they keep the overall T-gate resistance LOW

 


EELE 414 – Introduction to VLSI Design

Module #6
Page 46

CMOS Combinational Logic

Transmission Gate (Pass Gate)

- T-gates can be used to create combinational logic

 


EELE 414 – Introduction to VLSI Design

Module #6
Page 47

CMOS Combinational Logic

Transmission Gate (Pass Gate)

- complex logic using T-gates has an advantage when it comes to layout because of the symmetry of the PMOS and NMOS. One N-well can be used for all PMOS's

 

EELE 414 – Introduction to VLSI Design

Module #6
Page 48