


## EELE408 Photovoltaics

### Lecture 12: Solar Cell Sensitivities


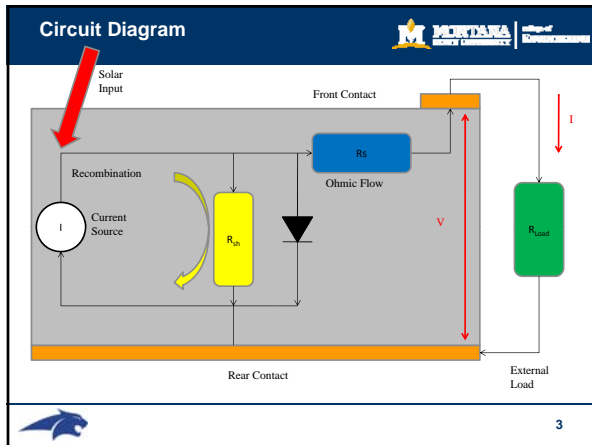
Dr. Todd J. Kaiser  
tjkaiser@ece.montana.edu

Department of Electrical and Computer Engineering  
Montana State University - Bozeman




### Effect of Parasitic Resistance

- Resistance effects in solar cells reduce the efficiency of the solar cell by dissipating power in the resistances.
- The resistances are included in the circuit model by adding a resistor in parallel with the diode called the **shunt resistance** and a resistor in series with the diode called the **series resistance**
- The key impact of parasitic resistance is to reduce the fill factor

### Series Resistance

- Series resistance caused by the movement of current through
  - The semiconducting layers forming the emitter and base
  - The contact resistance between the metal and silicon
  - The resistance of the top and rear metal layer
- Excessively high series resistance can reduce the short circuit current as well as reduce the fill factor
- Particular problem at high current densities under concentrated light




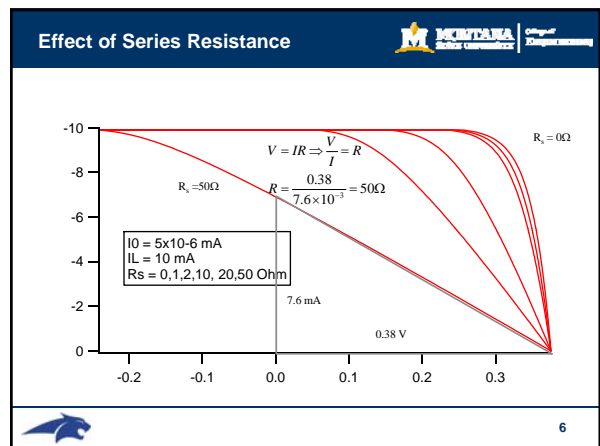
### Series Resistance

$$I = I_0 \left[ \exp\left(\frac{qV}{kT}\right) - 1 \right] - I_L$$

Add voltage drop across series resistor

$$= I_0 \left[ \exp\left(\frac{q(V - IR_s)}{kT}\right) - 1 \right] - I_L$$

$$\frac{I + I_L}{I_0} = \exp\left(\frac{q(V - IR_s)}{kT}\right) - 1 \Rightarrow \ln\left[\frac{I + I_L}{I_0}\right] = \frac{q(V - IR_s)}{kT}$$

$$V = V_t \ln\left[\frac{I + I_L}{I_0}\right] + IR_s$$



### Series Resistance Impact on Fill Factor

Max power – power lost in resistor

$$P'_{mp} \approx P_{mp} - I_{mp}^2 R_s = V_{mp} I_{mp} - I_{mp}^2 R_s$$

$$\approx V_{mp} I_{mp} \left( 1 - \frac{I_{mp}}{V_{mp}} R_s \right) = P_{mp} \left( 1 - \frac{1}{R_{ch}} R_s \right)$$

$$P'_{mp} \approx P_{mp} (1 - r_s) \quad r_s = \frac{R_s}{R_{ch}} \quad \text{Normalized series Resistance}$$

Assume the open circuit voltage and short circuit current are not perturbed significantly

$$V'_{oc} I'_{sc} FF' \approx V_{oc} I_{sc} FF (1 - r_s)$$

$$FF' = FF (1 - r_s)$$

$$FF' = FF (1 - 1.1 r_s) + \frac{r_s^2}{5.4}$$

Second Order Empirical Equation  
 $r_s < 0.4$


### Shunt Resistance

- Significant power losses due to shunt resistance are typically due to manufacturing defects rather than poor cell design
- Creates an alternative current path
  - Recombination
  - Junction shorting
- Reduces current flow through solar cell that reduces voltage of solar cell
- Severe at low light levels since less photogenerated current
- At low voltages shunt resistance has larger effect

### Shunt Resistance

$$I + I_L - I_d - \frac{V}{R_{sh}} = 0$$

← Add current through shunt resistor
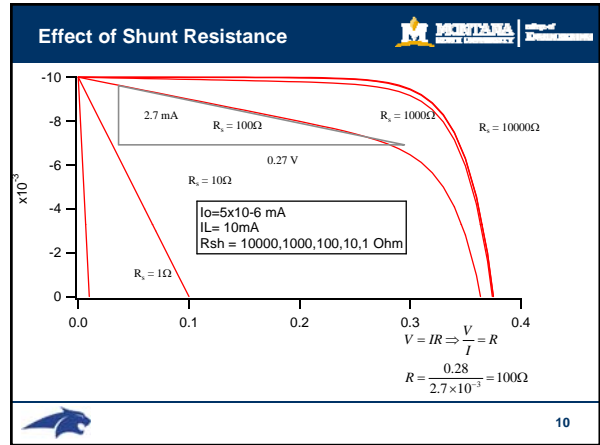
$$I = -I_L + I_0 \exp\left(\frac{qV}{kT}\right) + \frac{V}{R_{sh}}$$


### Shunt Resistance Impact on Fill Factor

Max power – power lost in resistor

$$P'_{mp} \approx P_{mp} - \frac{V_{mp}^2}{R_{sh}} = V_{mp} I_{mp} - \frac{V_{mp}^2}{R_{sh}}$$

$$\approx V_{mp} I_{mp} \left( 1 - \frac{V_{mp}}{I_{mp} R_{sh}} \right) = P_{mp} \left( 1 - \frac{R_{ch}}{R_{sh}} \right)$$

$$P'_{mp} \approx P_{mp} (1 - r_{sh}) \quad r_{sh} = \frac{R_{ch}}{R_{sh}} \quad \text{Normalized shunt Resistance}$$

Assume the open circuit voltage and short circuit current are not perturbed significantly

$$V'_{oc} I'_{sc} FF' \approx V_{oc} I_{sc} FF \left( 1 - \frac{1}{r_{sh}} \right)$$

$$FF' = FF \left( 1 - \frac{1}{r_{sh}} \right)$$

$$FF' = FF \left[ 1 - \frac{1}{r_{sh}} \right] + \frac{r_{sh}^2}{5.4}$$

Empirical Equation  
 $r_{sh} > 0.4$

### Impact of Both Parasitic Resistances


$$I = I_0 \left[ \exp\left(\frac{qV}{kT}\right) - 1 \right] - I_L$$

$$= I_0 \left[ \exp\left(\frac{q(V - IR_s)}{kT}\right) - 1 \right] - I_L + \frac{V - IR_s}{R_{sh}}$$

$$FF' = FF \left\{ 1 - \frac{v_{oc} + 0.7 FF}{v_{oc} r_{sh}} \right\} \quad FF' = FF (1 - 1.1 r_s) + \frac{r_s^2}{5.4}$$

$$FF' = FF \left[ (1 - 1.1 r_s) + \frac{r_s^2}{5.4} \right] \left[ 1 - \frac{V_{oc} + 0.7 FF}{V_{oc} r_{sh}} \left[ (1 - 1.1 r_s) + \frac{r_s^2}{5.4} \right] \right]$$

### Temperature Dependence ?



Solar Cells loose efficiency with the increase in temperature  
Colder is better


13

### Temperature effect

- Increased temperature increase electron energy in material
- Less energy is needed to break bonds
- Less bond energy implies smaller band gap
- Therefore increased temperature reduces the band gap
- The open circuit voltage is impacted the most reducing it

14

### Effect of Temperature

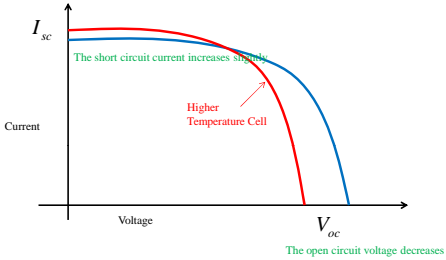

The short circuit current increases slightly  
Higher Temperature Cell  
The open circuit voltage decreases

15

### Temperature Sensitivity

- The open circuit voltage decreases with temperature because of the temperature dependence on  $I_0$
- Look at one side of a p-n junction:
- Most significant effect is the intrinsic concentration (squared)

$$n_i^2 = 4 \left( \frac{2\pi kT}{h^2} \right)^3 (m_e^* m_h^*)^{\frac{3}{2}} e^{-\frac{E_g}{kT}} \Rightarrow BT^3 e^{-\frac{E_g}{kT}}$$

$$I_0 = qA \frac{Dn_i^2}{LN_D}$$

$$I \propto n_i^2 \Rightarrow BT^\gamma e^{-\frac{E_g}{kT}}$$

16

### Temperature Dependence of Voc

- For silicon solar cells  $I_0$  doubles for every 10°C increase in temperature

$$V_{oc} = \frac{kT}{q} \ln \left( \frac{I_{sc}}{I_0} \right) = \frac{kT}{q} [\ln(I_{sc}) - \ln(I_0)] = \frac{kT}{q} \ln(I_{sc}) - \frac{kT}{q} \ln \left[ BT^\gamma e^{-\frac{E_g}{kT}} \right]$$

$$= \frac{kT}{q} \left[ \ln(I_{sc}) - \ln(B) - \gamma \ln(T) + \frac{qV_0}{kT} \right]$$

$$\frac{dV_{oc}}{dT} = \frac{V_{oc} - V_g}{T} - \gamma \left( \frac{k}{q} \right) \Rightarrow -2mV/^\circ C \Rightarrow \frac{1}{V_{oc}} \frac{dV_{oc}}{dT} = -0.003/^\circ C$$

17

### Temperature Dependence of Silicon Solar Cells

$$\frac{1}{V_{oc}} \frac{dV_{oc}}{dT} = -0.003/^\circ C$$

$$\frac{1}{I_{sc}} \frac{dI_{sc}}{dT} = +0.0006/^\circ C$$

$$\frac{1}{FF} \frac{d(FF)}{dT} \approx \frac{1}{6} \left[ \frac{1}{V_{oc}} \frac{dV_{oc}}{dT} - \frac{1}{T} \right] \approx -0.0015/^\circ C$$

$$\frac{1}{P_m} \frac{dP_m}{dT} = \frac{1}{P_m} \frac{d(V_{oc} I_{sc} FF)}{dT} = \frac{1}{V_{oc}} \frac{dV_{oc}}{dT} + \frac{1}{I_{sc}} \frac{dI_{sc}}{dT} + \frac{1}{FF} \frac{d(FF)}{dT}$$

$$= -(0.004 - 0.005)^\circ C$$

18

**Effects of Light Intensity**

- Light intensity impacts all solar cell parameters
- The light intensity on the solar cell is called the number of suns
- 1 sun corresponds to AM1.5 or 1kW/m<sup>2</sup>
- 10 kW/m<sup>2</sup> would be 10 suns or 10X
- Solar cells design to use concentrated sunlight are called **concentrators**

19

**Effect of Light Intensity**

The short circuit current increases linearly with light intensity

Fill Factor may reduce if the series resistance is high

The open circuit voltage increases logarithmically with light intensity

20

**Concentrator**

- Designed to operate at greater than 1 sun
- Sun light is focused or guided by optical elements
- Efficiency benefits stem from the logarithmic dependence of the open circuit voltage
- Can be offset by increases in series resistance and increased operation of temperature

$$V'_{oc} = \frac{nkT}{q} \ln\left(\frac{XI_{sc}}{I_0}\right) = \frac{nkT}{q} \left[ \ln\left(\frac{I_{sc}}{I_0}\right) + \ln(X) \right] = V_{oc} + \frac{nkT}{q} \ln(X)$$

21

**Low Intensity Light**

- Light intensities varies with time of day from 0-1kW/m<sup>2</sup>
- At low levels the shunt resistance value becomes more important
- As light intensity decreases, bias point and current decreases and equivalent resistance approaches shunt resistance
- Fraction of current through shunt resistance increases → fractional power loss increases
- A solar cell with a high shunt resistance retains a greater fraction of its original power under cloudy or low intensity conditions

22