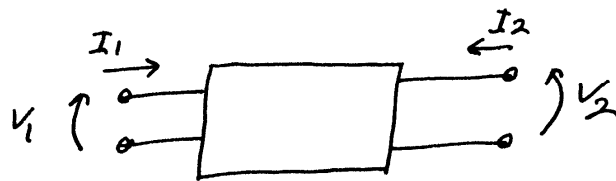


EE 43308 - Lecture 15

Microwave Network Analysis $\rightarrow$ Chapter 4
 $\rightarrow$ the N-port model

Consider a 2-port Network:

we have an input V_1 and I_1 ,
 and an output V_2 and I_2



we may represent this by Z, Y, H, E , or S parameters, $\rightarrow$ (and there are more!)

Z parameters:

$$\begin{aligned} V_1 &= Z_{11} I_1 + Z_{12} I_2 \\ V_2 &= Z_{21} I_1 + Z_{22} I_2 \end{aligned} \quad \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \Rightarrow \text{output open ckt}$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} \Rightarrow \text{"transfer impedance"}$$

13308-15

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} \quad Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$

H parameters $\rightarrow$ "Hybrid" parameters.

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

used for transistors.

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} \quad \text{input impedance}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} \quad \underbrace{\left. \frac{I_2}{I_1} \right|_{V_2=0}}_{\text{transistor current gain}} = \beta$$

Similar derivations for Y & C

Problem at microwave frequencies $\rightarrow$

we can't get good shorts or opens $\Rightarrow$

shorts & opens cause reflected waves $\Rightarrow Z(l)$


& the reference plane is frequency dependent

43308-15

the solution is to use S-parameters.

"Scattering" parameters are measured with matched source & load $\rightarrow$ eliminates reflections

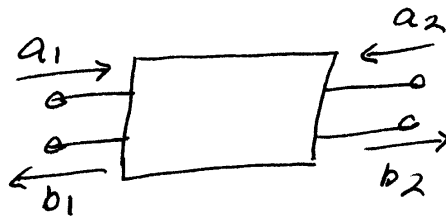Consider a 2 port with normalized waves a_1, a_2 incident, and b_1, b_2 reflected



the equations are:

$$b_1 = S_{11} a_1 + S_{12} a_2$$

$$b_2 = S_{21} a_1 + S_{22} a_2$$

a_i^2 = input power

b_i^2 = reflected power.

this may be expanded to an n-port network.

4


43308-15

$$\begin{bmatrix} b_1 \\ \vdots \\ b_n \end{bmatrix} = \begin{bmatrix} S_{11} & \dots & S_{1n} \\ \vdots & & \vdots \\ S_{m1} & \dots & S_{mn} \end{bmatrix} \begin{bmatrix} a_1 \\ \vdots \\ a_n \end{bmatrix}$$

$$b_n = \sum_k S_{nk} a_k.$$

output n

example - A microwave Circulator.

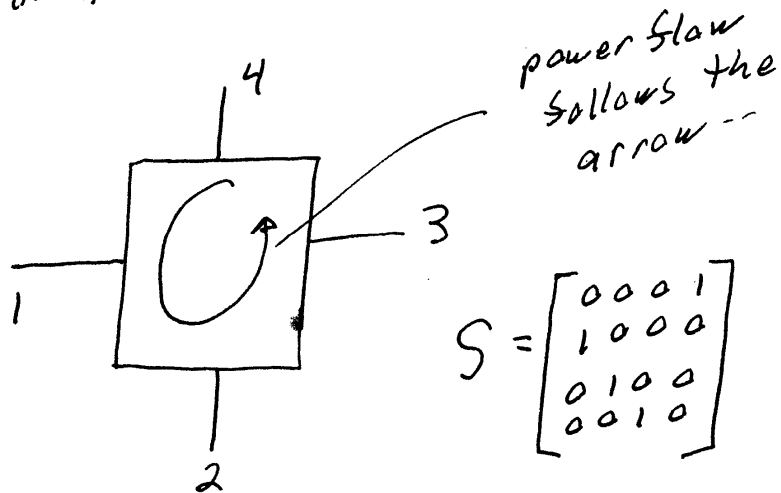

note: we have referred to V^+ & V^- as the peak voltages.
as input voltages.


$$P_i = a_i^2 = \frac{(V_i^+)^2}{2Z_0} \Rightarrow a_i = \frac{V_i^+}{\sqrt{2Z_0}}$$

43308-15

some texts show $a_i = \frac{V_i^+}{\sqrt{Z_0}}$ where

V_i^+ is the rms sine wave voltage. We will use this

S-parameters + power gains:

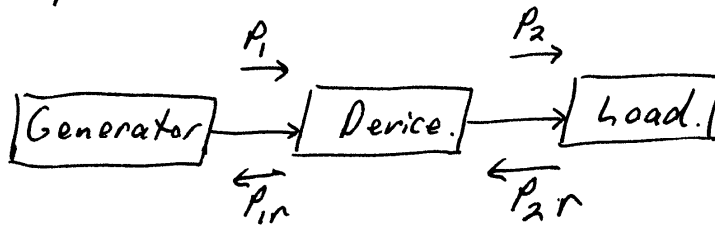

Transducer gain $G_T = |S_{21}|^2 = \frac{\text{Power delivered}}{\text{Power available}}$

(also called insertion gain.) $= \frac{P_2 - P_{2r}}{P_1}$

Power Gain

$$G_P = \frac{|S_{21}|^2}{1 - |S_{11}|^2} = \frac{\text{Power delv to load}}{\text{Power available from gen}} = \frac{P_2 - P_{2r}}{P_1 - P_{1r}}$$

Available gain

$$G_A = \frac{|S_{21}|^2}{1 - |S_{22}|^2} = \frac{\text{Power available at output}}{\text{Power available at gener}} = \frac{P_2}{P_1}$$

EE43308-15

max available gain.

$$MAG = \frac{|S_{21}|^2}{(1 - |S_{11}|^2)(1 - |S_{22}|^2)}$$


$$= \frac{\text{Power available at output}}{\text{power into the input port}} = \frac{P_2}{P_i - P_{ir}}$$

unilateral Power Gain.

$$U = \frac{|S_{11}| |S_{22}| |S_{12} S_{21}|}{(1 - |S_{11}|^2)(1 - |S_{22}|^2)}$$

 $f_{max} \Rightarrow$ point where $U = 1$ $f_T \Rightarrow$ point where $G_T = 1$


more on these gains later in the course.

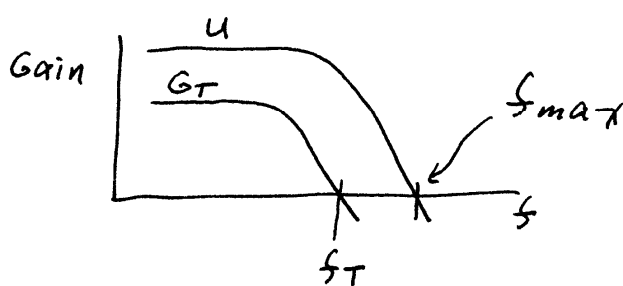

$$\begin{aligned} 1 - |S_{11}|^2 &\Rightarrow \text{input mismatch loss} \\ 1 - |S_{22}|^2 &\Rightarrow \text{output mismatch loss} \\ \frac{1}{1 - |S_{11}|^2} &\Rightarrow \text{gain increase} \end{aligned}$$

<end lecture 15>

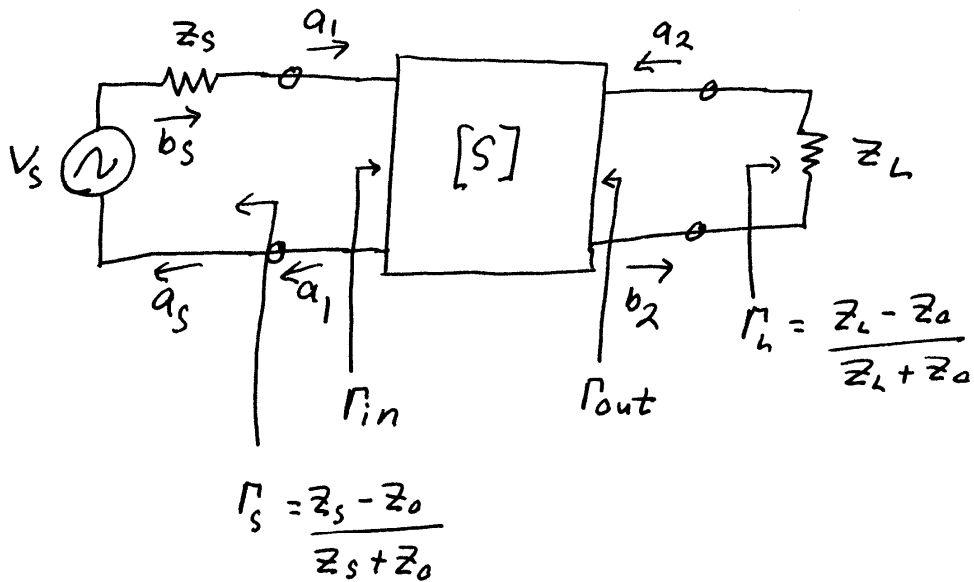43308-16 Lecture 16 → S-parameters
in a circuit:



$$\Gamma_{in} = S_{11} + \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L} \quad \Gamma_{out} = S_{22} + \frac{S_{12} S_{21} \Gamma_s}{1 - S_{11} \Gamma_s}$$

input
impedance
change due
to Γ_L & S_{12}
↳ reverse gain.

Unilateral 2-port ⇒ $S_{12} = 0$

then $\Gamma_{in} = S_{11}$ ⇒ Load does not
change the input
impedance.

43308-16

2.


it can be shown that

$$G_p = \underbrace{\frac{1 - |\Gamma_s|^2}{|1 - S_{11}\Gamma_s|^2}}_{\text{input miss-match Loss}} \underbrace{|S_{21}|^2 \frac{1}{1 - |\Gamma_{out}|^2}}_{\text{output miss-match Loss}}$$

(power gain.)

Voltage gain.

$$A_v = \frac{V_{out}}{V_{in}} = \frac{S_{21}(1 + \Gamma_L)}{(1 - S_{22}\Gamma_L) + S_{11}(1 - S_{22}\Gamma_L) + S_{12}S_{21}\Gamma_L}$$

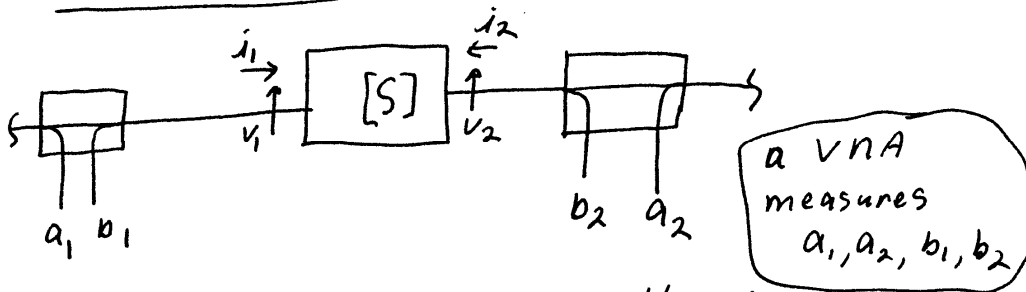Let $v_i^+ + v_i^-$ be rms voltages.

$$V_i = v_i^+ + v_i^- \quad (1)$$

$$i_i = i_i^+ - i_i^- = \frac{v_i^+}{Z_0} - \frac{v_i^-}{Z_0} \quad (2)$$

43308-16

3

$$a_1 = \frac{V_1^+}{\sqrt{Z_0}} = j_1^+ \sqrt{Z_0} \Rightarrow a_1^2 = \frac{(V_1^+)^2}{Z_0} = (j_1^+)^2 Z_0 \Rightarrow \text{input power.}$$

same approach for other terms.

Can show:

$$a_1 = \frac{1}{2\sqrt{Z_0}} [V_1 + Z_0 j_1] \quad (3)$$

$$b_1 = \frac{V_1^-}{\sqrt{Z_0}} = j_1^- \sqrt{Z_0} = \frac{1}{2\sqrt{Z_0}} [V_1 - \overset{\text{minus}}{Z_0 j_1}] \quad (4)$$

$$a_2 = \frac{V_2^+}{\sqrt{Z_0}} = j_2^+ \sqrt{Z_0} = \frac{1}{2\sqrt{Z_0}} [V_2 + Z_0 j_2] \quad (5)$$

$$b_2 = \frac{V_2^-}{\sqrt{Z_0}} = j_2^- \sqrt{Z_0} = \frac{1}{2\sqrt{Z_0}} [V_2 - Z_0 j_2] \quad (6)$$

using (3), (4):

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} = \frac{V_2 - j_1 Z_0}{V_1 + j_1 Z_0} = \frac{Z_1 - Z_0}{Z_1 + Z_0}$$

$$\Rightarrow \text{so } S_{11} = \Gamma_1 \text{ with } Z_L = 50, (\text{ie } \Gamma_L = 0)$$

This is how a VNA works!

Properties of the Scattering Matrix

- ▷ Reciprocal Networks: Passive networks containing only linear elements including resistors, capacitors, inductors and transformers.

$$\rightarrow Z_{mn} = Z_{nm}$$

$$\rightarrow S_{ij} = S_{ji} \quad \text{for } i \neq j$$

- ▷ Lossless Networks: A passive network containing no resistors.

Under the lossless case, the $[S]$ is unitary. That is,

$$\sum_{i=1}^N S_{ij} S_{ij}^* = 1 \quad j = 1, 2, \dots, N$$

In words: the sum of the products of each term of any one column (or row if network is reciprocal) multiplied by its own conjugate is unity.

For a two-port:

Column 1

$$S_{11} S_{11}^* + S_{21} S_{21}^* = 1$$

Column 2

$$S_{12} S_{12}^* + S_{22} S_{22}^* = 1$$


If the lossless network is reciprocal

$$S_{12} = S_{21} \quad |S_{11}| = |S_{22}|$$

$$|S_{11}|^2 + |S_{21}|^2 = 1$$


While the $[S]$ is the predominant descriptor of microwave networks, other matrices such as the impedance, admittance, and transmission matrix are also used.

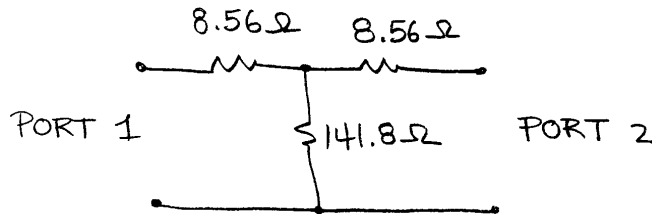Evaluation of S-parameters - ex. 4.4 Pozar



With
50Ω ports.

$$S_{11} = \frac{V_1^-}{V_1^+} \Big|_{\text{PORT 2 matched}} = \Gamma_1 = \frac{Z_{in1} - Z_0}{Z_{in1} + Z_0}$$

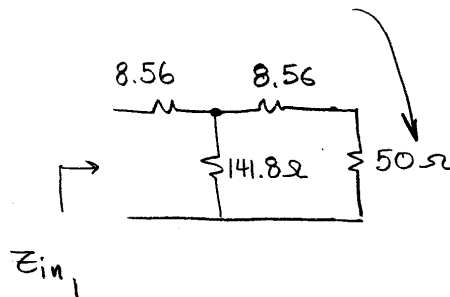


$$Z_{in1} = 8.56 + 141.8 \parallel 50 = 8.56 + 41.44 = 50\Omega$$

$$S_{11} = \frac{50 - 50}{50 + 50} = 0$$

By symmetry $S_{22} = S_{11} = 0$

$$S_{21} = \frac{V_2^-}{V_1^+} \Big|_{\text{PORT 2 matched}}$$

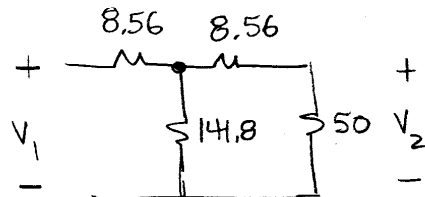

Important : Since $S_{11} = 0$

$$V_1 \text{ total} = V_1^+ \quad (\text{no } V_1^-), \quad \text{Since port 2 is matched}$$

$$V_2 \text{ total} = V_2^- \quad (\text{no } V_2^+)$$

Using Voltage division

$$V_2 = \left(\frac{50}{50 + 8.56} \right) \left(\frac{58.56 // 141.8}{58.56 // 141.8 + 8.56} \right) V_1 = \left(\frac{50}{58.56} \right) \left(\frac{41.44}{50} \right) V_1$$

$$\Rightarrow \frac{V_2}{V_1} = \frac{V_2^-}{V_1^+} = 0.707$$

The network is reciprocal and thus $S_{12} = S_{21} = 0.707$

$$\begin{bmatrix} 0 & 0.707 \\ 0.707 & 0 \end{bmatrix}$$

We should realize that, due to the existence of resistive elements, the network is not lossless. Let's verify

$$\text{Does } |S_{11}|^2 + |S_{21}|^2 = 1 ?$$

$$|0|^2 + |0.707|^2 = 0.5$$

$\Rightarrow$ Half the power ($10 \times \log 0.5 = -3\text{dB}$) is lost.


The network acts as a 3dB attenuator.

In general, loss in the ^{passive} network is given by

$$P_{\text{loss}} = 1 - |S_{11}|^2 - |S_{21}|^2$$


Another example

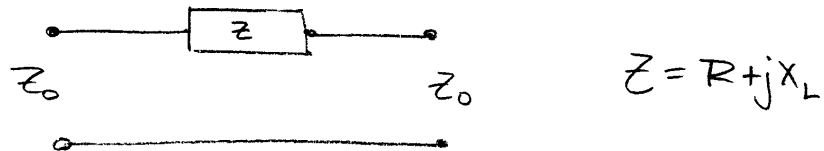What are the S-parameters for a series element?




Clearly reciprocal $\rightarrow S_{21} = S_{12}$

$$S_{11} = \left. \frac{V_1^-}{V_1^+} \right|_{\text{Port 2 matched } (V_2^+ = 0)}$$

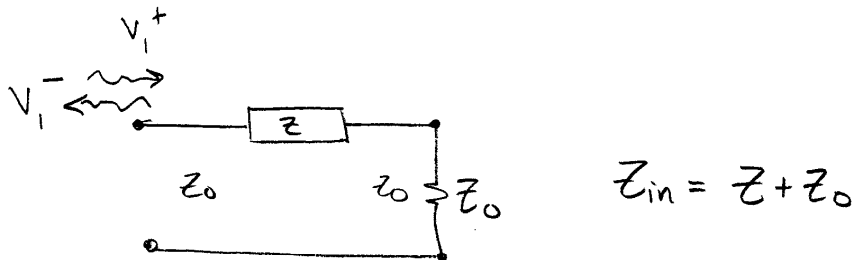

$$S_{11} = \frac{(Z + Z_0) - Z_0}{(Z + Z_0) + Z_0} \quad S_{11} = S_{22} = \frac{Z}{2Z_0 + Z}$$

$$S_{21} = \left. \frac{V_2^-}{V_1^+} \right|_{\text{Port 2 matched}}$$

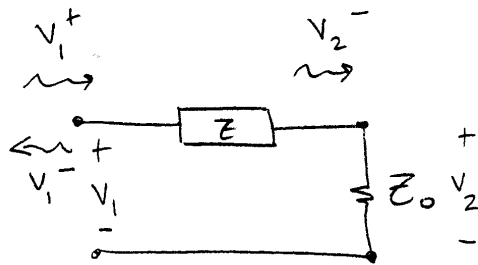

Since port 2 is matched,
no $V_2^+ \Rightarrow V_2 = V_2^-$

$$\frac{V_2}{V_1} = \frac{Z_0}{Z + Z_0} \quad \text{but} \quad V_1 = V_1^+ + V_1^- \quad (S_{11} \neq 0!)$$

$$V_2 = V_2^- = (V_1^+ + V_1^-) \frac{Z_0}{Z + Z_0} \quad (1)$$

$$\text{from before, } V_1^- = S_{11} V_1^+ = \frac{Z}{2Z_0 + Z} V_1^+ \quad (2)$$

$$(2) \rightarrow (1)$$


$$V_2^- = V_1^+ \left[1 + \frac{Z}{2Z_0 + Z} \right] \frac{Z_0}{Z + Z_0} = V_1^+ \left[\frac{2Z_0 + 2Z}{2Z_0 + Z} \cdot \frac{Z_0}{Z + Z_0} \right]$$

$$S_{21} = \frac{V_2^-}{V_1^+} = \frac{2Z_0}{2Z_0 + Z} = S_{12}$$

Additional information on the ABCD 2-port:


The Transmission Matrix

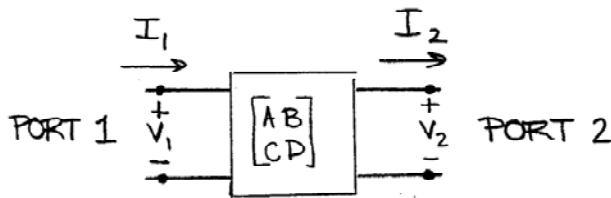- ▷ Also known as the "ABCD matrix" and "chain scattering parameters"
- ▷ Particularly useful when the overall network consists of a cascade of two-port networks



$$\begin{aligned} V_1 &= AV_2 + BI_2 \\ I_1 &= CV_2 + DI_2 \end{aligned} \quad \rightarrow \quad \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

Consider a cascade of two-ports

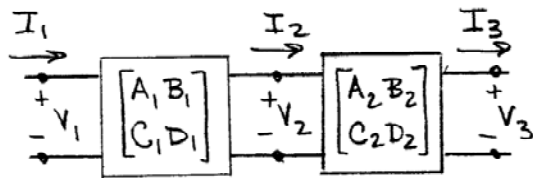

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_3 \\ I_3 \end{bmatrix}$$

The ABCD matrix of the cascade is equal to the product of the individual ABCD matrices.

TABLE 4.1 The $ABCD$ Parameters of Some Useful Two-Port Circuits

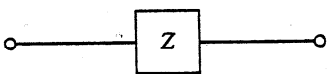
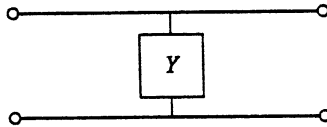
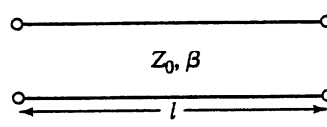
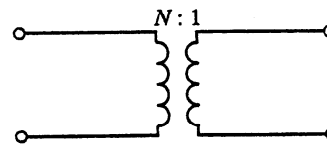
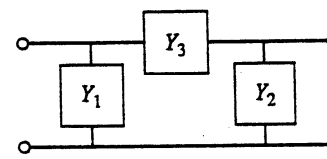
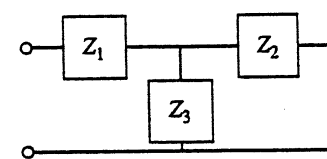
Circuit	$ABCD$ Parameters	
	$A = 1$ $C = 0$	$B = Z$ $D = 1$
	$A = 1$ $C = Y$	$B = 0$ $D = 1$
	$A = \cos \beta l$ $C = jY_0 \sin \beta l$	$B = jZ_0 \sin \beta l$ $D = \cos \beta l$
	$A = N$ $C = 0$	$B = 0$ $D = \frac{1}{N}$
	$A = 1 + \frac{Y_2}{Y_3}$ $C = Y_1 + Y_2 + \frac{Y_1 Y_2}{Y_3}$	$B = \frac{1}{Y_3}$ $D = 1 + \frac{Y_1}{Y_3}$
	$A = 1 + \frac{Z_1}{Z_3}$ $C = \frac{1}{Z_3}$	$B = Z_1 + Z_2 + \frac{Z_1 Z_2}{Z_3}$ $D = 1 + \frac{Z_2}{Z_3}$


TABLE 4.2 Conversions Between Two-Port Network Parameters

	S	Z	Y	$ABCD$
S_{11}	S_{11}	$\frac{(Z_{11} - Z_0)(Z_{22} + Z_0) - Z_{12}Z_{21}}{\Delta Z}$	$\frac{(Y_0 - Y_{11})(Y_0 + Y_{22}) + Y_{12}Y_{21}}{\Delta Y}$	$\frac{A + B/Z_0 - CZ_0 - D}{A + B/Z_0 + CZ_0 + D}$
S_{12}	S_{12}	$\frac{2Z_{12}Z_0}{\Delta Z}$	$\frac{-2Y_{12}Y_0}{\Delta Y}$	$\frac{2(AD - BC)}{A + B/Z_0 + CZ_0 + D}$
S_{21}	S_{21}	$\frac{2Z_{21}Z_0}{\Delta Z}$	$\frac{-2Y_{21}Y_0}{\Delta Y}$	$\frac{2}{A + B/Z_0 + CZ_0 + D}$
S_{22}	S_{22}	$\frac{(Z_{11} + Z_0)(Z_{22} - Z_0) - Z_{12}Z_{21}}{\Delta Z}$	$\frac{(Y_0 + Y_{11})(Y_0 - Y_{22}) + Y_{12}Y_{21}}{\Delta Y}$	$\frac{A + B/Z_0 - CZ_0 + D}{-A + B/Z_0 - CZ_0 + D}$
Z_{11}	$Z_0 \frac{(1 + S_{11})(1 - S_{22}) + S_{12}S_{21}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$	Z_{11}	$\frac{Y_{22}}{ Y }$	$\frac{A}{C}$
Z_{12}	$Z_0 \frac{2S_{12}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$	Z_{12}	$\frac{-Y_{12}}{ Y }$	$\frac{AD - BC}{C}$
Z_{21}	$Z_0 \frac{2S_{21}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$	Z_{21}	$\frac{-Y_{21}}{ Y }$	$\frac{1}{C}$
Z_{22}	$Z_0 \frac{(1 - S_{11})(1 + S_{22}) + S_{12}S_{21}}{(1 - S_{11})(1 + S_{22}) - S_{12}S_{21}}$	Z_{22}	$\frac{Y_{11}}{ Y }$	$\frac{D}{C}$
Y_{11}	$Y_0 \frac{(1 - S_{11})(1 + S_{22}) + S_{12}S_{21}}{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}$	$\frac{Z_{22}}{ Z }$	Y_{11}	$\frac{D}{B}$
Y_{12}	$Y_0 \frac{-2S_{12}}{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}$	$\frac{-Z_{12}}{ Z }$	Y_{12}	$\frac{BC - AD}{B}$
Y_{21}	$Y_0 \frac{-2S_{21}}{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}$	$\frac{-Z_{21}}{ Z }$	Y_{21}	$\frac{-1}{B}$
Y_{22}	$Y_0 \frac{(1 + S_{11})(1 - S_{22}) - S_{12}S_{21}}{(1 + S_{11})(1 - S_{22}) + S_{12}S_{21}}$	$\frac{Z_{11}}{ Z }$	Y_{22}	$\frac{A}{B}$
A	$\frac{(1 + S_{11})(1 - S_{22}) + S_{12}S_{21}}{2S_{21}}$	$\frac{Z_{11}}{Z_{21}}$	$\frac{-Y_{22}}{Y_{21}}$	A
B	$Z_0 \frac{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}{2S_{21}}$	$\frac{ Z }{Z_{21}}$	-1	B
C	$\frac{1}{Z_0} \frac{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}{2S_{21}}$	$\frac{1}{Z_{21}}$	$\frac{Y_{21}}{- Y }$	C
D	$\frac{(1 - S_{11})(1 + S_{22}) + S_{12}S_{21}}{2S_{21}}$	$\frac{Z_{22}}{Z_{21}}$	$\frac{Y_{21}}{-Y_{11}}$	D

211

$$|Z| = Z_{11}Z_{22} - Z_{12}Z_{21}; \quad |Y| = Y_{11}Y_{22} - Y_{12}Y_{21}; \quad \Delta Y = (Y_{11} + Y_0)(Y_{22} + Y_0) - Y_{12}Y_{21}; \quad \Delta Z = (Z_{11} + Z_0)(Z_{22} + Z_0) - Z_{12}Z_{21}; \quad Y_0 = 1/Z_0$$

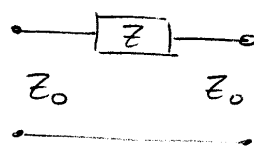An example using the above conversation table:



$$[ABCD] = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix}$$

from table 4.2

$$S_{11} = \frac{A + B/Z_0 - CZ_0 - D}{A + B/Z_0 + CZ_0 + D} = \frac{1 + Z/Z_0 - 1}{1 + Z/Z_0 + 1} = \frac{Z/Z_0}{2 + Z/Z_0}$$

$$S_{11} = \frac{Z}{2Z_0 + Z} \quad \checkmark \quad S_{22} = S_{11}$$


$$S_{21} = \frac{2}{A + B/Z_0 + CZ_0 + D} = \frac{2}{2 + Z/Z_0}$$

$$S_{21} = \frac{2Z_0}{2Z_0 + Z} \quad \checkmark \quad S_{21} = S_{12}$$

Equivalent Circuits For Two-Port Networks



It is often handy to construct equivalent circuits for two-port networks. The most common equivalent circuits are the T- and π -networks.


▷ T Equivalent

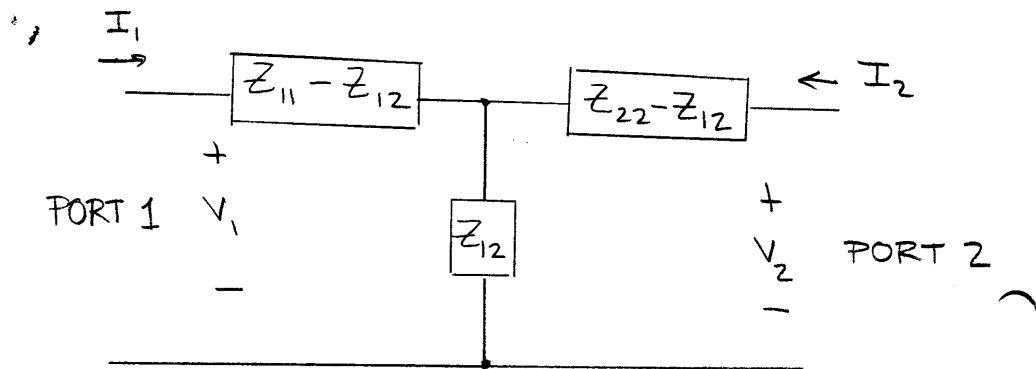

How is this derived?


$$\bullet \quad Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$$

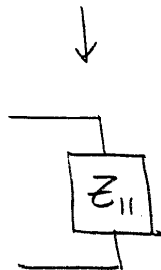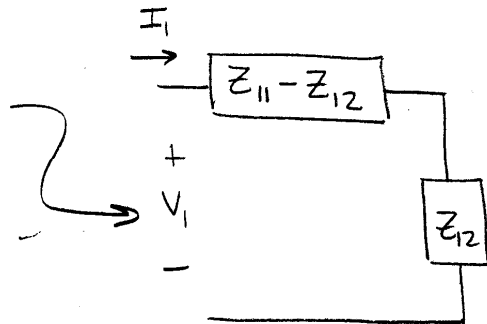

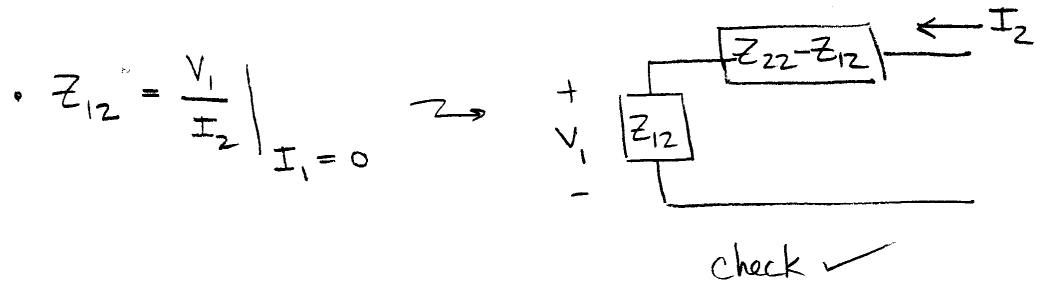

And similarly with Z_{21} & Z_{22} .

▷ π Equivalent

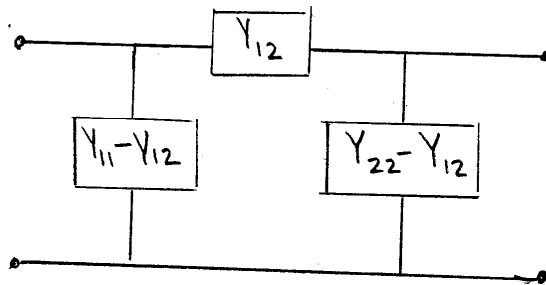


<end lecture 16 >

Passive Components at Microwave Frequencies

▷ Resistors

At DC  $V = IR$

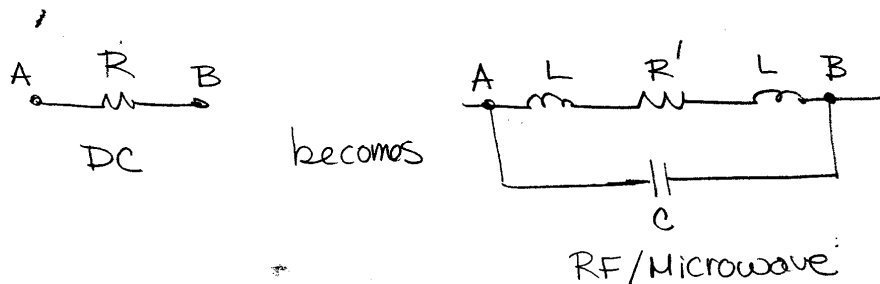At RF/Microwave frequencies a simple resistor is no longer such. Rather, a variety of parasitics emerge.



$L \rightarrow$ inductance from lead wire

$C \rightarrow$ parasitic capacitance


$R' \rightarrow$ skin effect ($R' > R$)

} often frequency dependent


Overall the impedance tends to decrease with increasing frequency due to parasitics

Resistor Types

- Carbon

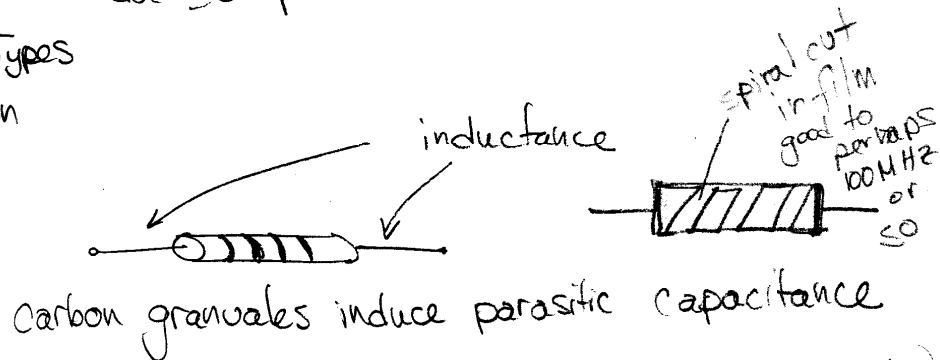


- Planar thin or thick film resistor

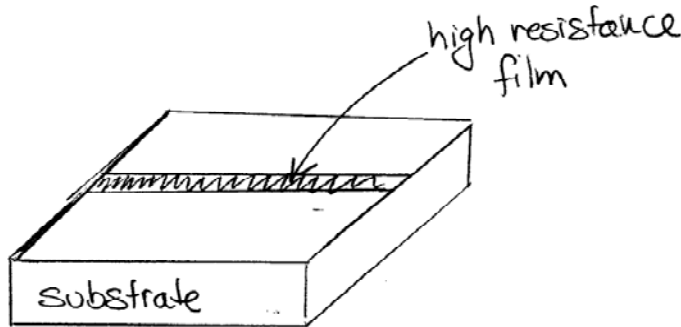

ex. NiCr ("Nichrome")
 Ta_xNy (Tantalum nitride)
 Doped Semiconductor

→ used extensively in Monolithic Microwave Integrated Circuits (MMICs)

- Chip Resistor

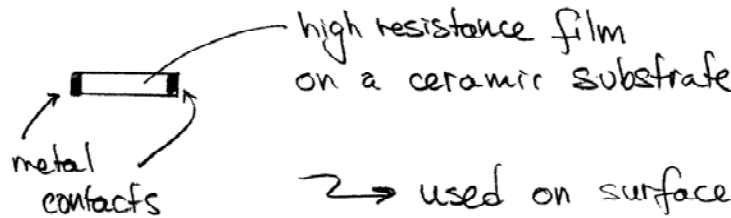

high resistance film on a ceramic substrate

→ used on surface mount boards

→ smaller component not only reduce real estate; parasitics are smaller → good to higher freq.


CHIP SIZE CODE	WIDTH (MILS)	LENGTH (MILS)
1218	120	180
1206	120	60
0805	80	50
0603	60	30
0504	50	40
0402	40	20

Capacitors

→ Again, parasitics a problem. Behavior strongly influenced by quality of the dielectric.

Capacitor Types


- Chip capacitor

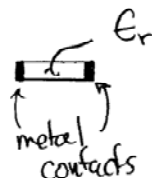

C up to a couple 100pF → depends on frequency range

(63)

• Metal-Insulator-metal (MIM)

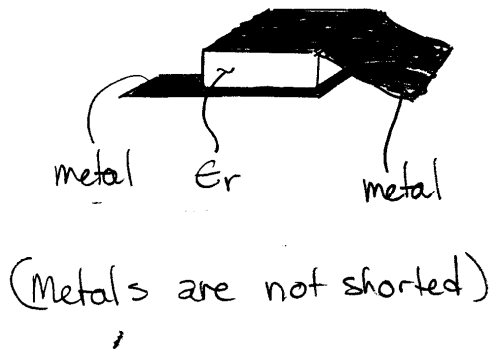

MIM's can provide C up to $\sim 25 \text{ pF}$

example dielectrics:

SiO_2 ($\epsilon_r \sim 3.9$)

SiN_3 ($\epsilon_r \sim 6-7$)

Al_2O_3 ($\epsilon_r \sim 6-9$)

Ta_2O_5 ($\epsilon_r \sim 20-25$)

• Transmission line




shunt stub $C < 0.1 \text{ pF}$
(more on this later)



Interdigital $C < 0.5 \text{ pF}$

The values quoted are approximate,

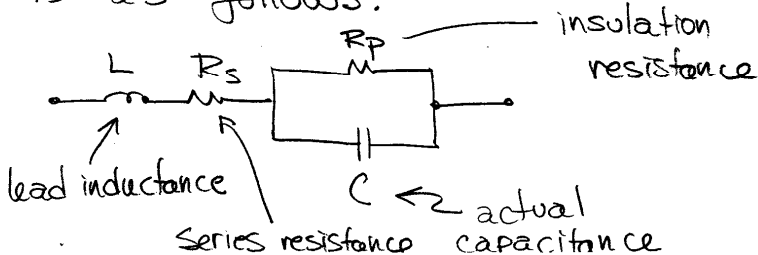One potential equivalent circuit of a chip capacitor is as follows:




clearly non-ideal

(64)

EE43308-17

The Lumped inductor.

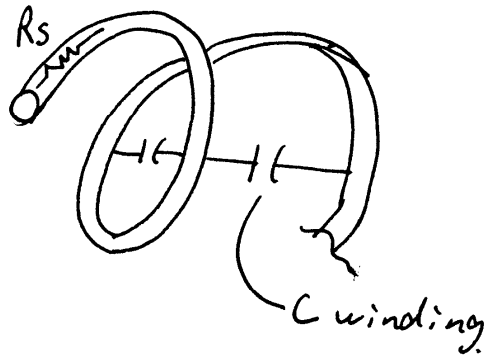


a practical coil inductor ~~is~~ has
a series resistance R_s and
interwinding capacitance, C_d

The R_s is the dc resistance of
the wire - plus additional frequency
dependent R due to skin effect
and radiation loss.


ideal

Equivalent circuit.

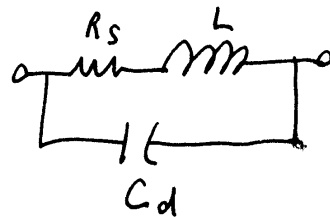

EE43308-18.

the impedance of the real inductor is:

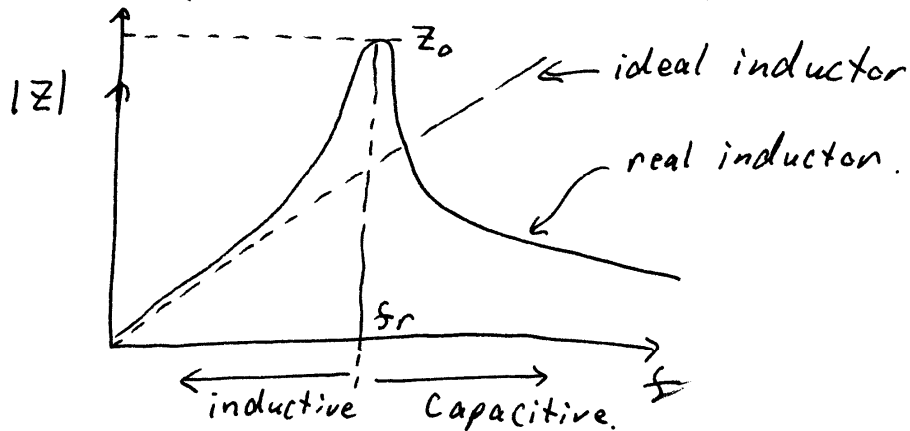

← inductor properties → (see Lab 2)

SRF $\Rightarrow$ self resonant frequency f_r

$$f_r = \frac{1}{2\pi\sqrt{LC_d}} \quad \begin{matrix} \text{Low freq.} \\ L \Rightarrow \text{value of inductor.} \end{matrix}$$

 $R_{dc} \rightarrow$ Low frequency R_s of the inductor.

$$R_s = \frac{\omega_0 L}{Q_w} \quad \begin{cases} Q_w = Q \text{ of inductor at frequency } \omega_0 \\ \omega_0 = 2\pi f_r \\ \text{(see Lab 2)} \end{cases}$$

high frequency R_s .

EE43308-17.

4

example.

Coilcraft LL2012-F series.

$$L = 10 \text{ nH} \rightarrow Q = 16 @ f_q = 100 \text{ MHz.}$$

$$Q = 46 @ f_q = 800 \text{ MHz}$$

$$S_{RF} = 2500 \text{ MHz.}$$

$$R_{DC} = 0.3 \Omega.$$

to find the model at 800 MHz .


$$S_{RF} = \frac{1}{2\pi\sqrt{LC}} \Rightarrow C = \frac{1}{(2\pi \times 8 \times 10^8)^2 \times 10^{-8}}$$

$$C = 3.96 \text{ pF}$$

$$Q = \frac{\omega L}{R_s} = \frac{\omega L}{R_s}$$

$$R_s = \frac{(2\pi \times 8 \times 10^8)^2 \times 10^{-8}}{46}$$

$$R_s = 1.093 \Omega.$$


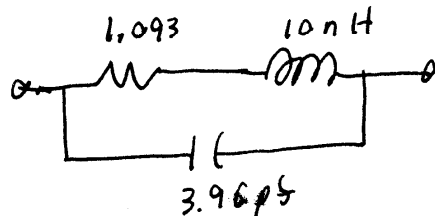
So the model ~~is~~ at 800 MHz is

EE433-08 Planer Microwave Circuit Design Notes

An actual data sheet:

TYPE LL2012-FHL

TOKO Part Number	Inductance & Tolerance					Q min.	Q (Typ.)							SRF (MHz) min.	RDC (Ω) max.	IDC (mA) max.
	at 100MHz		at 800 (500, 300, 200) MHz													
	Lo (nH)	L Tol.*	Lo (nH)	L Tol.*	Freq. (MHz)		100 MHz	100 MHz	300 MHz	500 MHz	800 MHz	1000 MHz	1800 MHz			
LL2012-FHL1N5S	1.5	S	1.5	± 0.5nH	800	11	15.3	27.5	37.5	52.0	61.5	79.3	4000	0.10	300	
LL2012-FHL1N8S	1.8	S	1.7	± 0.5nH	800	12	14.0	25.0	33.9	46.6	54.0	78.4	4000	0.10	300	
LL2012-FHL2N2S	2.2	S	2.1	± 0.5nH	800	12	16.7	29.5	39.9	55.0	62.6	96.4	3800	0.10	300	
LL2012-FHL2N7S	2.7	S	2.42	± 0.5nH	800	12	15.5	27.5	36.8	50.8	57.8	89.0	3600	0.10	300	
LL2012-FHL3N3S	3.3	S	3.0	± 0.5nH	800	12	15.4	29.0	39.2	52.6	59.2	96.4	3400	0.10	300	
LL2012-FHL3N9S	3.9	S	3.7	± 0.5nH	800	12	16.0	29.7	39.7	53.4	59.7	76.8	3200	0.10	300	
LL2012-FHL4N7S	4.7	S	4.6	± 0.5nH	800	12	16.5	30.4	40.9	54.3	61.0	81.0	2800	0.12	300	
LL2012-FHL5N6S	5.6	S	5.7	± 0.5nH	800	12	17.0	31.3	42.1	55.2	61.0	76.9	2800	0.15	300	
LL2012-FHL6N8J	6.8	J	6.7	± 10%	800	12	18.7	33.3	44.6	58.1	63.9	89.7	2100	0.15	300	
LL2012-FHL8N2J	8.2	J	8.2	± 10%	800	15	18.5	32.2	42.4	54.8	59.5	73.2	2000	0.18	300	
LL2012-FHL10NJ	10	J	10.2	± 10%	800	15	18.9	33.7	44.4	56.9	61.5	75.7	1600	0.20	300	
LL2012-FHL12NJ	12	J	12.7	± 10%	800	16	20.5	36.5	47.5	60.8	65.9	79.8	1350	0.22	300	

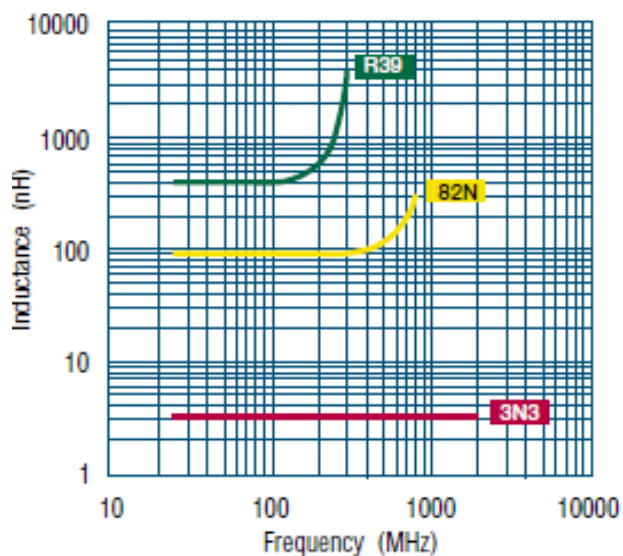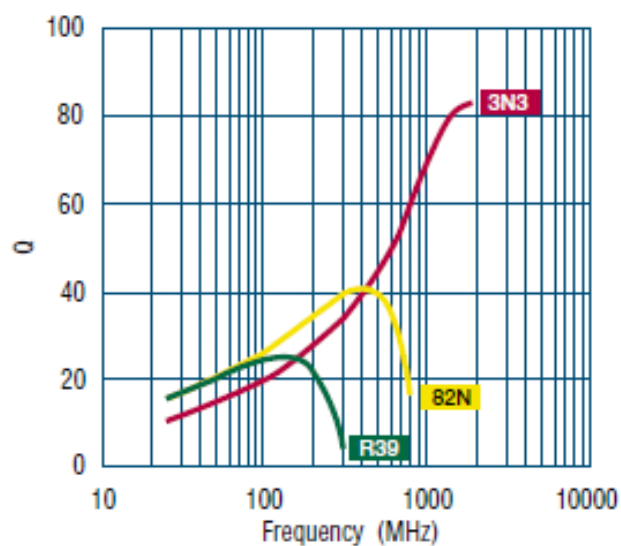

EE43308-17

5

Comments on inductor Q & effective value:


for an inductor $Q = \frac{\chi_L}{R_S}$

at low frequencies χ_L is small & Q is small. For our example inductor:

$Q = 16$ at 100MHz & $Q = 46$ at 800MHz .


the Q will increase to some maximum value at a frequency f_0 (not SRF)

Below Resonance;

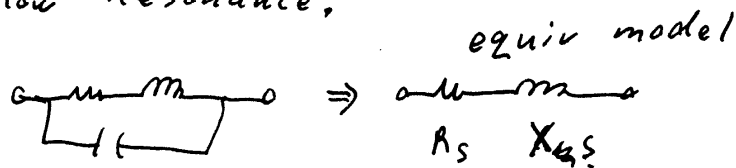


note that at SRF $\Rightarrow \chi_S = 0$ because

$\chi_C = \chi_L$ so $\text{para } Q = 0$

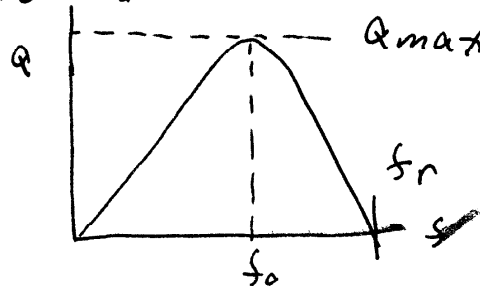


EE43308-17

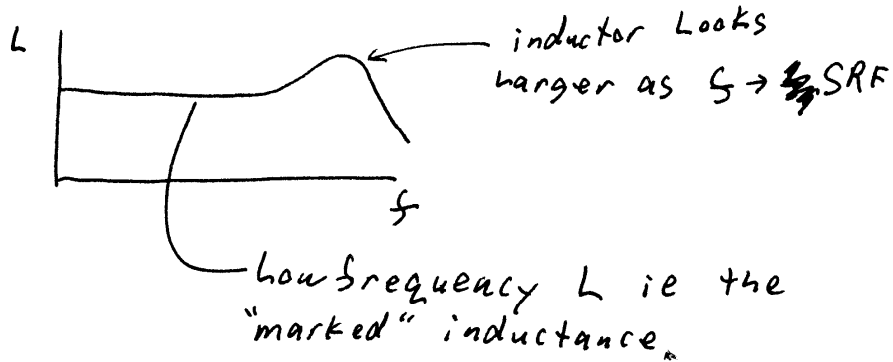data sheets often display an
"effective" L vs frequency



Real Capacitor model

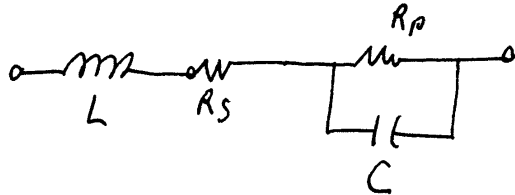

C = actual capacitor

$R_s \rightarrow$ Lead or termination resistance.

$L \rightarrow$ Lead or package parasitic inductance.

$R_p \rightarrow$ insulation resistance & dielectric loss.

R_s and R_p are functions of frequency

R_p is usually large & is ignored.


EE43308-17

78

Real capacitor model



plotting $Z(f)$ ← capacitive. inductive

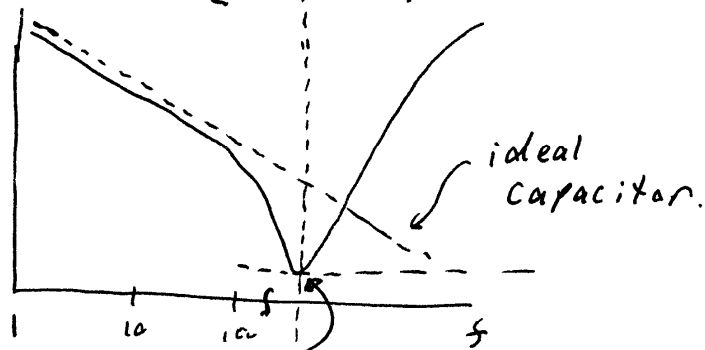

$$f_r \Rightarrow \text{SRF}$$

$$Z(f_r) = R_{s\text{ or }L} + j0$$

L series resistance.


{ note that near resonance the
actual $-jX_c$ is greater than an ideal
capacitor ~~at this~~

43308-17

8

Example: from Lab 2 curves for a


100 pF capacitor:

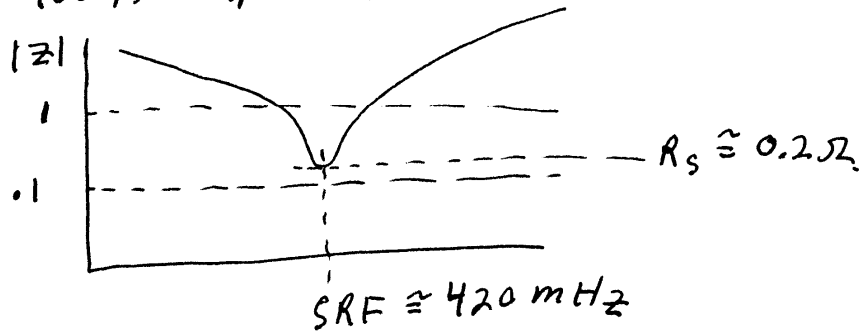

$$L_s = \frac{1}{(2\pi 420 \times 10^6)^2 10^{-10}}$$

$$L_s = 1.44 \text{ nH}$$

So the model is

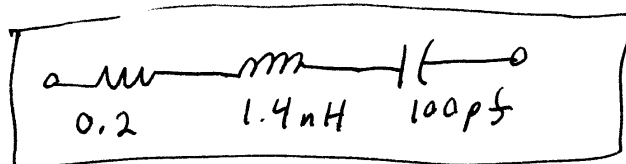

For the same value capacitor.

The smaller the physical part -

the higher the SRF $\Rightarrow$ the smaller L_s is.

<end lecture 17>