

Recall that the average power flow is constant at any point along a lossless TL. We have just discovered that the voltage oscillates on a mismatched line. Taken together, these two facts suggest that the impedance looking down the line will vary with position on a mismatched line!

At a distance $l = -z$ from the load, the input impedance seen looking toward the load is,

$$Z_{in} = \frac{V(-l)}{I(-l)} = \frac{V_0^+ [e^{j\beta l} + \Gamma_L e^{-j\beta l}]}{V_0^+ [e^{j\beta l} - \Gamma_L e^{-j\beta l}]} Z_0 = \frac{1 + \Gamma_L e^{-j2\beta l}}{1 - \Gamma_L e^{-j2\beta l}} Z_0$$

Also, $\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$

$$Z \rightarrow \boxed{Z_{in}(-l) = Z_0 \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l}}$$

The TL Impedance Equation

Special Cases of a lossless terminated TL

I. Open-circuit load $\rightarrow Z_L = \infty$

$$\Gamma = \frac{\infty - Z_0}{\infty + Z_0} = 1$$


↑ The reflection coefficient at the load

$$Z_0 \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} = \frac{Z_L + jZ_0 \tan \beta l}{1 + jZ_L \tan \beta l / Z_0}$$

$$\xrightarrow{Z_L} Z_{in}(-l) = Z_0 \frac{\infty + jZ_0 \tan \beta l}{Z_0 + j\infty \tan \beta l} = -jZ_0 \cot \beta l$$

$$Z_{in, open}(l) = -jZ_0 \cot \beta l$$

Purely Reactive!

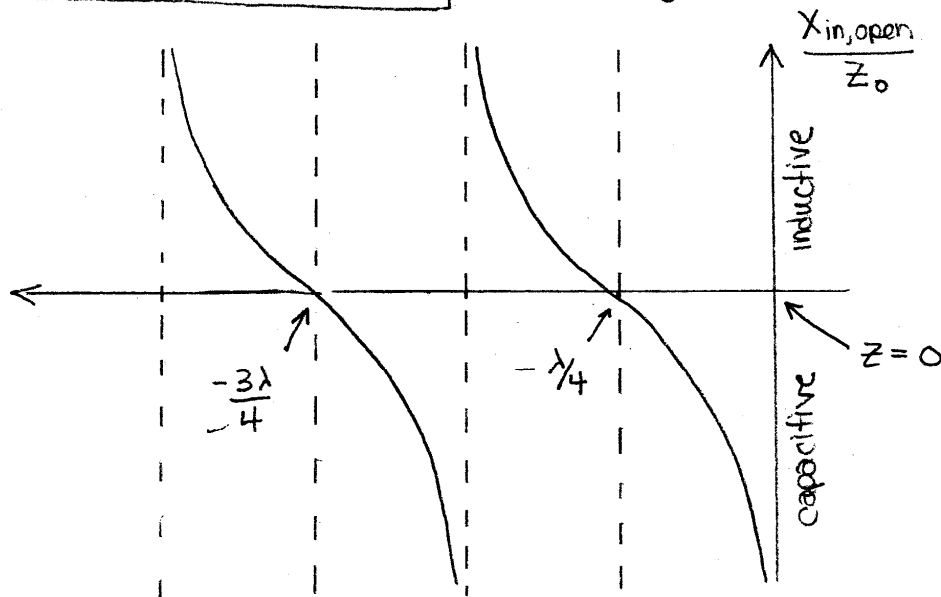


stop 9/10/08.

II. Short-Circuit load $\rightarrow Z_L = 0$

$$\Gamma_L = \frac{0 - Z_0}{0 + Z_0} = -1$$

$$Z_{in}(-l) = Z_0 \frac{0 + jZ_0 \tan \beta l}{Z_0 + j0 \tan \beta l} = jZ_0 \tan \beta l$$
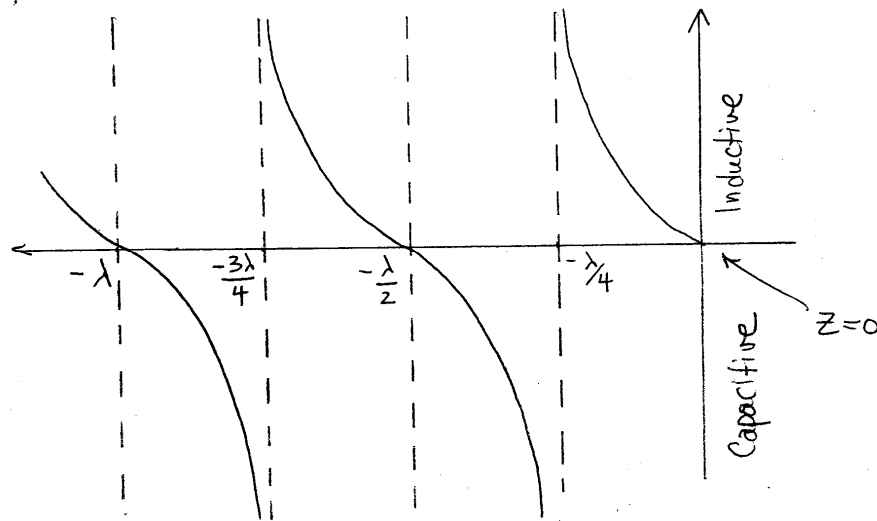
$$Z_{in, short}(-l) = jZ_0 \tan \beta l \quad \text{Purely Reactive!}$$



III. Matched Load $\rightarrow Z_L = Z_0, \Gamma = 0, \boxed{Z_{in, matched}(l) = Z_0}$

* An important fact to remember is that an open-circuit or a short-circuit section of TL may provide any value of reactance. We will use this to our advantage in "stub matching."

4/23/08

(36)