

EE433-08 Homework 1  
Due 9/30/2008

Do problems 2.1, 2.2, 2.6, 2.11, 2.18 in the text as shown:

Problems 87

**PROBLEMS**

2.1 The current on a transmission line is given as  $i(t) = 1.2 \cos(1.51 \times 10^{10}t - 80.3z)$  A. Determine (a) the frequency, (b) the wavelength, (c) the phase velocity, and (d) the phasor representation of this current.

2.2 A transmission line has the following per unit length parameters:  $L = 0.2 \mu\text{H/m}$ ,  $C = 300 \text{ pF/m}$ ,  $R = 5 \Omega/\text{m}$ , and  $G = 0.01 \text{ S/m}$ . Calculate the propagation constant and characteristic impedance of this line at 500 MHz. Recalculate these quantities in the absence of loss ( $R = G = 0$ ).

2.6 RG-402U semi-rigid coaxial cable has an inner conductor diameter of 0.91 mm, and a dielectric diameter (equal to the inner diameter of the outer conductor) of 3.02 mm. Both conductors are copper, and the dielectric material is Teflon. Compute the  $R$ ,  $L$ ,  $G$ , and  $C$  parameters of this line at 1 GHz, and use these results to find the characteristic impedance and attenuation of the line at 1 GHz. Compare your results to the manufacturer's specifications of  $50 \Omega$  and  $0.43 \text{ dB/m}$ , and discuss reasons for the difference.

2.11 A  $100 \Omega$  transmission line has an effective dielectric constant of 1.65. Find the shortest open-circuited length of this line that appears at its input as a capacitor of  $5 \text{ pF}$  at  $2.5 \text{ GHz}$ . Repeat for an inductance of  $5 \text{ nH}$ .

2.18 A generator is connected to a transmission line as shown below. Find the voltage as a function of  $z$  along the transmission line. Plot the magnitude of this voltage for  $-\ell \leq z \leq 0$ .

